

POWER ELECTRONICS LAB MANUAL

FOR

IV SEMESTER B.E (EC / TC / ML)

(For private circulation only)

VISVESVARAYA TECHNOLOGICAL UNIVERSITY



Name :


Reg no :

DEPARTMENT OF ELECTRONICS & COMMUNICATION
SRI SIDDHARTHA INSTITUTE OF TECHNOLOGY
MARLUR, TUMKUR-572105


CONTENTS

<u>Experiment No</u>	<u>Page. No</u>
1. SCR Characteristics	3
2. TRIAC Characteristics	9
3. MOSFET Characteristics	15
4. IGBT Characteristics	17
5. RC Triggering Circuit – HWR & FWR	19
6. UJT Triggering of SCR	23
7. (LC Commutation Circuit) Oscillation Chopper Circuit	29
8. UJT Triggering of SCR – HWR & FWR	33
9. Digital Firing Circuit	39
10. AC Voltage control by using TRIAC & DIAC	41
11. Single Phase FWR	45
12. Impulse Commutated Chopper	49
13. Speed control of a 1 ϕ Induction motor	51
14. Speed Control of Universal motor	53
15. Series Inverter	55
16. Parallel Inverter	57
Question bank	58
Viva questions	59
Data sheets	64


Circuit Diagram: -

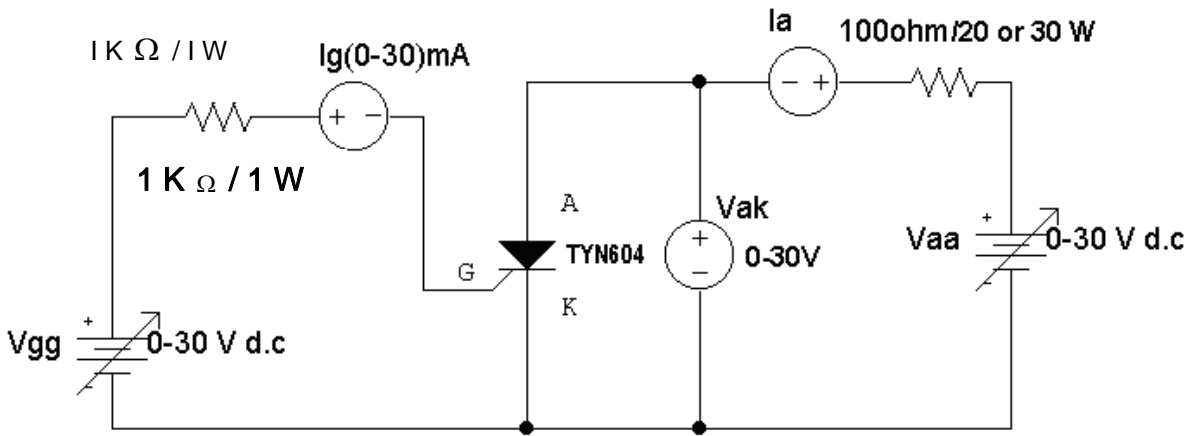

Ideal Graph: -

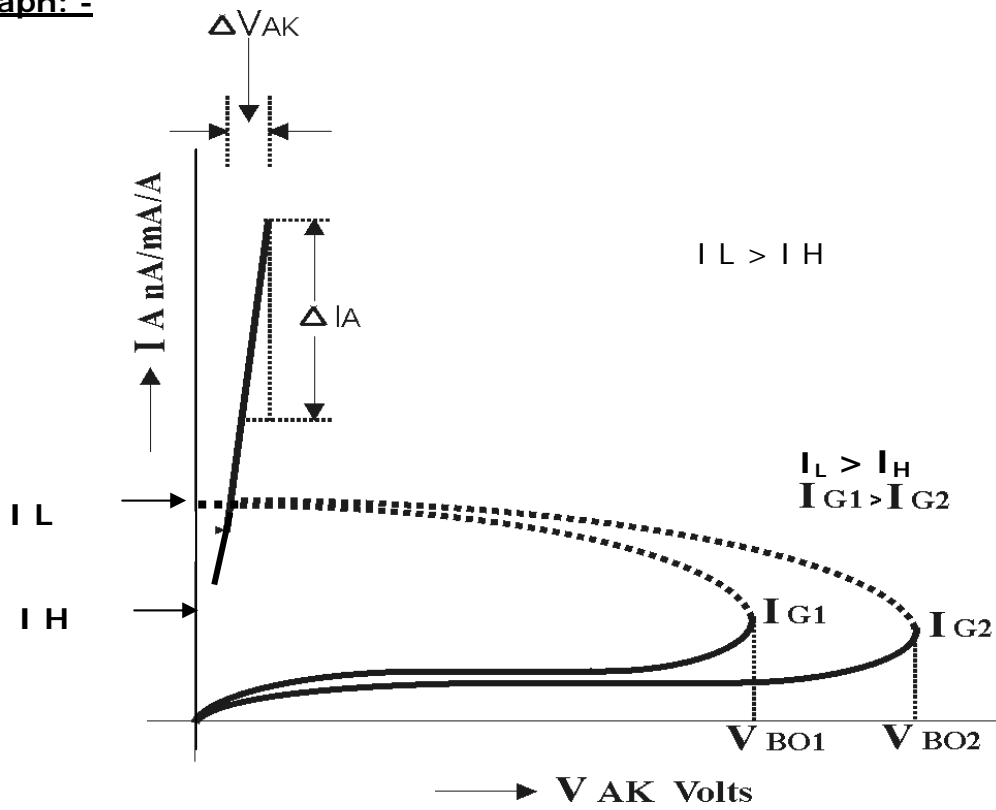

Base Diagrams of 2N3669/70 & TY604: -

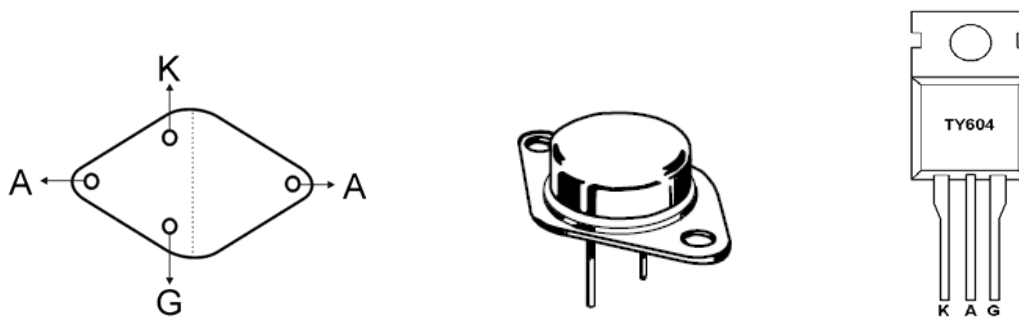

Experiment No: 1

DATE: __/__/____

S.C.R. Characteristics

Aim: -

To study the V-I characteristics of S.C.R. and determine the Break over voltage, on state resistance Holding current. & Latching current

Apparatus required: -

SCR – TY604, Power Supplies, Wattage Resistors, Ammeter, Voltmeter, etc.,

Procedure: -

1. Connections are made as shown in the circuit diagram.
2. The value of gate current I_G , is set to convenient value by adjusting V_{GG} .
3. By varying the anode- cathode supply voltage V_{AA} gradually in step-by-step, note down the corresponding values of V_{AK} & I_A . Note down V_{AK} & I_A at the instant of firing of SCR and after firing (by reducing the voltmeter ranges and in creasing the ammeter ranges) then increase the supply voltage V_{AA} . Note down corresponding values of V_{AK} & I_A .
4. The point at which SCR fires, gives the value of break over voltage V_{BO} .
5. A graph of V_{AK} V/S I_A is to be plotted.
6. The on state resistance can be calculated from the graph by using a formula.
7. The gate supply voltage V_{GG} is to be switched off
8. Observe the ammeter reading by reducing the anode-cathode supply voltage V_{AA} . The point at which the ammeter reading suddenly goes to zero gives the value of Holding Current I_H .
9. Steps No.2, 3, 4, 5, 6, 7, 8 are repeated for another value of the gate current I_G .

Designing Equations:-

Wkt,

Let $I_a = 300\text{mA}$
 $V_{scr} = 1\text{v}$
 $V_{aa} = 30\text{v}$

$$V_{aa} = I_a R_L + V_{scr}$$

$$R_L = \frac{V_{aa} - V_{scr}}{I_a}$$

$$R_L = \frac{30-1}{300 \times 10^{-3}} = 96.66\Omega \cong 100\Omega$$

Wattage:-

Power in watts = $I^2 R_L = (300 \times 10^{-3})^2 \times 100 = 9 \text{ watts}$ (select 20 watts)

\therefore Load resistor = $R_L = 100\Omega$, 20watts

Gate Resistance (Rg):-

Wkt,

Let $I_g = 15\text{mA}$
 $V_{gt} = 1\text{v}$
 $V_{gg} = 15\text{v}$

$$V_{gg} = I_g R_g + V_{gt}$$

$$R_g = \frac{V_{gg} - V_{gt}}{I_g}$$


$$R_g = \frac{15-1}{15 \times 10^{-3}} = 933\Omega \cong 1\text{K}\Omega$$

Wattage:-

Power in watts = $I^2 R_g = (15 \times 10^{-3})^2 \times 10^3 = 0.225\text{w}$ (select 1 watt)

\therefore Gate resistor = $R_g = 1\text{K}\Omega$, 1 watts

Note: - Follow the same design procedure for TRIAC connection sting

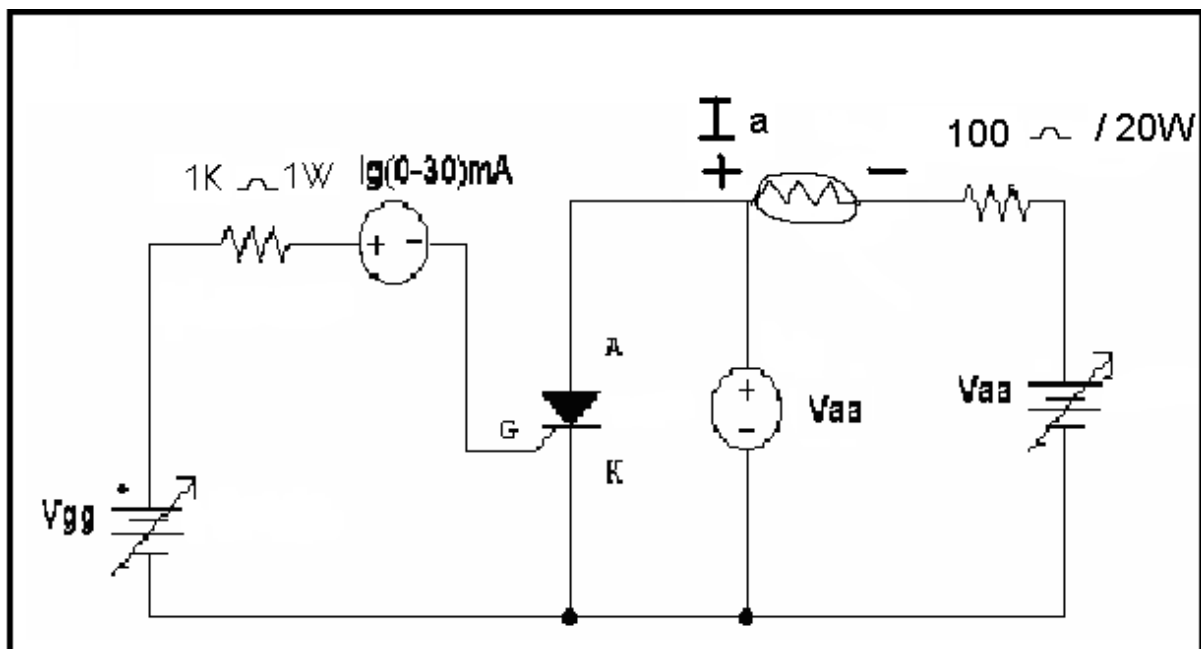Latching Current

Alternate Method: -

1. Connections are made as shown in the circuit diagram
2. Adjust the value of I_g to zero or some minimum value
3. By varying the voltage V_{ak} from 0 to 10 volts with a step of 2 volts, note down corresponding values of I_a
4. Now apply the gate voltage gradually, until SCR fires, then note down the values of I_g and also the values of I_a and V_{ak}
5. Increase V_{aa} to some value and note down I_a and V_{ak}
6. Reduce gate voltage to zero, observe ammeter reading by reducing V_{aa} which gives the values of I_h (holding current) at the point at which, current suddenly drops to zero
7. Repeat the steps 2, 3, 4, 5 & 6 for different values of break over voltage
8. Plot a graph of V_{ak} v/s I_a
9. The on state resistance can be calculated from the graph by using formula,

$$R_{ON - STATE} = \frac{\Delta V_{AK}}{\Delta I_A} \Omega$$

Tabular column: -

$I_g = \underline{\hspace{2cm}} \text{mA}$

Sl.No	V_{AK} Volts	I_A $\mu\text{A}/\text{mA}/\text{A}$

$I_g = \underline{\hspace{2cm}} \text{mA}$

Sl.No	V_{AK} Volts	I_A $\mu\text{A}/\text{mA}/\text{A}$

Procedure (Latching current)





1. connections one made as shown in the circuit diagram
2. Set V_{gg} at 7 volts
3. Set V_{aa} at particular value, observe I_a , by operating the switch (on & off).
if it goes to zero after opening of the switch, indicates $I_a < I_L$
4. Repeat step 3 such that the current I_a should not go to zero after opening of the switch. Then I_a gives the value of I_L .

Viva questions: -

1. Explain the working operation of VI characteristics of S.C.R.
2. Define Holding current, Latching current on state resistance, Break down voltage
3. Explain the working operation of S.C.R. characteristics by using two transistor analogy
4. Write an expression for anode current
5. Mention the applications of S.C.R.?

.....
Signature of the staff with date

CIRCUIT DIAGRAM: -

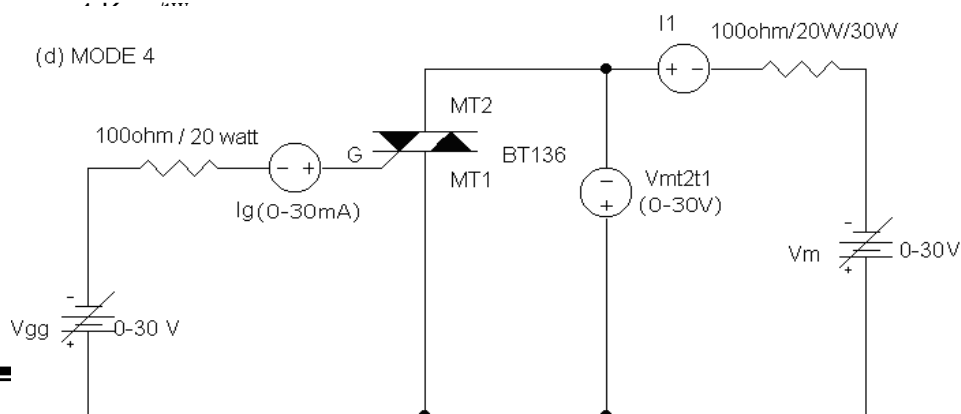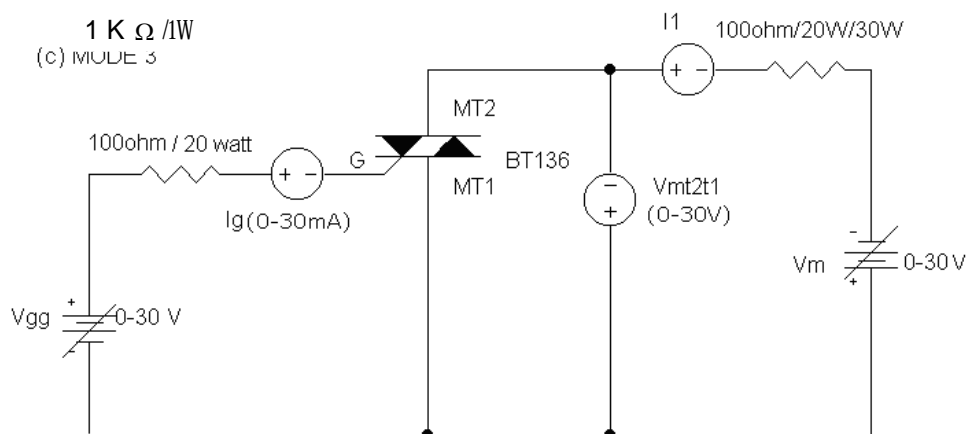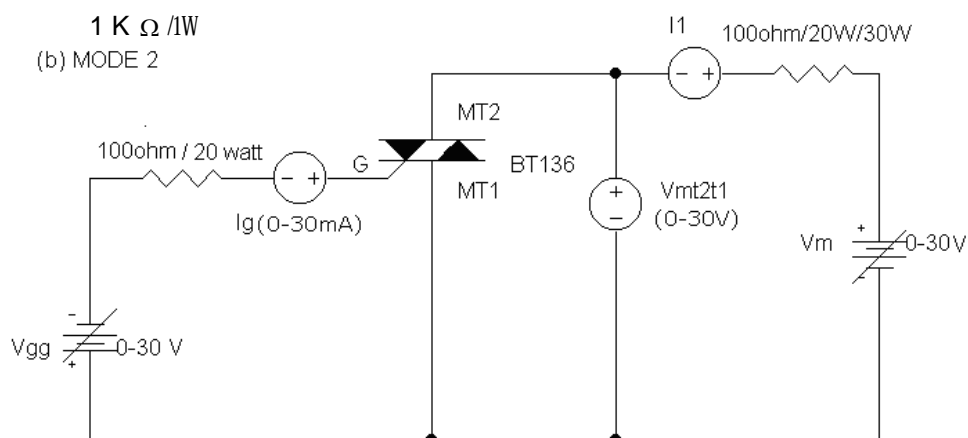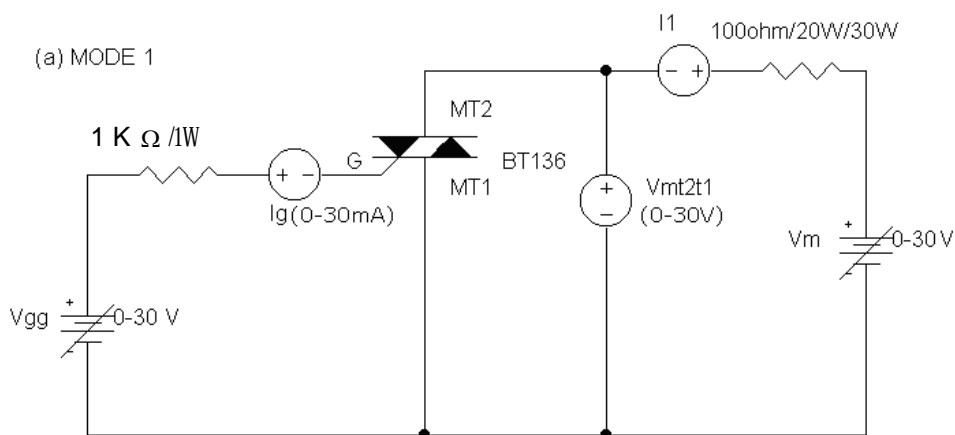

Experiment No: 2

DATE: __/__/____

TRIAC Characteristics

Aim: -

To study the v-1 characteristics of a TRIAC in both directions and also in different (1, 2, 3 & 4) modes of operation and determine break over voltages, holding current, latching current and comment on sensitivities.

Apparatus required: -

TRIAC – BT 136, power supplies, wattage resistors, ammeter, voltmeter, etc.,

Procedure: -

I mode


1. Connections are made as shown in the circuit diagram (a)
2. The value of gate current i_g is set to convenient value by adjusting v_{gg} .
3. By varying the supply voltage V_m gradually in step-by-step, note down the corresponding values of V_{mt2t1} and i_1 . Note down V_{mt2t1} and i_1 at the instant of firing of TRIAC and after firing (by reducing the voltmeter ranges and increasing the ammeter ranges) then increase the supply voltage V_{mt2t1} and i_1 .
4. The point at which TRIAC fires gives the value of break over voltage v_{bo1}
5. A graph of v_{mt2t1} v/s i_1 is to be plotted.
6. The gates supply voltage. V_{gg} is to be switched off
7. Observe the am meter reading by reducing the supply voltage v_{mt} . The point at which the ammeter reading suddenly goes to zero gives the value of holding current i_h .

II mode: -


1. Connections are made as shown in the circuit diagram (b)
2. The gate current is set as same value as in i-mode
3. Repeat the step no. s 3, 4, 5, 6, & 7 of I-mode

Characteristic curve: -

Normal Method

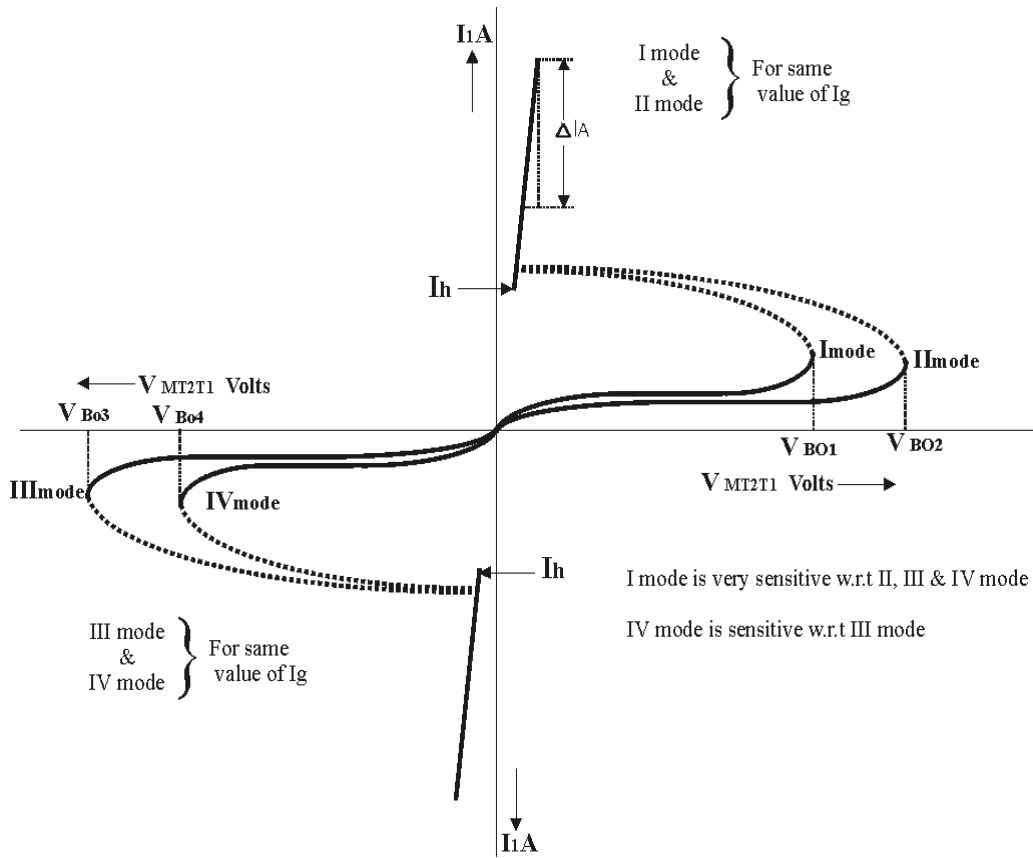

Alternate Method

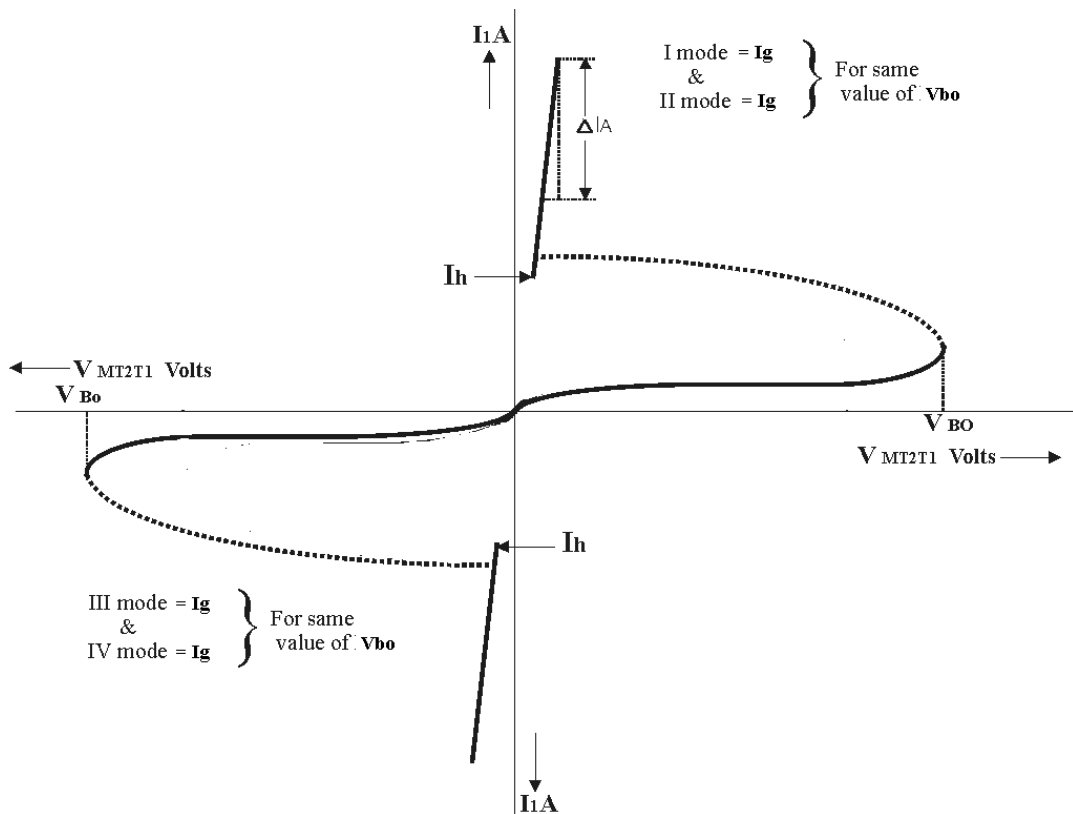

III mode

1. Connections are made as shown in the circuit diagram (c).
2. Step nos 2, 3, 4, 5, 6, & 7 are to be repeated as in i-mode.

IV mode

1. Connections are made as shown in the circuit diagram (d)
2. Repeat the step nos 2, 3, 4, 5, 6, & 7 of i-mode.

Alternate Method: -

1. Connections are made as shown in the circuit diagram
2. Adjust the value of I_g to zero or some minimum value
3. By varying the voltage V_{mt2mt1} from 0 to 10 volts with a step of 2 volts, note down corresponding values of I_1
4. Now apply the gate voltage gradually, until SCR fires, then note down the values of I_g and also the values of I_1 and V_{mt2mt1} .
5. Increase V_m to some value and note down I_1 and V_{mt2mt1} .
6. Reduce gate voltage to zero, observe ammeter reading by reducing V_m which gives the values of I_h (holding current) at the point at which, current suddenly drops to zero
7. Repeat the steps 2, 3, 4, 5 & 6 for different values of break over voltages
8. Plot a graph of V_{mt1mt2} v/s I_1
9. Repeat the steps 1, 2, 3, 4, 5, 6 & 7 for different modes
10. Compare sensitivity of TRIAC and comment on sensitivities.
11. Refer same design procedure for selection of R_L and R_g as that of SCR.
12. Follow the same procedure as that of SCR experiment to find latching current.

Tabular column: -

I-mode

$i_g =$ ma

Sl.no	V_{TRIAC} volts	I_{TRIAC} ma

II-mode

$I_g =$ ma

Sl.no	V_{TRIAC} volts	I_{TRIAC} ma

III-mode

$i_g =$ ma


Sl.no	V_{TRIAC} volts	I_{TRIAC} ma

IV-mode

$I_g =$ ma

Sl.no	V_{TRIAC} volts	I_{TRIAC} ma

Base diagram of BT136:

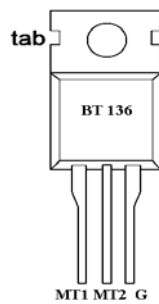


Viva questions: -


1. Explain the different working modes of operations of a TRIAC?
2. Why i-mode is more sensitive among all modes?
3. What are the applications of TRIAC
4. Compare SCR, TRIAC & DIAC
5. Why I & II modes are operating in Ist quadrant and III & IV modes are operating in IIIrd quadrant?

.....
Signature of the staff with date


Circuit Diagram: -

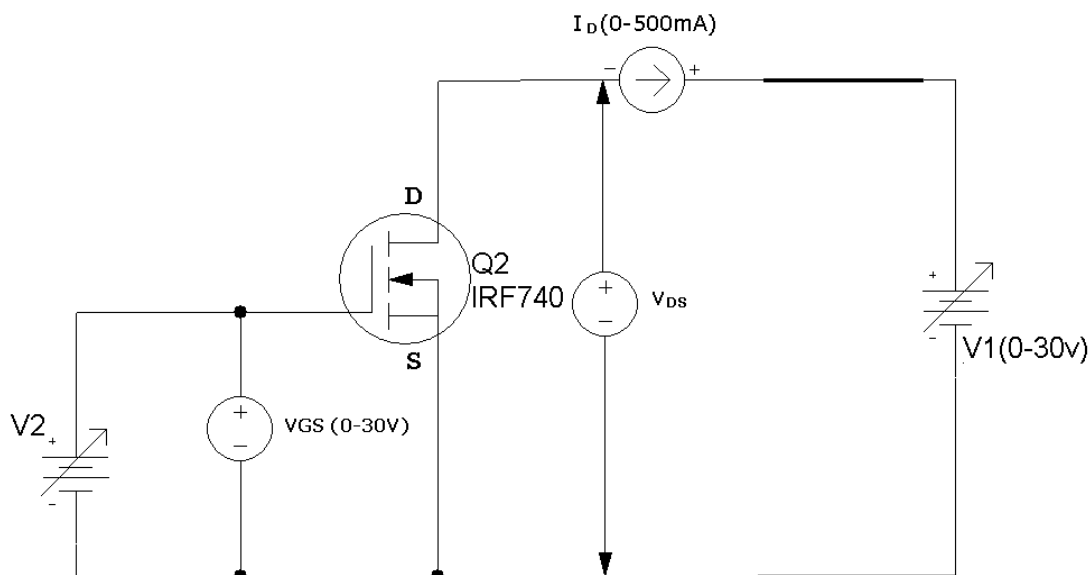

Ideal Graphs: -

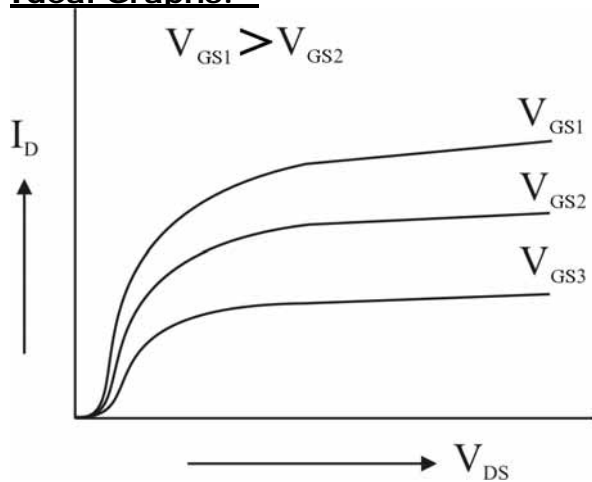

Drain Characteristics

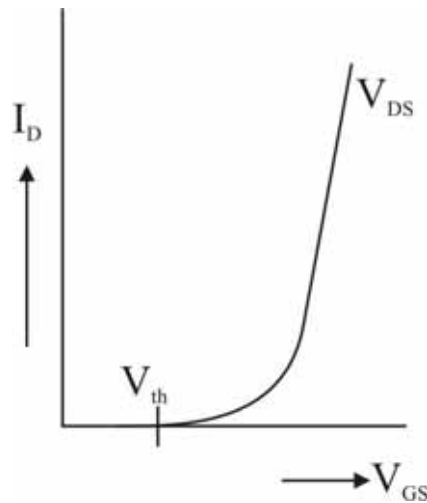

Transconductance Characteristics

Tabular Column

$V_{GS} =$	
$V_{DS}(V)$	$I_D(mA)$

$V_{GS} =$	
$V_{DS}(V)$	$I_D(mA)$

$V_{DS} =$	
$V_{GS}(V)$	$I_D(mA)$

$V_{DS} =$	
$V_{GS}(V)$	$I_D(mA)$

--	--	--	--	--	--	--	--

Experiment No: 3

DATE: __/__/____

MOSFET Characteristics

Aim: -

To study the characteristics of MOSFET

Apparatus required: -

MOSFET-IRF740, Power Supplies, Wattage Resistors, Ammeter, Voltmeter, etc.,

Procedure: -

Drain Characteristics

1. Connections are made as shown in the circuit diagram.
2. Adjust the value of V_{GS} slightly more than threshold voltage V_{th}
3. By varying V_1 , note down I_D & V_{DS} and are tabulated in the tabular column
4. Repeat the experiment for different values of V_{GS} and note down I_D v/s V_{DS}
5. Draw the graph of I_D v/s V_{DS} for different values of V_{GS} .


Transconductance Characteristics

1. Connections are made as shown in the circuit diagram.
2. Initially keep V_1 and V_2 zero.
3. Set $V_{DS} =$ say 0.6 V
4. Slowly vary V_2 (V_{GE}) with a step of 0.5 volts, note down corresponding I_D and V_{DS} readings for every 0.5v and are tabulated in the tabular column


5. Repeat the experiment for different values of V_{DS} & draw the graph of I_D v/s V_{GS}
6. Plot the graph of V_{GS} v/s I_D

.....
Signature of the staff-in-charge


Circuit Diagram: -

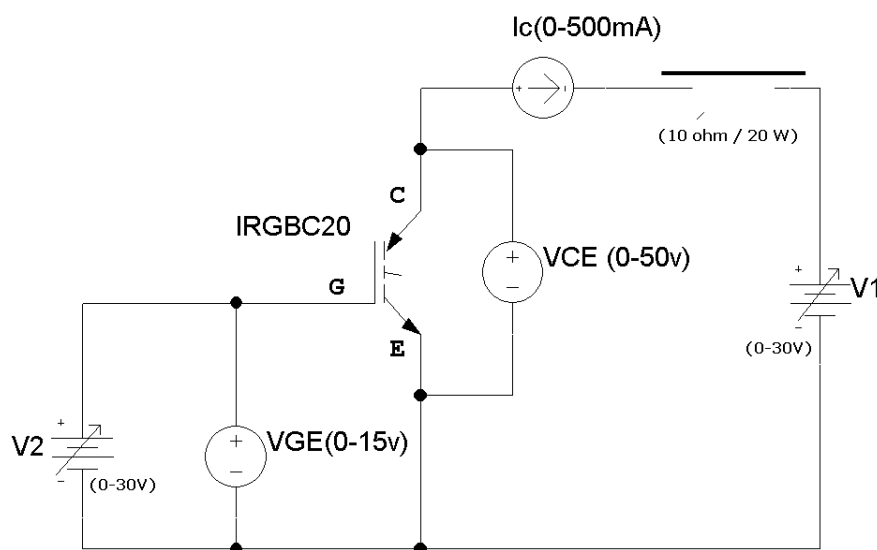

Ideal Graphs: -

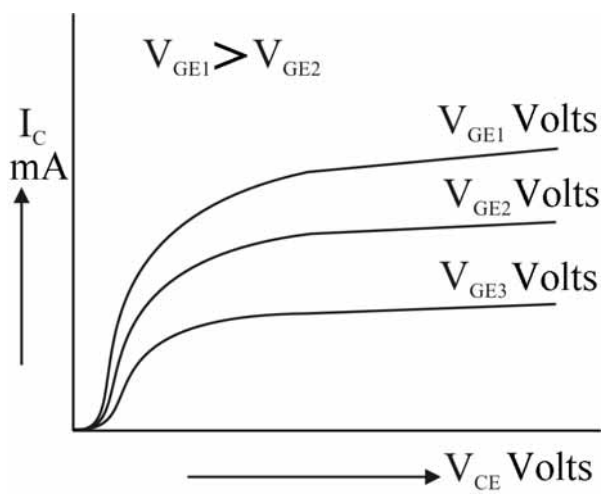

Collector Characteristics

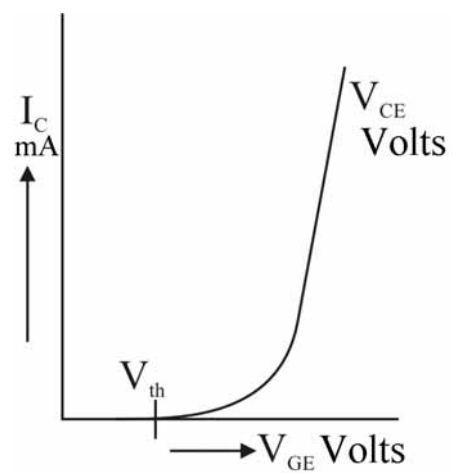

Transconductance Characteristics

Tabular Column

$V_{GE} =$		$V_{GE} =$		$V_{CE} =$		$V_{CE} =$	
$V_{CE}(V)$	$I_C(mA)$	$V_{CE}(V)$	$I_C(mA)$	$V_{GE}(V)$	$I_C(mA)$	$V_{GE}(V)$	$I_C(mA)$

Experiment No: 4

DATE: __/__/____

IGBT Characteristics

Aim: -

To study the characteristics of IGBT

Apparatus required: -

IGBT-IRGBC 20S, Power Supplies, Wattage Resistors, Ammeter, Voltmeter, etc.,

Procedure: -

Collector Characteristics

1. Connections are mode as shown in the circuit diagram.
2. Initially set V2 to $V_{GE1} = 5v$ (slightly more than threshold voltage)
3. Slowly vary V1 and note down I_C and V_{CE}
4. For particular value of V_{GE} there is pinch off voltage (V_p) between collector and emitter
5. Repeat the experiment for different values of V_{GE} and note down I_C v/s V_{CE}
6. Draw the graph of I_C v/s V_{CE} for different values of V_{GE} .

Transconductance Characteristics


1. Connections are mode as shown in the circuit diagram.
2. Initially keep V1 and V2 at zero.
3. Set $V_{CE1} =$ say 0.8 v

4. Slowly vary V_2 (V_{GE}) and note down I_C and V_{CE} readings for every 0.5v and enter tabular column
5. Repeat the experiment for different values of V_{CE} and draw the graph of I_C v/s V_{GE}


.....
Signature of the staff-in-charge

Half Wave Rectifier using RC Triggering

Circuit diagram:-


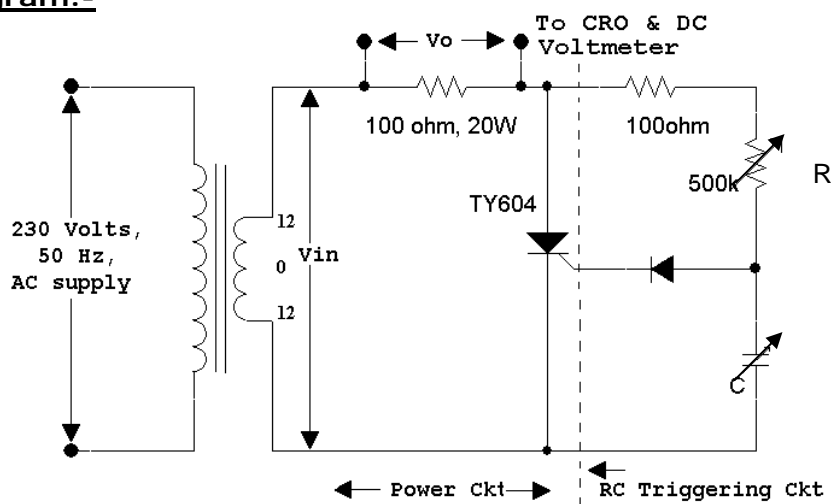


Waveforms:-

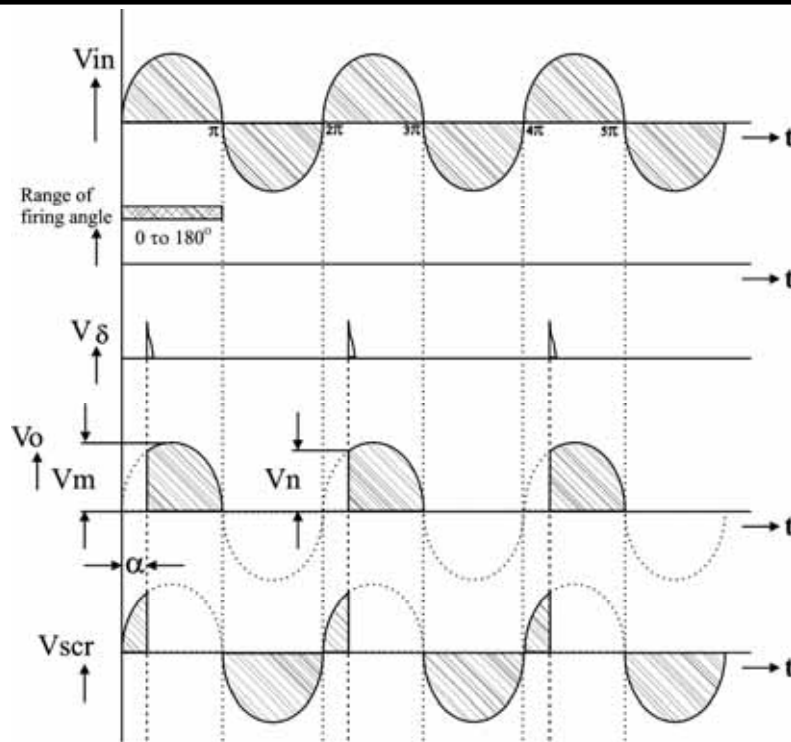

Where α = firing angle

Graph: -

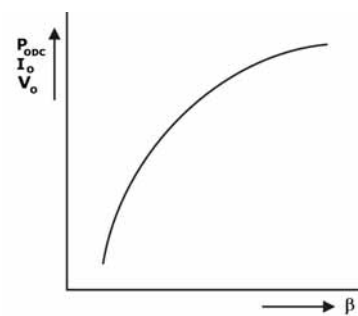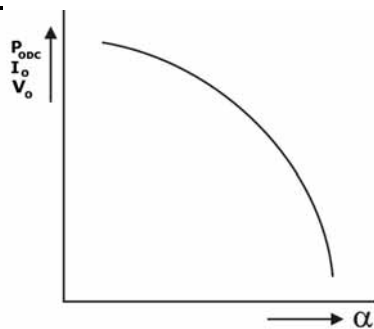

Experiment No: 5

DATE: __/__/__

RC Triggering Circuit – HWR & FWR

AIM: -

To study the performance & waveforms of HWR & FWR by using RC triggering Circuit

APPARATUS REQUIRED: -

Transformer, SCR – TY604, BY127, Resistor, Capacitor, Ammeter, Voltmeter

PROCEDURE: -

Half Wave Rectifier

1. Connections are made as shown in the circuit diagram
2. By varying a resistance R gradually in step by step, note down the corresponding values of V_n & V_m from CRO and V_{odc} from the DC voltmeter. The readings are tabulated in the tabular column.
3. If the firing angle ranges from 0 to 90° , then the firing angle α is calculated by using a formula $\alpha = \sin^{-1}\left(\frac{V_n}{V_m}\right)$ in degrees.
4. The conduction angle β is calculated by using a formula, $\beta = 180 - \alpha$.
5. The current and power is calculated by

$$I_{odc} = \frac{V_{odc}}{R} \text{ A \& } P_{odc} = \frac{V_{odc}^2}{R} \text{ Watts respectively.}$$

6. A graph of V_o v/s α , V_o v/s β , I_o v/s α , I_o v/s β , P_{odc} v/s α , P_{odc} v/s β are to be plotted.
7. Compare practical output voltage with theoretical output voltage,


$$V_{oth} = \frac{V_m}{2\pi}(1 + \cos\alpha) \text{ volts} \quad \text{where } V_m = \sqrt{2}V_{rms}$$

Full Wave Rectifier

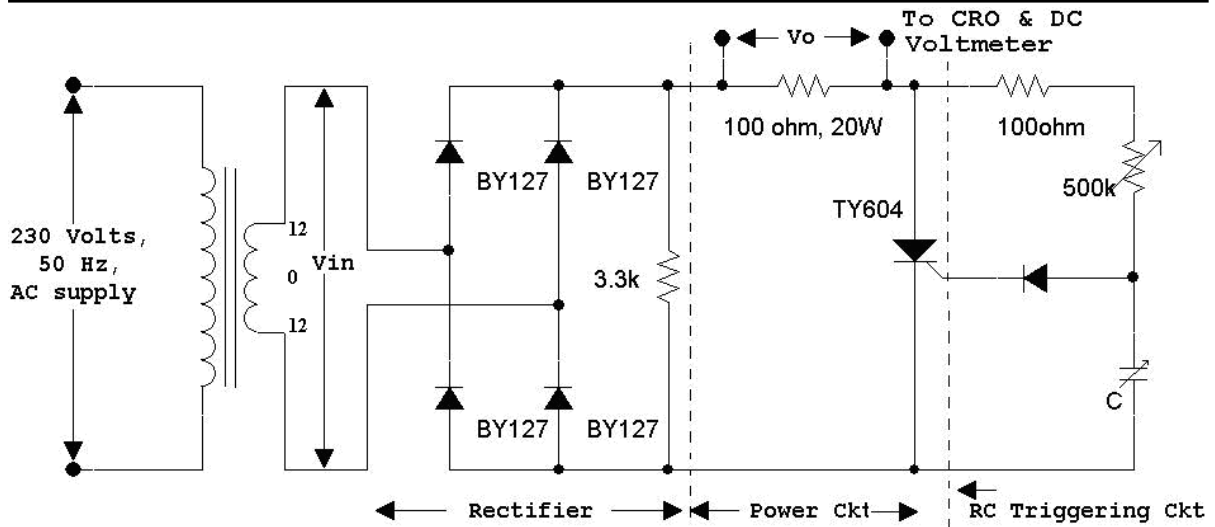
1. Repeat the above said procedure for full wave rectifier.

$$V_{oth} = \frac{V_m}{\pi}(1 + \cos\alpha) \text{ volts} \quad \text{where } V_m = \sqrt{2}V_{rms}$$

Full Wave Rectifier using RC Triggering**Circuit diagram:-**



Waveforms:-

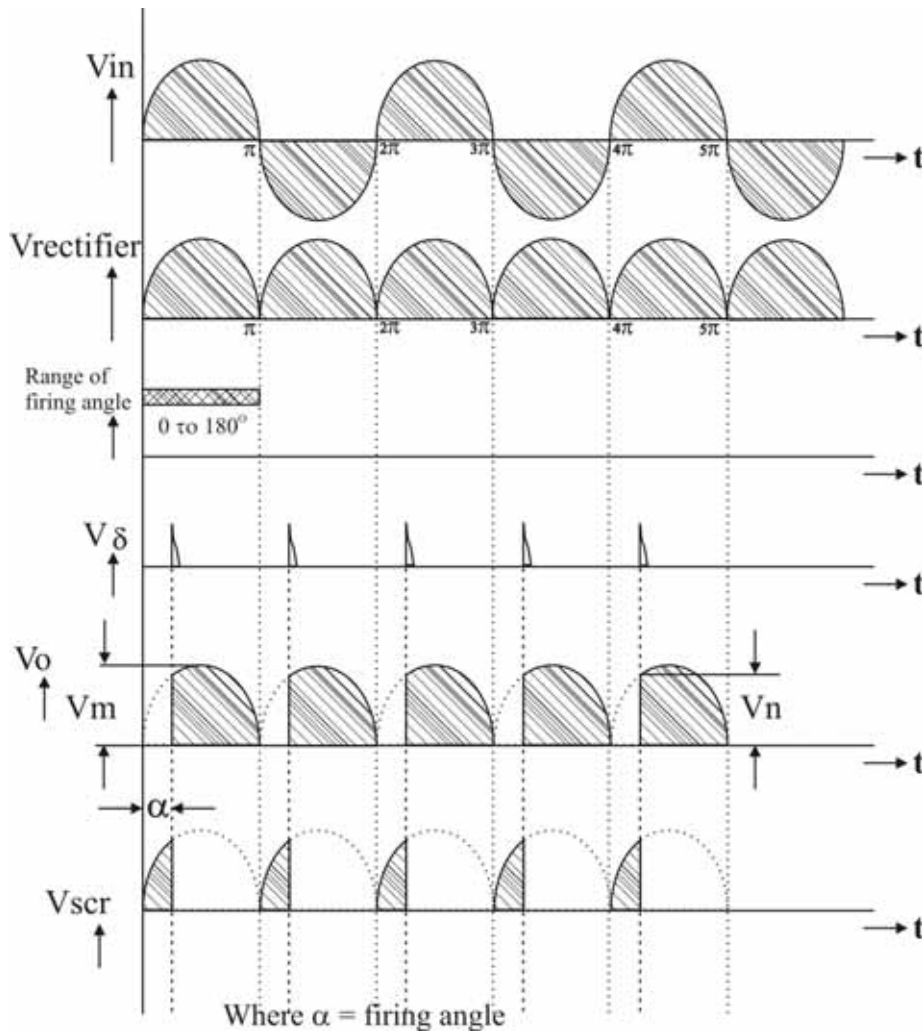

Tabular Columns:-

Half Wave Rectifier

Sl. No.	V_n	V_m	$(\alpha < 90^\circ)$	$(\alpha > 90^\circ)$	V_{dc}	V_{oth}
---------	-------	-------	-----------------------	-----------------------	----------	-----------

			$\alpha = \sin^{-1}\left(\frac{V_n}{V_m}\right)$	$\alpha = 180 - \sin^{-1}\left(\frac{V_n}{V_m}\right)$		

Full Wave Rectifier


Sl. No.	Vn	Vm	$(\alpha < 90^\circ)$ $\alpha = \sin^{-1}\left(\frac{V_n}{V_m}\right)$	$(\alpha > 90^\circ)$ $\alpha = 180 - \sin^{-1}\left(\frac{V_n}{V_m}\right)$	Vodc	V _{oth}

Viva Questions: -

1. Explain the working operation of the circuit?
2. What are the limitations of R triggering circuit?
3. What are the limitations of RC triggering circuit?
4. Mention different methods of triggering SCR?
5. Why gate triggering is preferred?


.....
Signature of the staff-in-charge

CIRCUIT DIAGRAM: -

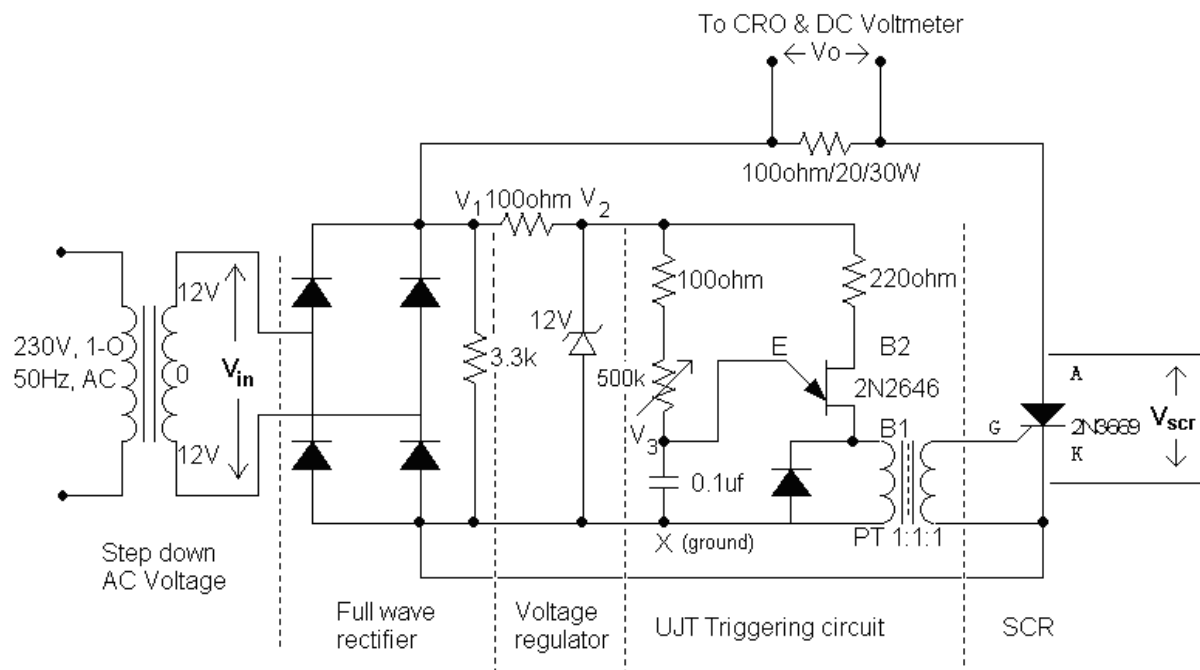


Base Diagrams: -

SCR-TY604

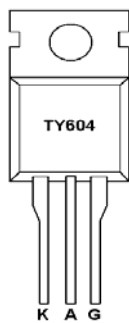


UJT: -2N2646

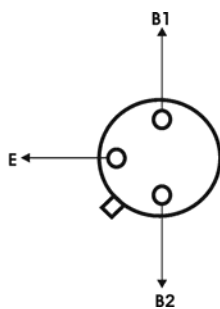

Diode: - BY127



Pulse Transformer

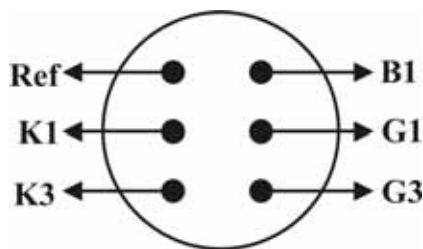

Experiment No: 6

DATE: __/__/____

U. J. T. Triggering of S. C. R

AIM: - To study the performance & waveforms of U.J.T triggering of S.C.R.

APPARATUS REQUIRED: -

SCR-TY604, Power supplies, Wattage Resistors, Ammeter, Voltmeter, UJT-2N2646, Pulse Transformer, etc.,

PROCEDURE: -

1. Connections are made as shown in the circuit diagram
2. By varying a resistance R gradually in step by step, note down the corresponding values of V_n & V_m from CRO and V_{Odc} from D.C voltmeter. The readings are tabulated in the tabular column.
3. If firing angle ranges from 0 to 90° , then firing angle can be calculated from

$$\alpha = \sin^{-1}\left(\frac{V_n}{V_m}\right) \quad \text{in degrees}$$

If firing angle ranges from 90° to 180° , then firing angle can be calculated by using a formula,

$$\alpha = 180 - \sin^{-1}\left(\frac{V_n}{V_m}\right) \quad \text{in degrees}$$

4. The conduction angle β can be calculated by using a formula,

$$\beta = 180 - \alpha$$


5. The current & power is calculated by

$$I_{dc} = \frac{V_{dc}}{R} \text{ Amps}$$

$$P_{dc} = \frac{V_{dc}^2}{R} \text{ Watts respectively}$$

6. A graph of V_{dc} v/s α , V_{dc} v/s β , I_{dc} v/s α , I_{dc} v/s β , P_{dc} v/s α , and P_{dc} v/s β are to be plotted on a graph sheet.

IDEAL WAVEFORMS: -

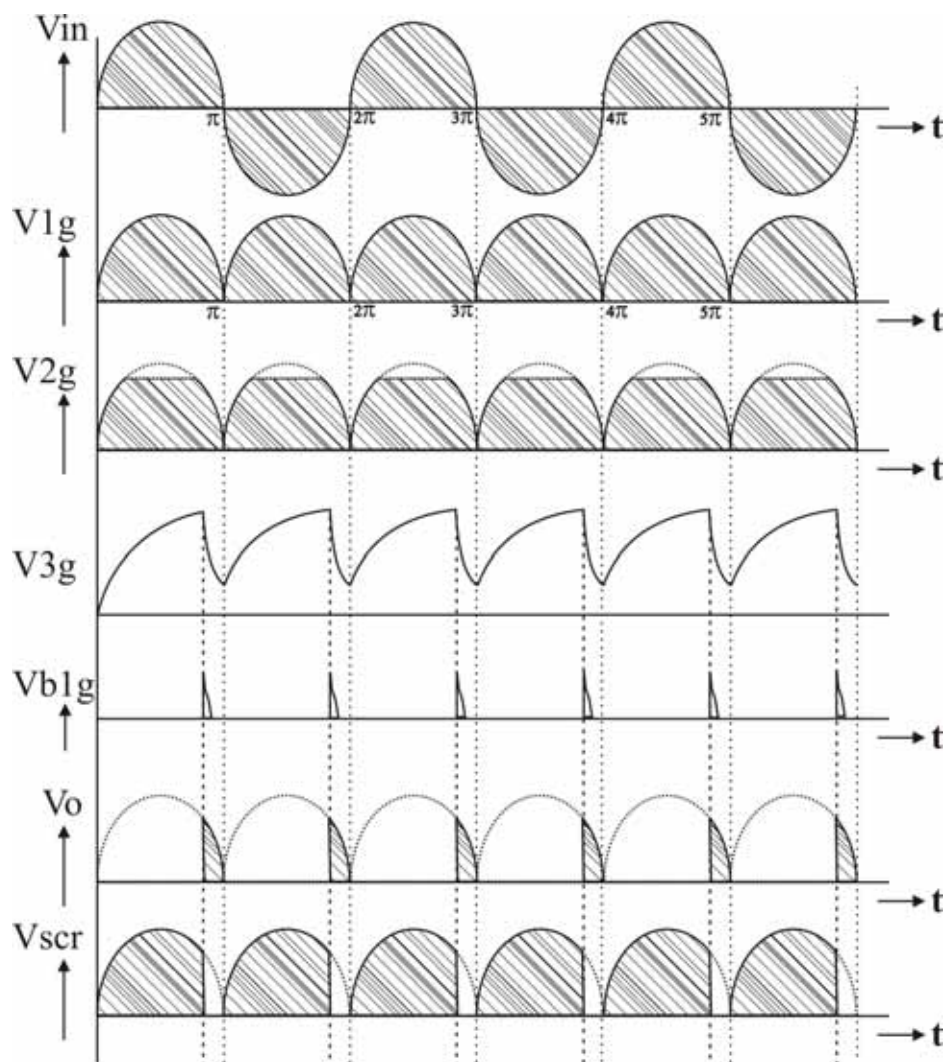

Tabular Column: -

Sl. No	FROM C.R.O								V _{DC} (V _{load}) volts	I _{dc} = V _{dc} /R A	P _{dc} = V _{dc} ² /R Watts	V _{oth}
	0 TO 90°				90° TO 180°							
	V _n volts	V _m volts	$\alpha = \sin^{-1}\left(\frac{V_n}{V_m}\right)^\circ$	$\beta = 180 - \alpha$	V _n volts	V _m volts	$\alpha = 180 - \sin^{-1}\left(\frac{V_n}{V_m}\right)^\circ$	$\beta = 180 - \alpha$				

7. For given frequency, the value of R can be calculated by using a formula,

$$T = 2.303RC \cdot \log_{10} \frac{1}{1 - \eta}$$

$$R = \frac{T}{2.303C \cdot \log_{10} \frac{1}{1 - \eta}} \Omega$$

When $C = 0.1 \text{ mF}$ & $N = \text{Intrinsic stand off ratio} = 0.67$

8. This value of R is set in the circuit, Step No S 3. 4. 5. & 6. are repeated and waveforms are observed at different points as shown.
9. Compare V_{oth} with $V_{\text{oPractical}}$ where $V_{\text{oth}} = \frac{V_m}{\pi} [1 + \cos \alpha]$

VIVA QUESTIONS: -

1. Explain the working operation of U.J.T. triggering circuit waveforms?
2. Why U.J.T. Triggering circuit is superior when compared to R & RC triggering circuit?
3. What is the use of pulse transformer?
4. Explain the design part of UJT?
5. Write equivalent circuit of UJT and show that $V_{\text{peak}} = V_{\text{emitter}} = V_{\gamma} + \eta V_{\text{BB}}$.
6. Why do we require turn-on circuits for thyristors?
7. Why do we require turn-off circuits for thyristors?
8. Comment on Forced & Natural Commutation techniques.

.....
Signature of the staff-in-charge

Designing of zener voltage regulator

$$\text{O/p of diode rectifier} = \frac{2v_m}{\pi} = \frac{2\sqrt{Z}}{\pi} V_{rms} = \frac{(2\sqrt{Z})24}{\pi} = 21.6 \text{ volts}$$

$$V_o = 21.6 \text{ volts}$$

$$\text{Take (assume) } V = 21.6 \pm 2$$

$$V_{\min} = 19.6 \text{ Volts and } V_{\max} = 23.6 \text{ volts}$$

$$V_z = 12 \text{ V, } I_L = 10 \text{ ma, } P_z = 400 \text{ mw} = 0.4 \text{ w}$$

$$V_{\min} = 19.6 \text{ volts, } V_{\max} = 23.6 \text{ volts,}$$

$$1) R_L = \frac{V_z}{I_L} = \frac{12}{0.01} = 1.2 \text{ K}\Omega$$

$$2) I_z = \frac{P_z}{V_z} = \frac{0.4}{12} = 33.33 \text{ mA}$$

$$I_s = I_z + I_L = (33.33 \times 10^{-3}) + (10 \times 10^{-3}) = 43.33 \times 10^{-3} \text{ A}$$

$$I_s = 43.33 \text{ ma}$$

$$\text{When } V = V_{\max} = 23.6 \text{ volts,}$$

$$R_s = \frac{V_{\max} - V_o}{I_s} = \frac{23.6 - 12}{0.04333} = 267.72 \Omega$$

$$\text{when } V = V_{\min} = 19.6 \text{ volts,}$$

$$R_s = \frac{V_{\min} - V_o}{I_s} = \frac{19.6 - 12}{0.04333} = 175.4 \Omega$$

$$\therefore 175.4 \Omega < R_s < 267.22 \Omega$$

$$\text{select } R_s = 300 \Omega$$

$$\text{wattage} = I_s^2 R_s = (43.33 \times 10^{-3})^2 \times 300 = 0.563 \text{ w}$$

$$\therefore \text{Select } R_s = 300 \Omega, 1 \text{ w}$$

Design of UJT

$$\text{We have } V_p = nV_{bb} + V_{thode} = (0.63)(12) + 0.7 = 8.26 \text{ volts}$$

Select $V_p = 8.26$ volts, $V_V = 1$ volt

$I_V = 10$ ma $I_p = 5$ micro amps

$$I. \text{ WKT, } R_{\max} = \frac{V_{bb} - V_p}{I_p} = \frac{12 - 8.26}{0.000005} = 748k\Omega$$

$$II. \quad R_{\min} = \frac{V_{bb} - V_V}{I_V} = \frac{12 - 1}{0.01} = 1.1k \Omega$$

$$\therefore R_{\min} < R < R_{\max}$$

$$\therefore R \text{ varies from } 1.1k\Omega \text{ to } 748K\Omega$$

$$III. \quad R_2 = 10000/n \quad V_B = 1000/(0.63)(12) = 1.32 K\Omega$$

Select $R_2 = 220\Omega$

Designing of fuming pulses

Let $F = 1$ kHz, $C = 0.01$ micro farads


$$T = 1/f = 1/1k = 1 \text{ ms}$$

$$\therefore \text{WKT, } T = 2.303 RC \log_{10} \frac{1}{1-n}$$


$$\therefore R = \frac{T}{2.303C \log_{10} \frac{1}{1-n}} = \frac{0.011}{2.303 \times 0.00000001 \times \log_{10} \frac{1}{1-0.63}} = 18.75k\Omega$$

$$R = 18.75 K \Omega$$


CIRCUIT DIAGRAM: -

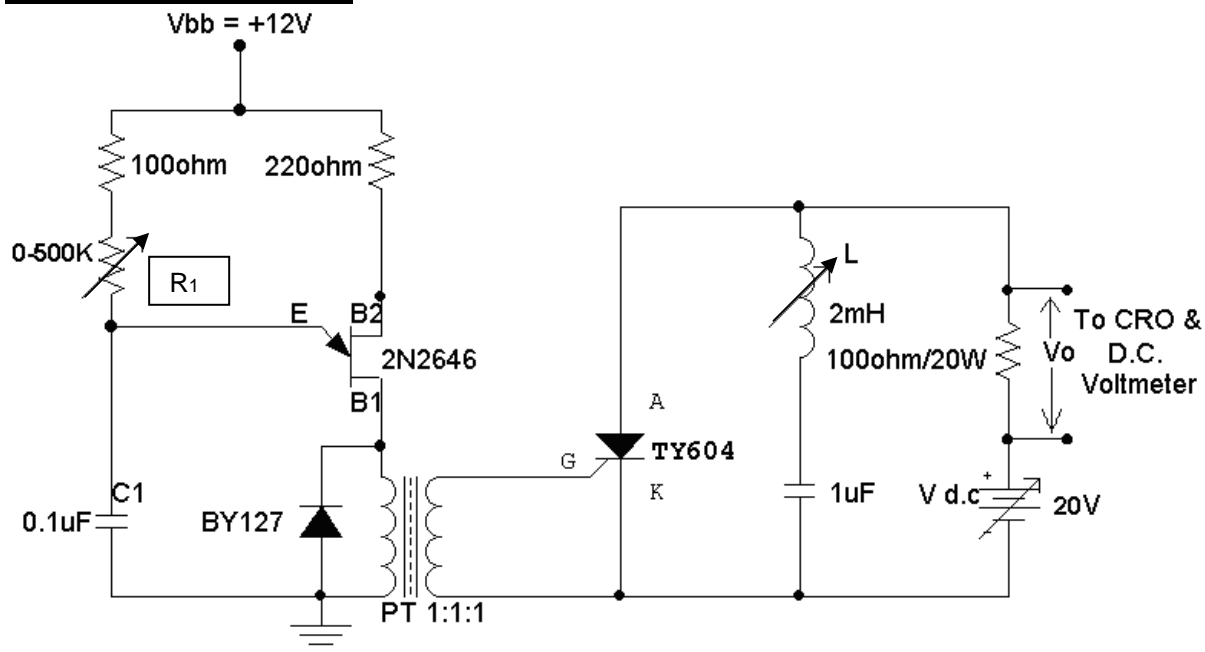

IDEAL WAVEFORMS: -

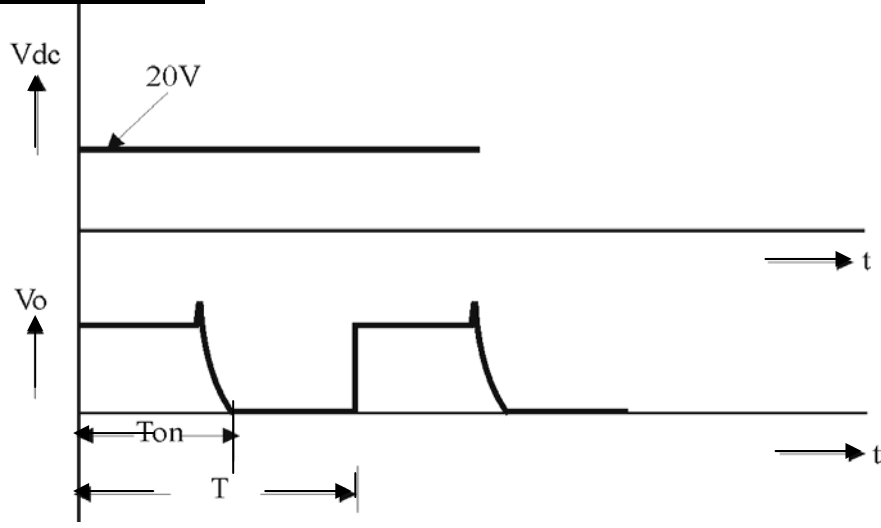

IDEAL GRAPH: -

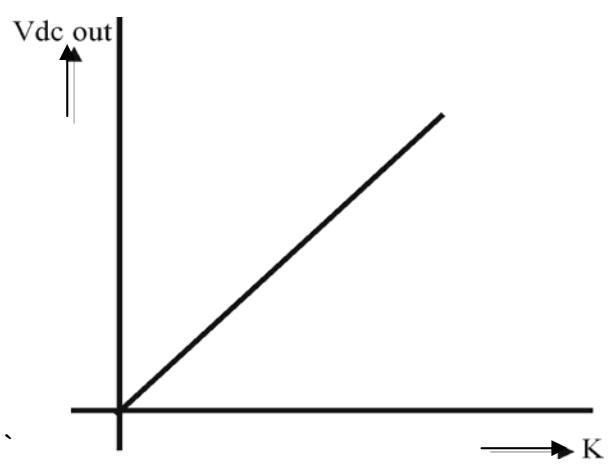

Experiment No: 7

DATE: __/__/____

Oscillation Chopper Circuit

AIM: -

- a) To convert variable D.C. voltage from a fixed D.C. input voltage.
- b) Plot a graph of V_{DCOUT} v/s Duty cycle (K)

APPARATUS REQUIRED: -

SCR-TY604, UJT-242646, Pulse Transformer, Power supplies, Wattage resistor, Ammeter, Voltmeter, etc.,

PROCEDURE: -

A. Variable Frequency Operation

1. Connections are made as shown in the circuit diagram.
2. The input D.C. voltage V_{DC} is set as convenient value say 20 V
3. Select proper values of L, for a given duty cycle C is calculated so that T_{ON} is constant.
4. By varying the variable resistor R_1 in step-by-step gradually, note down T_{ON} and T from CRO and V_O or V_{DCout} from D.C voltmeter.
5. The theoretical T_{on} and theoretical T are to be calculated by using a formula.

$$T_{ONth} = \pi\sqrt{LC} \qquad T_{th} = 2.303R_1C_1 \cdot \log_{10} \frac{1}{1-\eta}$$

Where η = Intrinsic stand off ratio = 0.67

6. The theoretical output voltage V_O or $V_{DCout-th}$ are to be calculated using formula,

$$V_{O_{th}} = V_{DCout_{th}} = \frac{T_{ONth}}{T_{th}} \times V_{DC} \qquad V_{O_{CRO}} = V_{DCout_{CRO}} = \frac{T_{ON_{CRO}}}{T_{CRO}} \times V_{DC}$$

7. All observations and calculations are tabulated in a tabular column.
8. Compare V_{oth} , V_{oCRO} & V_O d.c.voltmeter
9. Plot a graph of V_{odc} v/s duty cycle (k)

Turn-off Circuit Design: -

$$I_{peak} = V \sqrt{\frac{C}{L}}$$

Where $I_{peak} = 2I_o$

$$T_{off} = \frac{\pi\sqrt{LC}}{2}$$

T_{off} = Device turn off time

Tabular Column:- (A)

SI.No	V _{DC} Volts	R ₁ Ω	C ₁ μF	L H	C μF	T _{ONth} = π√LC	T _{th} = 2.303 RC.log ₁₀ $\frac{1}{1-\eta}$	T _{ONCRO}	T _{CRO}	V _{Oth} = $\frac{T_{ONth}}{T_{th}} \times V_{DC}$	V _{OCRO} = $\frac{T_{ONCRO}}{T_{CRO}} \times V_{DC}$	V _O D.C.Voltmeter

Tabular Column:- (B)

SI.No	V _{DC} Volts	R ₁ Ω	C ₁ μF	L H	C μF	T _{ONth} = π√LC	T _{th} = 2.303 RC.log ₁₀ $\frac{1}{1-\eta}$	Duty cycle K = $\frac{T_{ON}}{T}$	V _O = $\frac{T_{ON}}{T} \times V_{DC}$

Let $I_o = 100 \text{ mA}$ $I_{peak} = V \sqrt{\frac{C}{L}}$

$I_{peak} = 200 \text{ mA}$ $\sqrt{\frac{C}{L}} = \frac{I_{peak}}{V} = \frac{200 \times 10^{-3} \text{ C}}{20 \text{ V}} = \{1 \times 10^{-4}\}$

$V = 20 \text{ volts}$ $C = (1 \times 10^{-4})L \dots (1)$

$T_{off} = 50 \mu s$

$T_{off} = \frac{\pi \sqrt{LC}}{2}$ $\therefore LC = \left(\frac{2T_{off}}{\pi}\right)^2 = \left(\frac{2 \times 50 \times 10^{-6}}{\pi}\right)^2 = 1 \times 10^{-9}$

solving 1 & 2 we get

We know that $C = (1 \times 10^{-4})L$ $\therefore L = \sqrt{\frac{1 \times 10^{-9}}{1 \times 10^{-4}}} = 3.16 \text{ mH}$

$\therefore C = (1 \times 10^{-4})L = (1 \times 10^{-4})(3.16 \times 10^{-3}) = 3.16 \times 10^{-7} = 0.316 \mu F$

For successful commutation, turn off time of the circuit should be greater than turn off time of the device.

Select $C = 1\mu\text{F}$ and $L = 3\text{mH}$.

$$\therefore \text{Circuit turn off time} = \frac{\pi\sqrt{LC}}{2} = \frac{\pi}{2}\sqrt{1 \times 10^{-6} \times 3 \times 10^{-3}} = 86\mu\text{s}$$

\therefore Circuit turn off time > turn off time of the device

$$\text{i.e., } 86\mu\text{s} > 50\mu\text{s}$$

B. Fixed Frequency Operation

1. The value of variable resistor R1 is set at some value is T is fixed
2. By varying L at different values, calculate the duty cycle $K = \frac{T_{ON}}{T}$ Where

$$T_{ON_{th}} = \pi\sqrt{LC} \quad \text{and} \quad T = 2.303RC \cdot \log_{10} \frac{1}{1-\eta}$$

3. Note down the corresponding o/p D.C. Voltage V_{DCOUT} from D.C. Voltmeter

$$V_{O_{th}} = V_{DCout_{th}} = \frac{T_{ON_{th}}}{T_{th}} \times V_{DC} \qquad V_{O_{CRO}} = V_{DCout_{CRO}} = \frac{T_{ON_{CRO}}}{T_{CRO}} \times V_{DC}$$

4. Plot a graph of V_{DCOUT} v/s Duty cycle (K)

VIVA QUESTIONS: -

1. Explain the working operation of oscillation chopper circuit?
2. What type of commutation circuit is employed in this circuit? Why it is necessary?
3. Why UJT triggering is preferred?
4. Explain the working function of each component?
5. Explain the different types of commutation circuit


Note: - for $T = 10 \text{ ms}$, $K = 30\%$ means $T_{ON} = 0.3 T$

$T = T_{ON} + T_{OFF}$ $K = 50\%$ means $T_{ON} = 0.5 T$


.....
Signature of the staff-in-charge

CIRCUIT DIAGRAM: -

Half Wave Rectifier

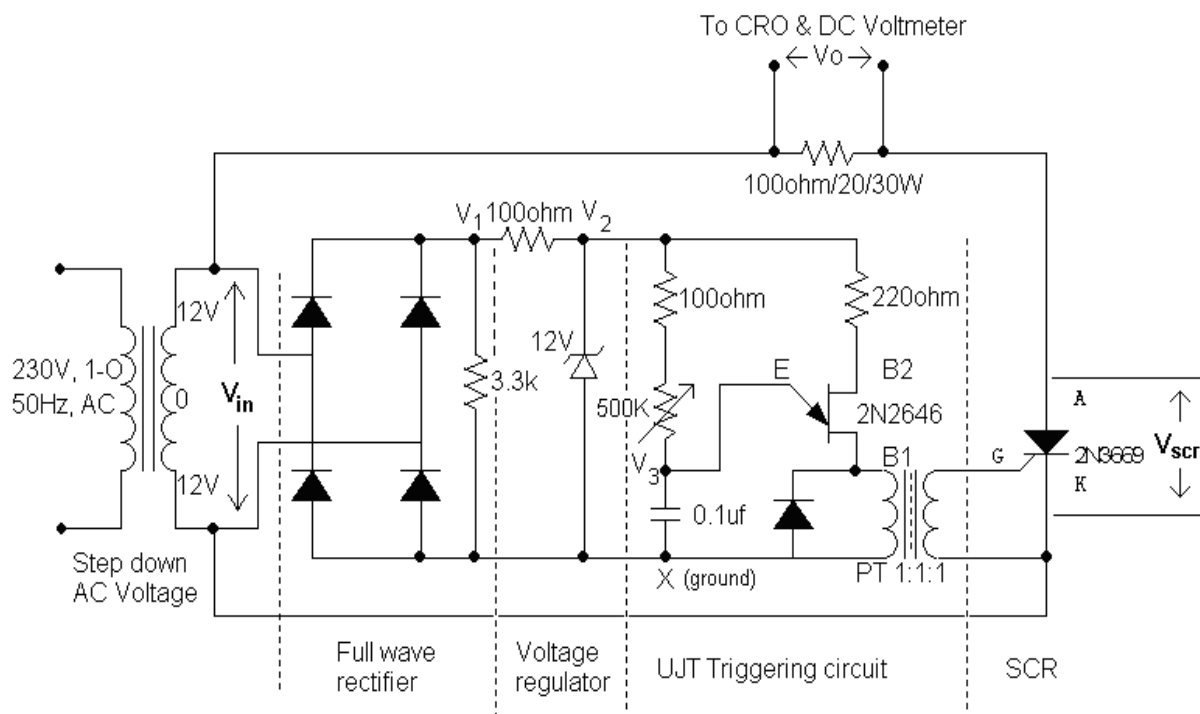

Full Wave Rectifier

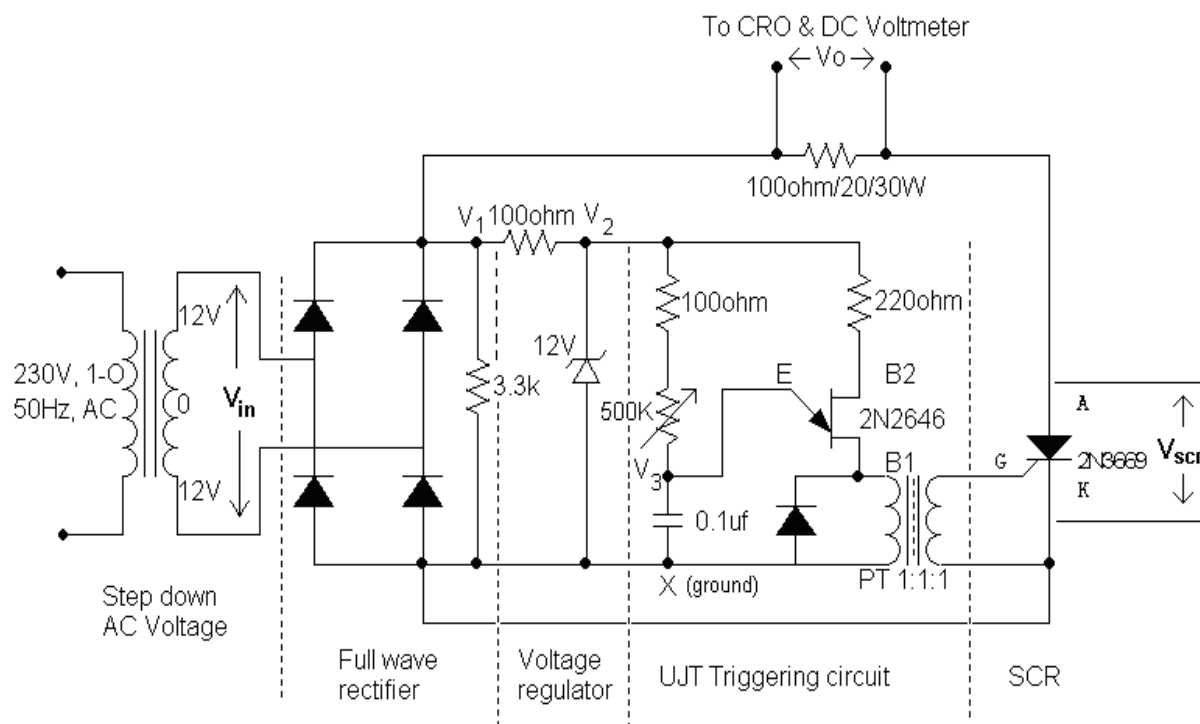

Experiment No: 8

DATE: __/__/____

U. J. T. Triggering for HWR & FWR

AIM: - To study the performance & waveforms of U.J.T triggering of S.C.R.

APPARATUS REQUIRED: -

SCR-TY604, Power supplies, Wattage Resistors, Ammeter, Voltmeter, UJT-2N2646, Pulse Transformer, etc.,

PROCEDURE: -

1. Connections are made as shown in the circuit diagram
2. By varying a resistance R gradually in step by step, note down the corresponding values of V_n & V_m from CRO and V_{dc} from D.C voltmeter. The readings are tabulated in the tabular column.
3. If firing angle ranges from 0 to 90° , then firing angle can be calculated from

$$\alpha = \sin^{-1}\left(\frac{V_n}{V_m}\right) \quad \text{in degrees. If firing angle ranges from } 90^\circ \text{ to } 180^\circ,$$

then firing angle can be calculated by using a formula,


$$\alpha = 180 - \sin^{-1}\left(\frac{V_n}{V_m}\right) \quad \text{in degrees}$$

4. The conduction angle β can be calculated by using a formula, $\beta = 180 - \alpha$
5. The current & power is calculated by

$$I_{dc} = \frac{V_{dc}}{R} \text{ Amps} \quad P_{dc} = \frac{V_{dc}^2}{R} \text{ Watts respectively}$$

6. A graph of V_{dc} v/s α , V_{dc} v/s β , I_{dc} v/s α , I_{dc} v/s β , P_{dc} v/s α , and P_{dc} v/s β are to be plotted on a graph sheet.

IDEAL WAVEFORMS: -

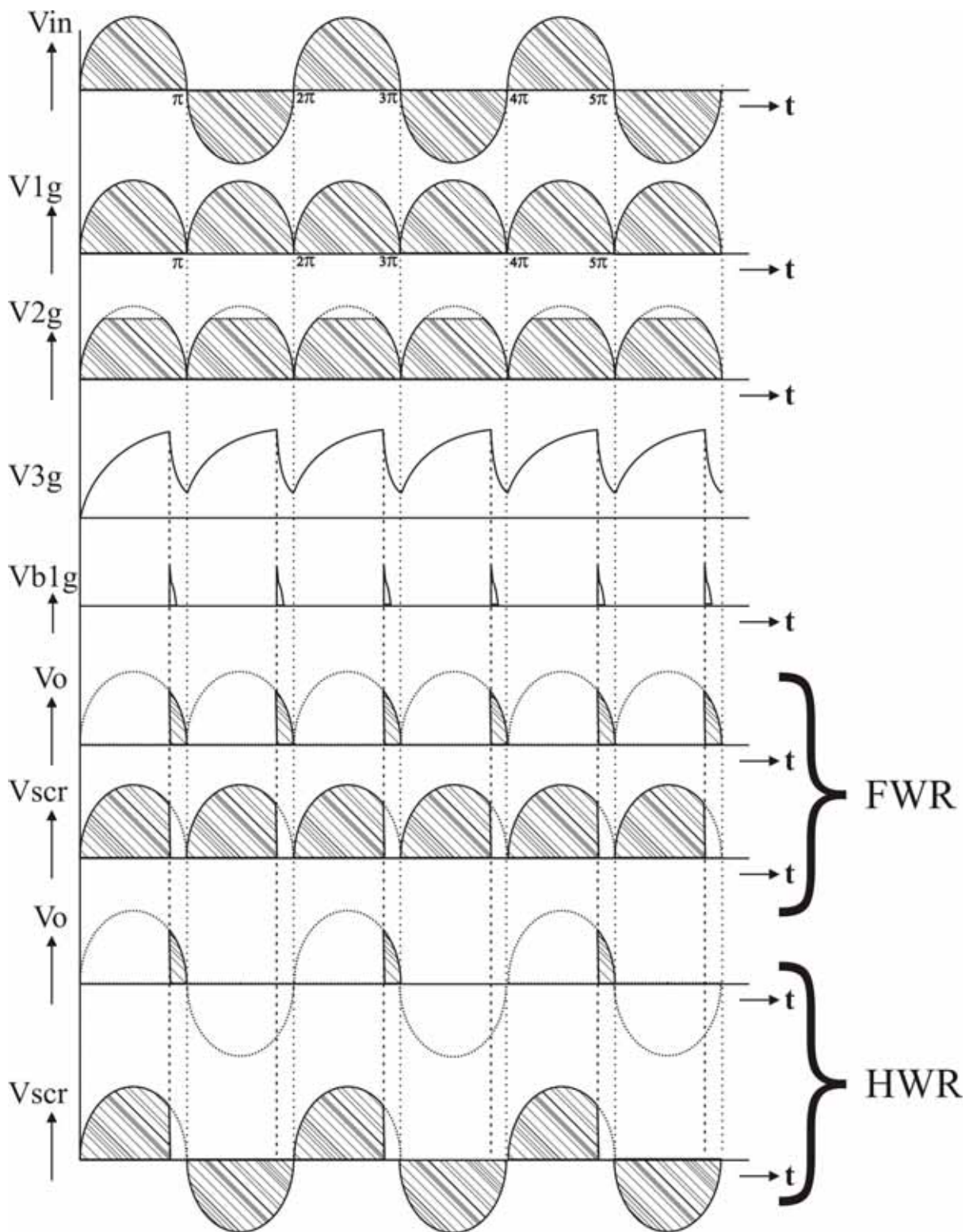

7. For given frequency, the value of R can be calculated by using a formula,

$$T = 2.303RC. \log_{10} \frac{1}{1 - \eta}$$

$$R = \frac{T}{2.303C. \log_{10} \frac{1}{1 - \eta}} \Omega$$

When $C = 0.1 \text{ mF}$ & $N = \text{Intrinsic stand off ratio} = 0.67$


8. This value of R is set in the circuit, Step No S 3. 4. 5. & 6. are repeated and waveforms are observed at different points as shown.

9. The practical o/p voltage ($V_{o \text{ meter}}$) is compared with V_{oth}

$$\text{For HWR } V_{oth} = \frac{V_m}{2\pi} (1 + \cos\alpha) \text{ volts where } V_m = \sqrt{2} V_{irms}$$

$$\text{For FWR } V_{oth} = \frac{V_m}{\pi} (1 + \cos\alpha) \text{ volts}$$

Graph: -

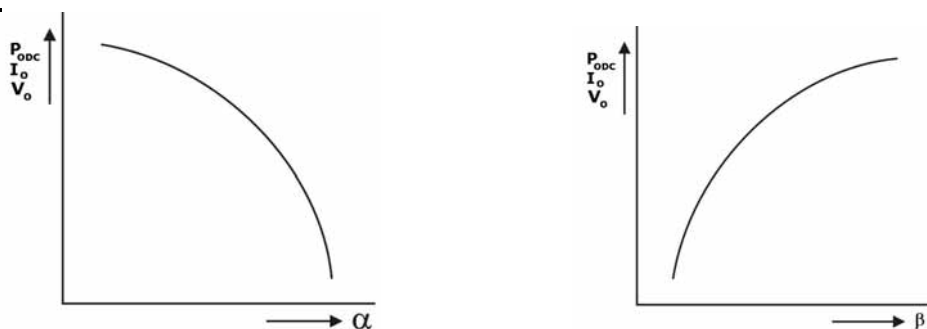

Tabular Column:- a) Half wave switches

Sl.No	FROM C.R.O								V _{DC} (V _{load}) volts	I _{dc} = V _{dc} /R A	P _{dc} = V _{dc} ² /R Watts
	0 TO 90°				90° TO 180°						
	V _n volts	V _m volts	$\alpha = \sin^{-1}\left(\frac{V_n}{V_m}\right)^\circ$	$\beta = 180 - \alpha$	V _n volts	V _m volts	$\alpha = 180 - \sin^{-1}\left(\frac{V_n}{V_m}\right)^\circ$	$\beta = 180 - \alpha$			

Full wave switches



Sl. No	FROM C.R.O								V _{DC} (V _{load}) volts	I _{dc} = V _{dc} /R A	P _{dc} = V _{dc} ² /R Watts
	0 TO 90°				90° TO 180°						
	V _n volts	V _m volts	$\alpha = \sin^{-1}\left(\frac{V_n}{V_m}\right)^\circ$	$\beta = 180 - \alpha$	V _n volts	V _m volts	$\alpha = 180 - \sin^{-1}\left(\frac{V_n}{V_m}\right)^\circ$	$\beta = 180 - \alpha$			

Base Diagrams: -

SCR-TY604

UJT: -2N2646


Diode: - BY127

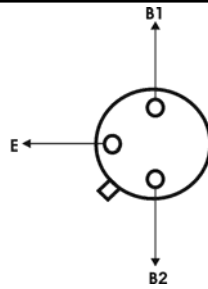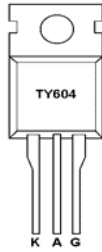**VIVA QUESTIONS: -**


1. Explain the working operation of U.J.T. triggering circuit waveforms?
2. Why U.J.T. Triggering circuit is superior when compared to R & RC triggering circuit?
3. What is the use of pulse transformer?
4. Explain the design part of UJT?
5. Write equivalent circuit of UJT and show that $V_{\text{peak}} = V_{\text{emitter}} = V_{\gamma} + \eta V_{\text{BB}}$.
6. Why do we require turn-on circuits for thyristors?
7. Why do we require turn-off circuits for thyristors?
8. Comment on Forced & Natural Commutation techniques.

.....
Signature of the staff-in-charge

Circuit Diagram:

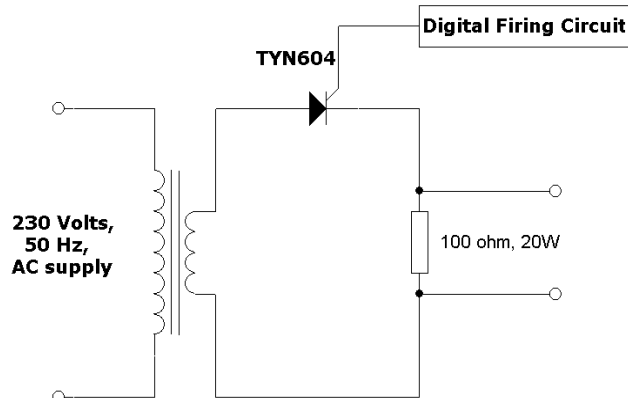


Wave form:-

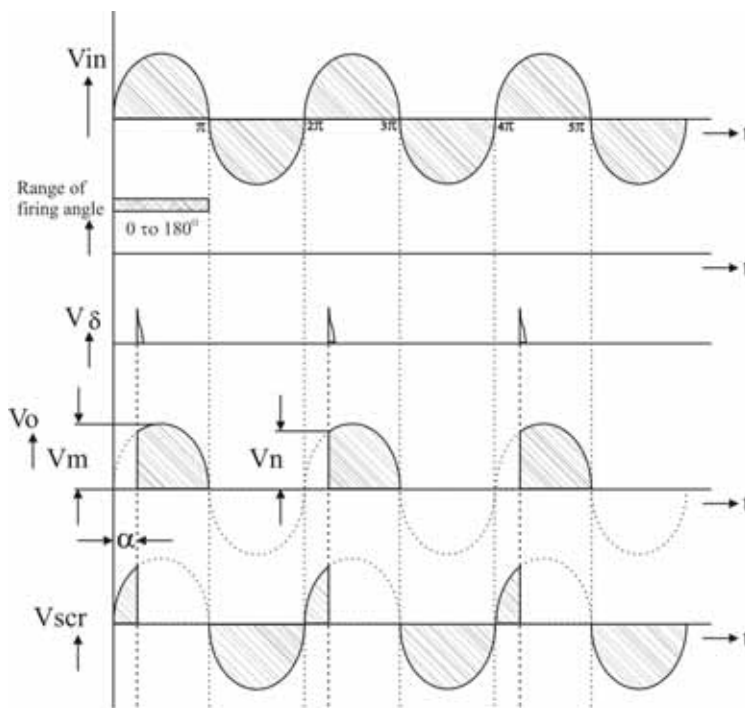

Where α = firing angle

Graph:-

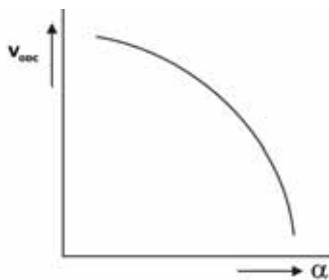

Tabular Column:-

Sl. No.	Firing Angle (α)	V_{ODC}

Experiment No: 9

DATE: __/__/____

Digital Firing Circuit

Aim: -

To demonstrate digital firing circuit to turn on SCR (HW) for R-Load and to plot V_{ODC} v/s α .

Apparatus required: -

Digital Firing Module, SCR-TYN604, Resistor, etc.,

Procedure: -

1. Connections are made as shown in the circuit diagram.
2. Firing angle α is varied in steps gradually, note down corresponding values of V_{ODC} (DC voltmeter reading) and tabulate.
3. A graph of α v/s V_{ODC} is plotted.


Result: -

Digital Firing Circuit to turn on SCR is studied and a graph of α v/s V_{ODC} is plotted.


.....
Signature of the staff with date


CIRCUIT DIAGRAM: -

(a) ILLUMINATION CONTROL

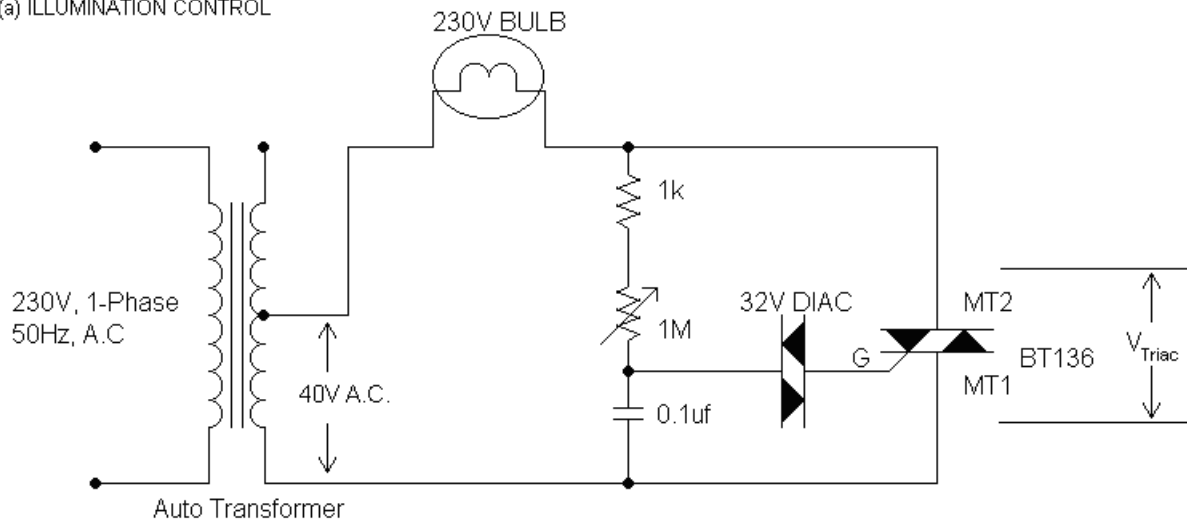

(b)

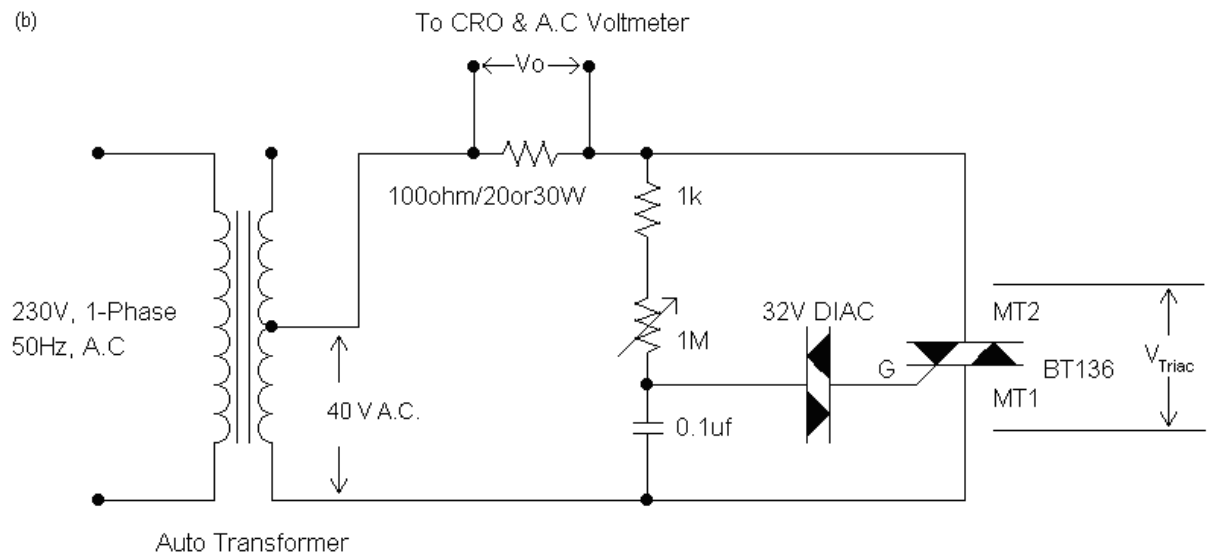

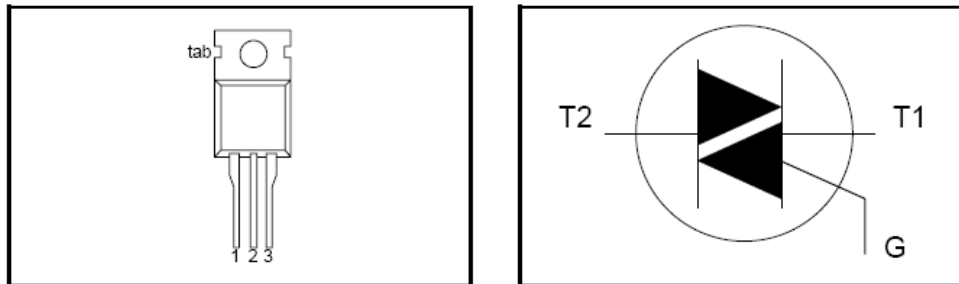

PIN	DESCRIPTION
1	main terminal 1
2	main terminal 2
3	gate
tab	main terminal 2

Experiment No: 10

DATE: __/__/____

AC Voltage Control by using TRIAC-DIAC Combination

AIM: -

1. To study the AC voltage control by using TRIAC-DIAC combination

APPARATUS REQUIRED: -

TRIAC, DIAC, supply voltage, wattage resistors, Ammeter, Voltmeter, etc.,

PROCEDURE: -**A.**

1. Connections are made as shown in the circuit diagram (a)
2. By varying the variable resistance R_1 in step by step, observe the variation of intensity of light.

B.

1. Connections are made as shown in the circuit diagram (b)
2. By varying the resistance R , in step-by-step note down the corresponding values of V_n & V_m from C.R.O. and $V_{a.c}$ from A.C. voltmeter the readings are tabulated in the tabular column

3. If delay angle ranges from 0 To 90°, then firing angle can be calculated

from $\alpha = \text{Sin}^{-1}\left(\frac{V_n}{V_m}\right)$ in degrees. If firing angle ranges from 90° To 180° then

can be calculated by using a formula, $\alpha = 180 - \text{Sin}^{-1}\left(\frac{V_n}{V_m}\right)$ in degrees

4. The conduction angle B can be calculated by using a formula,

$$\beta = 180 - \alpha \text{ in degrees}$$

5. The current can be calculated by $I_{ac} = \frac{V_{ac}}{R}$


6. A graph of I_{ac} v/s α , V_{ac} or load voltage v/s α are to be plotted

7. Compare V_{oeter} with V_{oth} where $V_{oth} = V_{in\text{rms}} \sqrt{\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right)}$

Tabular Column: -

Sl. No	FROM C.R.O								V_{DC} (V_{load}) volts	$I_{dc} =$ $\frac{V_{dc}}{R}$ A	V_{in} Volt s	Speed rpm
	0 TO 90°				90° TO 180°							
	V_n volts	V_m volts	$\alpha = \text{Sin}^{-1}\left(\frac{V_n}{V_m}\right)^\circ$	$\beta = 180 - \alpha$	V_n volts	V_m volts	$L = 180 - \text{Sin}^{-1}\left(\frac{V_n}{V_m}\right)^\circ$	$\beta = 180 - \alpha$				

Waveforms:-

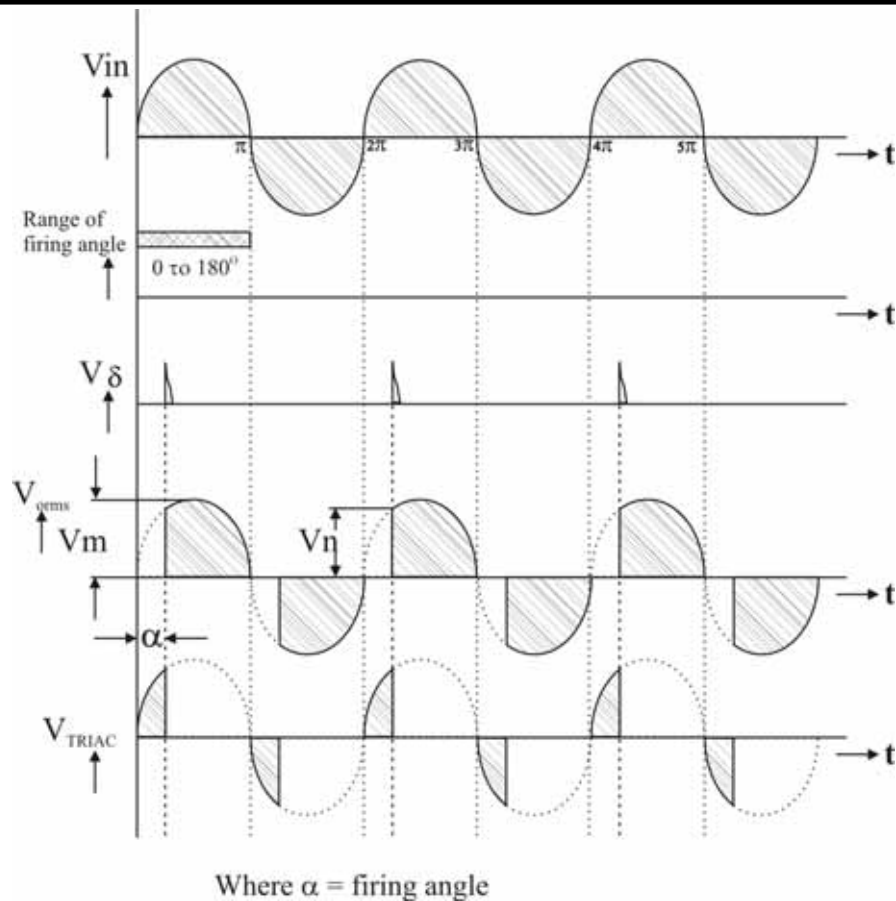


VIVA QUESTIONS: -



1. Explain the features of TRIAC?
2. Explain the working operation of illumination control & various voltage output waveforms by using TRIAC?
3. Compare S.C.R, DIAC & TRIAC?
4. What is universal motor?
5. Comment on the different graphs of this experiment?
6. Mention the applications of TRIAC?

.....

Signature of the staff with date

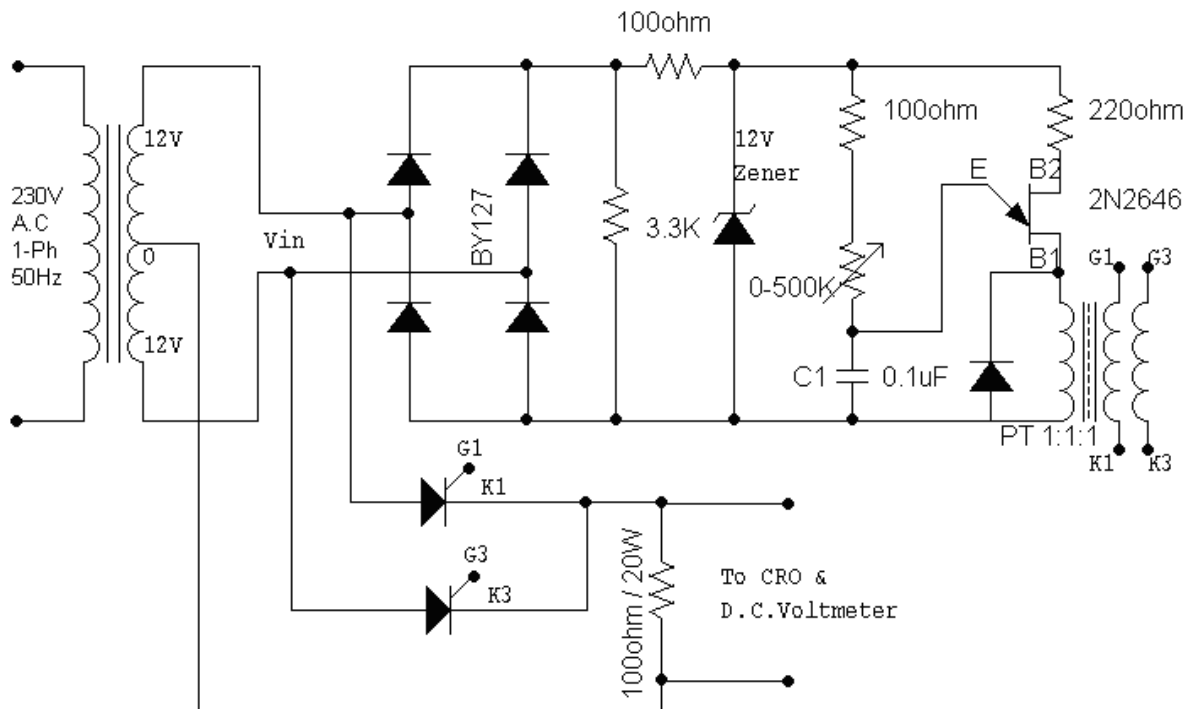CIRCUIT DIAGRAM: - (a) With R-load (Resistive load)



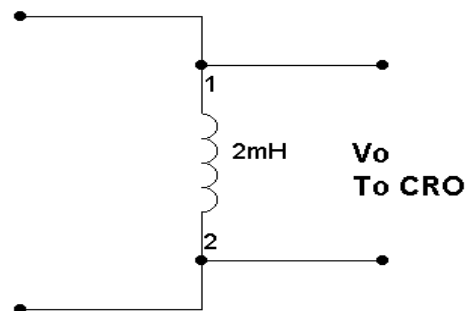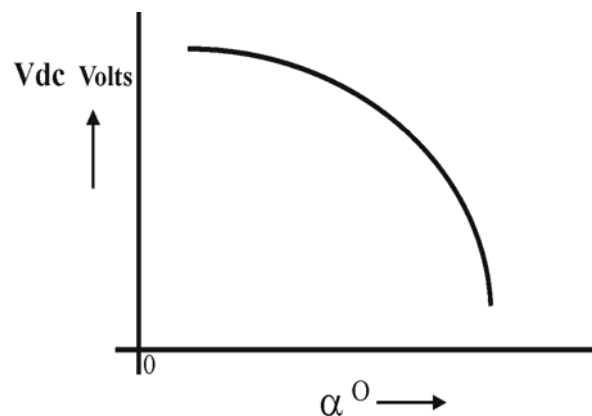(b) WITH L LOAD (Inductive load)**GRAPHS: -**

Experiment No: 11

DATE: __/__/____

Single Phase Full Wave Controlled Rectifier**AIM: -**

1. To study the performance and waveforms of full wave controlled rectifier with Resistance load and Inductive load
2. Plot a graph of V_o v/s for R-load

APPARATUS REQUIRED: -

SCR-TY604, Power supplies, Wattage Resistors, Ammeter, Voltmeter, UJT-2N2646, BY127, Inductor, Pulse Transformer, etc.,

PROCEDURE: -

1. Connections are made as shown in the circuit diagram for resistive load.

2. By varying a variable resistor R in step-by-step gradually. Note down corresponding values of V_N , V_M , from C.R.O. and V_O or V_{load} or V_{DC} from d.c.voltmeter for resistive load, the readings are tabulated in the tabular column

3. If α varies from 0 To 90° , then firing angle can be calculated from

$$\alpha = \text{Sin}^{-1}\left(\frac{V_n}{V_m}\right) \quad \text{in degrees}$$

If α varies from 90° to 180° then α is

$$\alpha = 180 - \text{Sin}^{-1}\left(\frac{V_n}{V_m}\right) \quad \text{in degrees}$$


4. The conduction angle $\beta = 180 - \alpha$ in degrees is calculated for each value of α

5. Plot a graph of V_{DC} or V_{load} or V_O v/s firing angle α

6. Observe the waveforms at different points as shown and waveforms are traced on tracing paper.

7. For Inductance load repeat step no. s 1,2,3,4,5 & 6.

WAVEFORMS: -

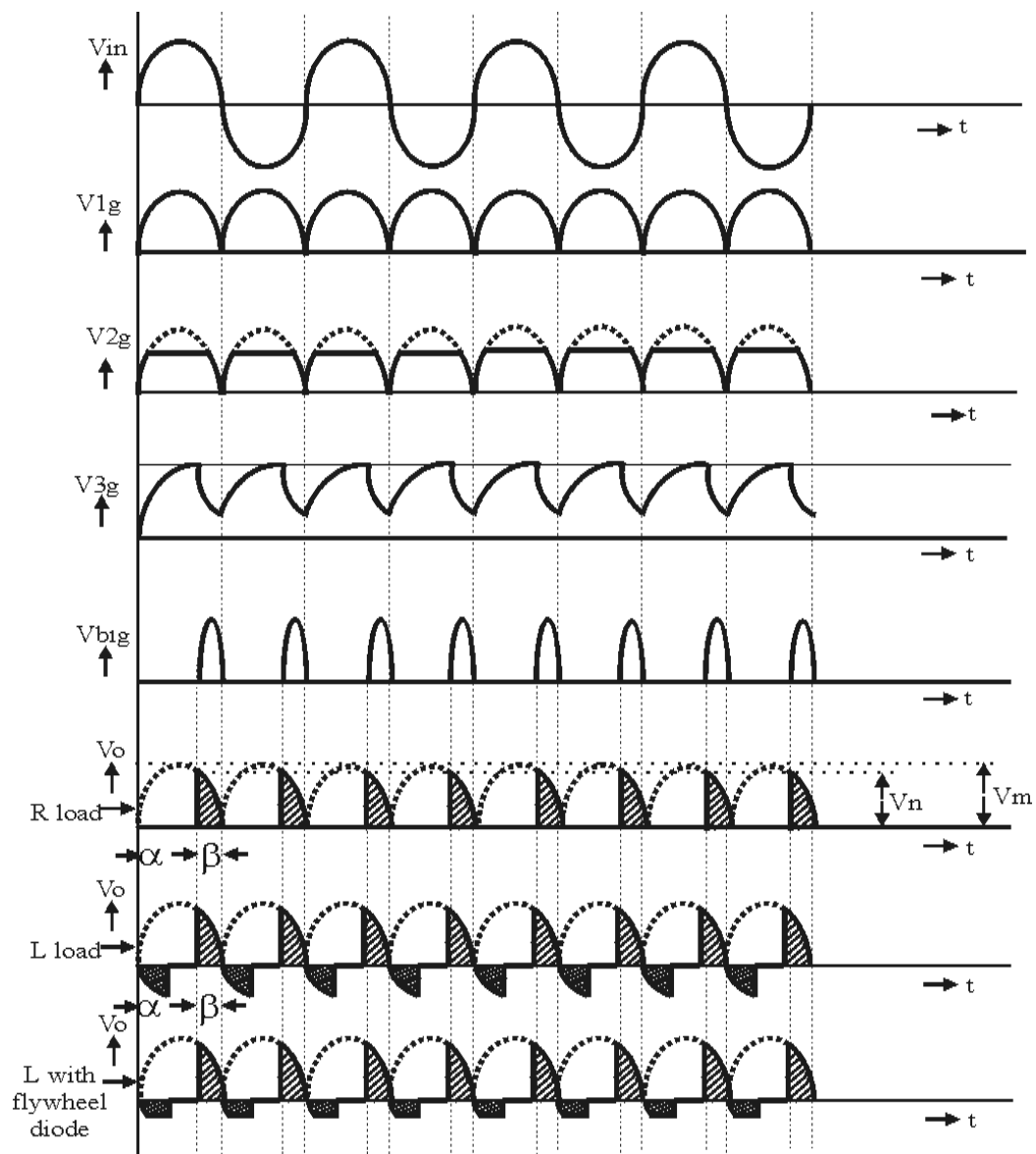

TABULAR COLUMN: -

(a) For Resistive load

Sl.No	From CRO								Vo or VDC or VLOAD volts
	0° – 90°				90° – 180°				
	V _N volts	V _M volts	$\alpha = \sin^{-1}\left(\frac{V_n}{V_m}\right)^\circ$	$\beta = 180 - \alpha$	V _N volts	V _M volts	$\alpha = 180 - \sin^{-1}\left(\frac{V_n}{V_m}\right)^\circ$	$\beta = 180 - \alpha$	

b) Inductive load:

Sl.No	From CRO								V _O or V _{DC} or V _{LOAD} volts
	0° – 90°				90° – 180°				
	V _N volts	V _M volts	$\alpha = \sin^{-1}\left(\frac{V_n}{V_m}\right)^{\circ}$	$\beta = 180 - \alpha$	V _N volts	V _M volts	$\alpha = 180 - \sin^{-1}\left(\frac{V_n}{V_m}\right)^{\circ}$	$\beta = 180 - \alpha$	

C) R L with Free wheeling diode


Sl.No	From CRO								V _O or V _{DC} or V _{LOAD} volts
	0° – 90°				90° – 180°				
	V _N volts	V _M volts	$\alpha = \sin^{-1}\left(\frac{V_n}{V_m}\right)^{\circ}$	$\beta = 180 - \alpha$	V _N volts	V _M volts	$\alpha = 180 - \sin^{-1}\left(\frac{V_n}{V_m}\right)^{\circ}$	$\beta = 180 - \alpha$	

VIVA QUESTIONS: -


1. Explain the performance and working operation of single-phase full controlled rectifier with relevant waveforms for Resistive load, Inductive load.
2. Compare H.C.R with F.C.R
3. In cyclo-converter, why H.C.R with Inductive load cannot be implemented

.....
Signature of the staff with date


Impulse Commutated Chopper:

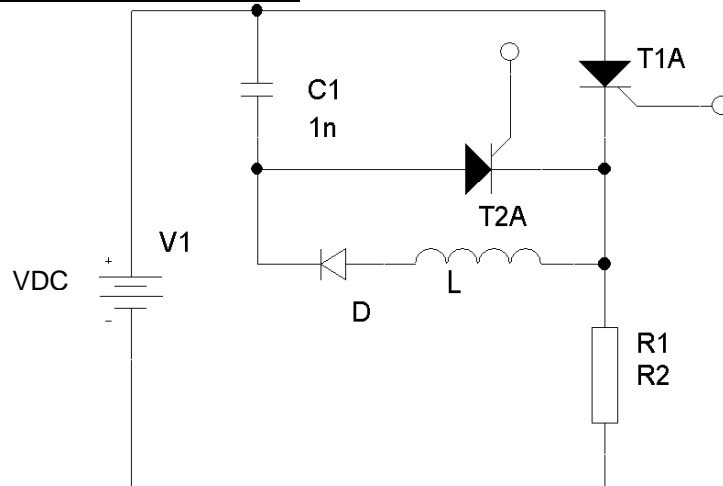

Wave forms:-

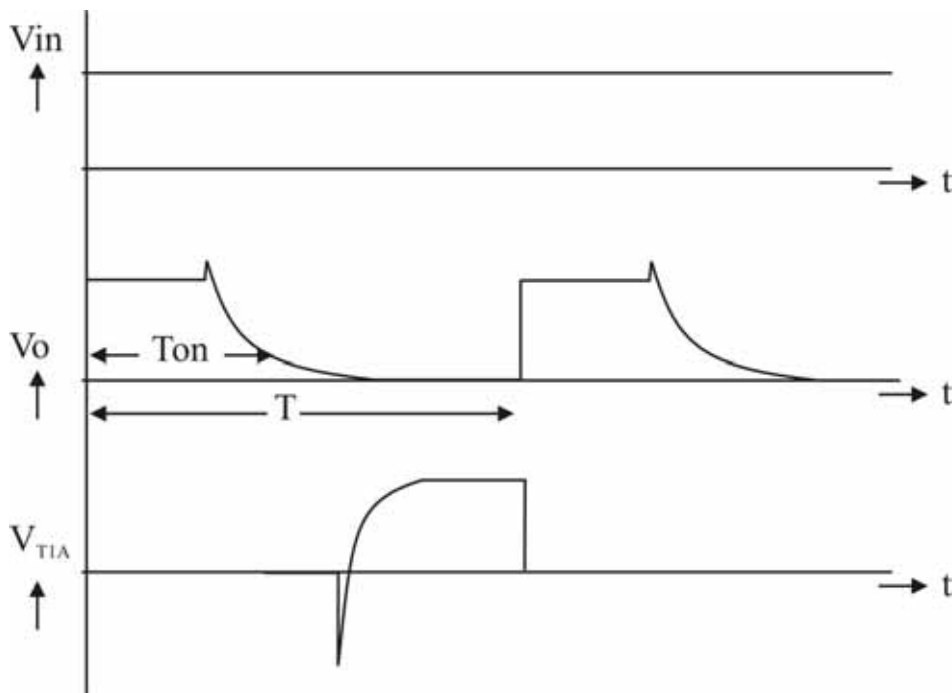

Graph:-

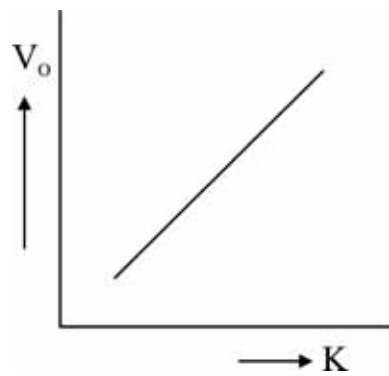

Experiment No: 12

DATE: __/__/____

Impulse Commutated Chopper

Aim: -

To study the performance of voltage commutated chopper for constant frequency operations.

Apparatus required: -

Module, SCRs, Diodes, inductor, capacitors, etc.,

Procedure: -


1. Connections are made as shown in the circuit diagram.
2. Input DC voltage is set to convenient value (10v to 25v).
3. By varying duty cycle knob of triggering circuit module step by step gradually note down corresponding T_{on} and T from the CRO and V_o from DC voltmeter and tabulate.
4. Duty cycle 'K' is calculated by using $K = \frac{T_{on}}{T}$.
5. A graph of V_o v/s K is plotted.
6. Observe load and device voltage waveforms.

Tabular Column: -


Sl. No.	Duty Cycle knobs	$T_{ON\ cro}$	T_{CRO}	$K = \frac{T_{ON}}{T}$	V_o (V)

.....
Signature of the staff with date

Single Phase Induction Motor:

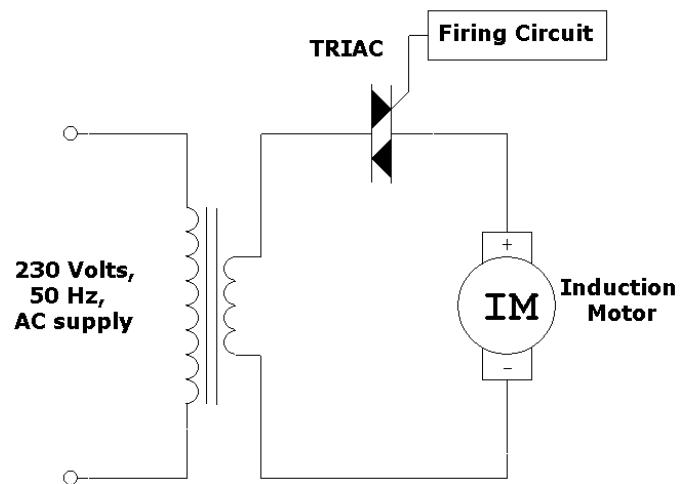

Graph:-

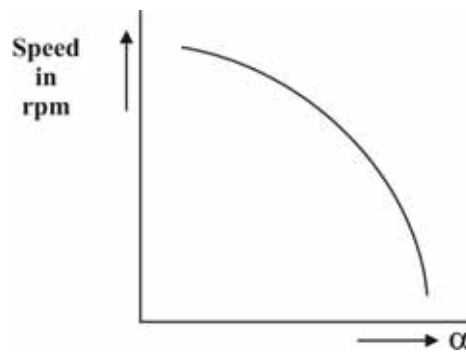

Tabular Column:-

Sl. No.	Firing Angle (α)	Speed in RPM

Experiment No: 13

DATE: __/__/____

Speed Control of Single Phase Induction Motor

Aim: -

To study speed control of Induction motor and plot speed v/s α .

Apparatus required: -

Module, TRIAC, Induction Motor, etc.,

Procedure: -


1. Connections are made as shown in the circuit diagram.
2. Firing angle α is varied in steps gradually, note down corresponding speed of the induction motor using Tachometer and tabulate.
3. A graph of α v/s speed is plotted.

Result: -


Speed control of Induction Motor is studied and a graph of α v/s speed is plotted.

.....
Signature of the staff with date


Universal Motor (DC):

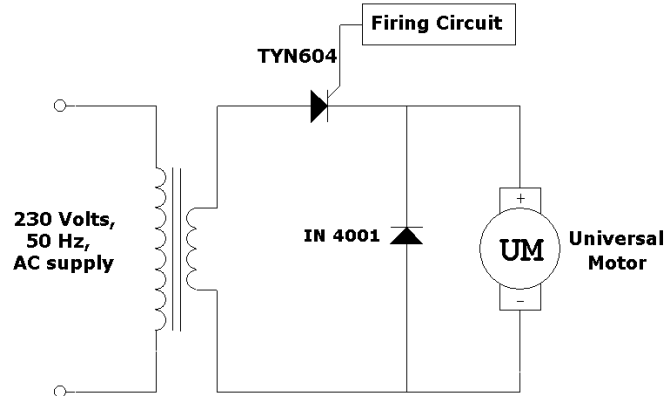

Universal Motor (AC):

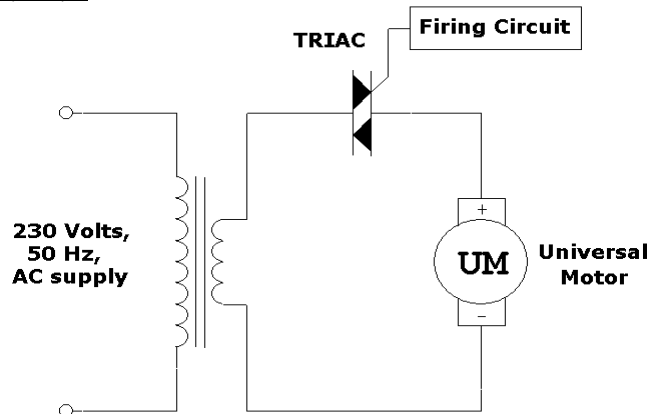

Graph:-

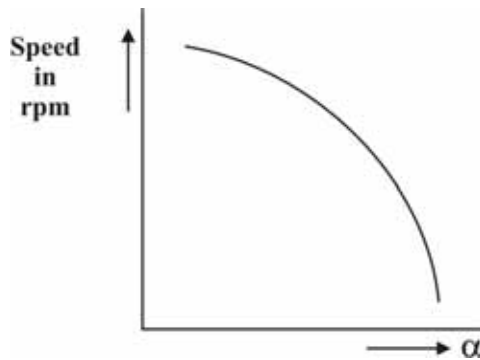

Tabular Column:-

AC Motor			DC Motor		
Sl. No.	Firing Angle (α)	Speed in RPM	Sl. No.	Firing Angle (α)	Speed in RPM

Experiment No: 14

DATE: __/__/____

Speed Control of Universal Motor

Aim: -

To study speed control of Universal motor and plot speed v/s α .

Apparatus required: -

Module, TRIAC-BT136, Universal Motor, Diode-IN4001 etc.,

Procedure: -

DC Motor: -

1. Connections are made as shown in the circuit diagram.
2. Firing angle α is varied in steps gradually, note down corresponding speed of the induction motor using Tachometer and tabulate.
3. A graph of α v/s speed is plotted.

AC Motor: -


1. Above procedure is repeated for AC Motor.

Result: -


Speed control of Universal Motor is studied and a graph of α v/s speed is plotted.

.....
Signature of the staff with date

Series Inverter

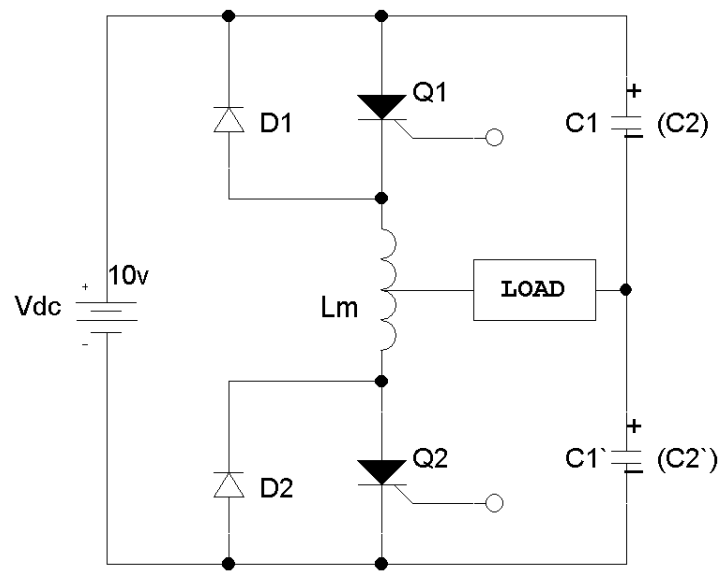

Wave forms:-

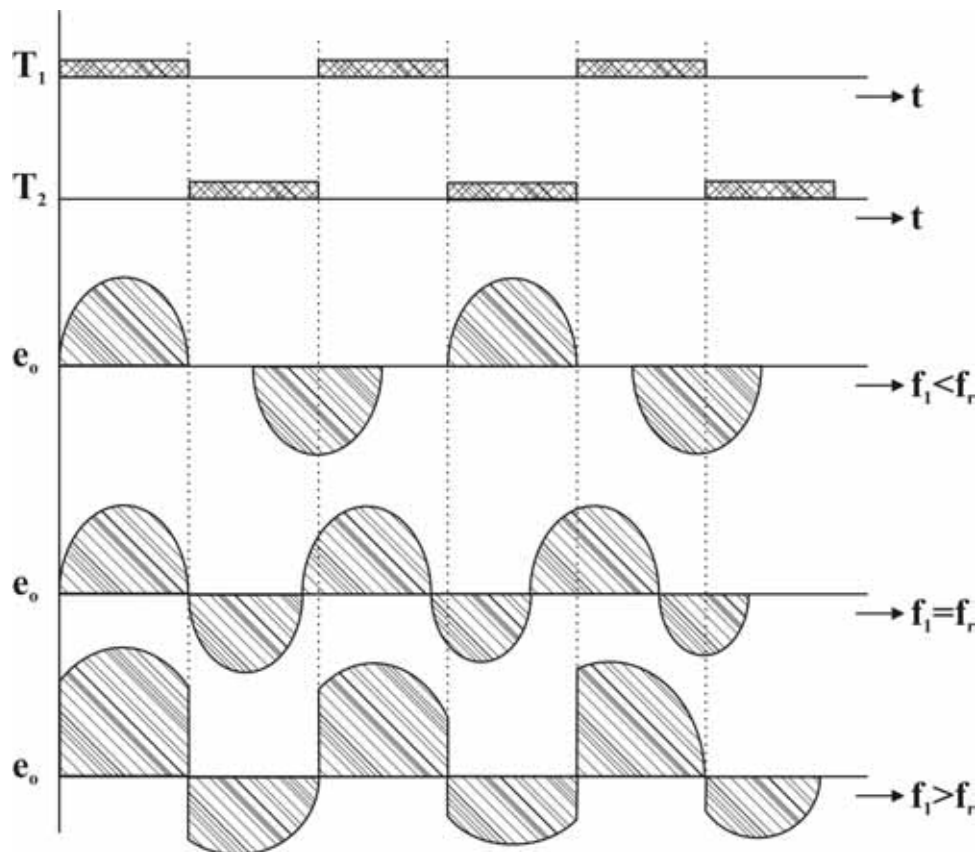

Experiment No: 15

DATE: __/__/____

Series Inverter

Aim: -

To obtain variable AC from DC ripple input.

Apparatus required: -

Module, SCRs, Diodes, inductor, capacitors, etc.,

Procedure: -

1. To begin with switch on the power supply to the firing circuit check that trigger pulses by varying the frequency.
2. Connections are made as shown in the circuit diagram.
3. Now connect trigger outputs from the firing circuits to gate and cathode of SCRs T1 & T2.
4. Connect DC input from a 30v/2A regulated power supply and switch on the input DC supply.
5. Now apply trigger pulses to SCRs and observe voltage waveform across the load.
6. Measure V_{orms} & frequency of o/p voltage waveform.



Resonance frequency: -

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

$$L=10\text{mH}, C = 10\mu\text{F}, R = 20\Omega, f_{\text{th}}=477\text{Hz}, f_p=250\text{KHz}$$

.....
Signature of the staff with date

Parallel Inverter

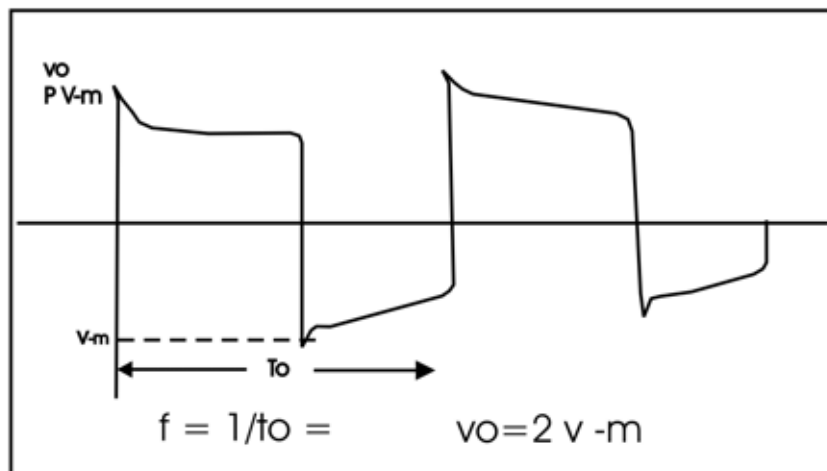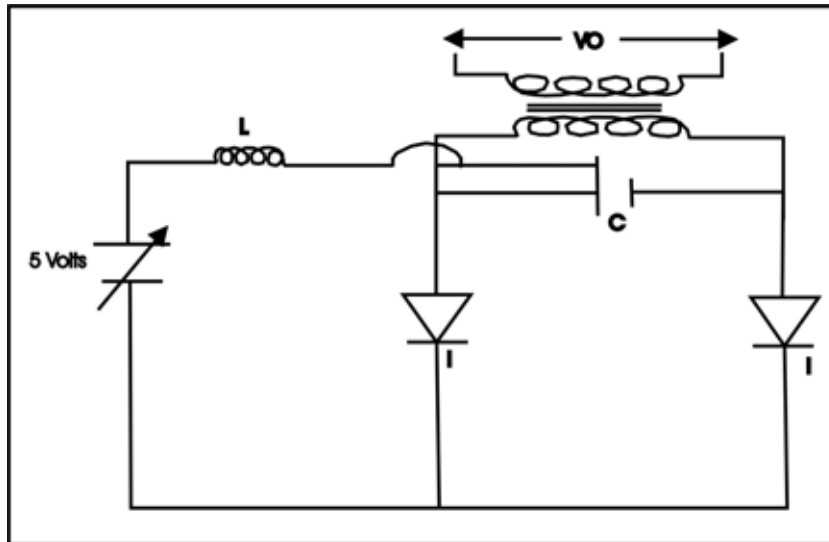

.....
Signature of the staff with date

Parallel Inverter

Aim :-

To obtain variable AC from DC ripple input.

Apparatus required:-

Module, SCRs, Diodes, inductor, capacitors, etc.,

Procedure:-

1. Connecting are made as shown in the circuit diagram
2. Select values of $c =$, $L =$
3. Set input voltage to 5 volts
4. Apply trigger voltage, observe corresponding output voltage (ac voltage and wave forms) at load terminal
5. Note down the voltage & frequency of out put wave form
6. The o/p ac voltage is almost equal to the two times of the dc i/p voltage.

.....
Signature of the staff with date

QUESTION BANK

4TH Semester EC/TC/ML

1. Obtain the VI characteristics of the SCR by conducting a suitable current and hence determine the holding current, forward ON state resistance & break over voltage.
2. Conduct a suitable experiment to obtain VI characteristics of the given three layer bi-directional switch experimentally. Determine the holding current and break over voltage in I and III quadrants and comment on its sensitivity.
3. Conduct a suitable experiment to obtain collector and transfer characteristics of IGBT.
4. Conduct a suitable experiment to obtain drain and transfer characteristics of MOSFET.
5. Conduct an experiment to obtain synchronized triggering pulses to turn ON SCR in full wave rectifier with resistive load. Show load voltage and triggering pulse waveform. Plot average DC voltage v/s delay angle.
6. Conduct an experiment to obtain synchronized triggering pulses to turn ON SCR in full wave rectifier with resistive and inductive load. Show load voltage and triggering pulse waveform. Plot average DC voltage v/s delay angle.
7. Conduct an experiment on controlled half wave rectifier to vary the DC power fed to load by using RC triggering. Plot o/p voltage v/s firing angle.
8. Conduct an experiment on controlled full wave rectifier to vary the DC power fed to load by using RC triggering. Plot o/p voltage v/s firing angle.
9. Conduct an experiment to control the illumination of incandescent lamp using TRIAC, DIAC combination. Plot the graph of V_{ORMS} v/s α .
10. Conduct an experiment to produce variable DC o/p voltage (chopper), plot o/p voltage v/s duty cycle for Variable frequency & Fixed Frequency.
11. Conduct an experiment to produce variable DC o/p voltage using voltage commutated chopper, plot o/p voltage v/s duty cycle for Fixed frequency operation.
12. Conduct a suitable experiment to control the speed of Induction motor. Plot speed v/s α .
13. Conduct a suitable experiment to control the speed of Universal motor. Plot speed v/s α .
14. Conduct a suitable experiment to obtain AC o/p using Series Inverter.
15. Demonstrate the digital firing circuit to turn ON SCR (HW) for R load. Plot V_{ODC} v/s α

**VIVA QUESTIONS
OF
POWR ELECTRONICS LAB**

Viva Questions Power Electronics Lab

1. What is power electronics?
2. Mention the different methods of varying the power?
3. What are the advantages of silicon over germanium?
4. What is power device?
5. Mention different types power devices?
6. What is SCR?
7. What are the features of SCR?
8. What are the features of Diac?
9. What is Diac?
10. What are the features of diac?
11. What are the applications of diac?
12. What is Triac?
13. What are the applications of Triac?
14. What are the applications of Triac?
15. What is power MOSFET?
16. What is power IGBT?
17. What are the applications of MOSFET & IGBT?
18. Compare SCR, Diac & Triac?
19. Compare MOSFET, BJT & IGBT?
20. What is turn of time?
21. What is turn off time?
22. What is static characteristics?
23. What is dynamic Characteristics?
24. What are the differences between static & dynamic Characteristics?
25. Explain gate characteristics & turn off characteristics of SCR?
26. Explain gate characteristics of SCR?
27. What is current controlled device?
28. What is voltage controlled device?
29. Explain o/p & transfer characteristics of MOSFET & IGBT?
30. What is the intention of using power device in power control circuit?
31. What is power control?
32. Why SCR is called as bidirectional an controlled device?
33. Why Diac is called as bidirectional an controlled Device?
34. Why Triac is called as bidirectional controlled device?
35. What is rectifier?
36. What is an inverter?
37. What is steep down chopper? What is its o/p voltage equation?
38. What is step up chopper? What is its o/p voltage equation?
39. What is buck boost regulator? What is its o/p voltage equation?

-
40. What is a buck regulator? What is its o/p voltage equation?
Explain the working operation of single phase controlled half wave rectifier with
 41. (a) R load
(b) RL load
(c) RL load with freewheeling diode
 42. What is the intention of using freewheeling across inductive load in rectifier circuit?
 43. What is pulse width?
 44. Why turn off time of the circuit should be greater than turn off time of the device?
Explain the working operation of single phase Full wave controlled rectifier with
 45. a) R load
b) RL load
c) RL load with freewheeling diode?
Explain the working operation of single phase Half controlled bridge rectifier with
 46. a) R load
b) RL load
c) RL load with freewheeling diode?
Explain the working operation of single phase full controlled bridge rectifier with
 47. a) R load
b) RL load
c) RL load with freewheeling diode?
 48. Define average output voltage, Rms Voltage, peak or maximum voltage?
 49. Derive an expression of average output voltage, Rms output voltage of any wave form concerned to rectifier, ac voltage controller, chopper?
 50. What is a cyclo converter?
 51. What is a cyclo inverter?
 52. Why forced commutation circuit is employed in case of a cyclo inverter?
 53. What are the advantages of a three phase circuit over a single phase circuit?
 54. What is firing angle or delay angle?
 55. What is conduction period?
 56. What is the meaning of triggering?
 57. What are the different types of triggering methods (Can be used to trigger SCR)?
 58. What is anode triggering, dv/dt triggering, temperature triggering, light triggering & gate triggering?
 59. Why gate triggering is preferred than other types?
 60. Mention the different types of gate triggering circuits?
 61. Explain the working operation of R- triggering circuit?
 62. Why firing angle in case of R- triggering circuit is limited to 90 degrees?
 63. Explain the working operation of RC triggering circuit?
 64. Explain how firing angle will be extended to more than 90° by using RC triggering circuit?
 65. What is a Uni-junction transistor (UJT)?
 66. Write equivalent circuit of UJT?
 67. Show that $V_{peak} = V_p = nV_{BB} + V_{diode}$ Where n = intrinsic standoff ratio, V_{BB} = applied or base voltage
-

68. Why UJT triggering circuit is superior than R & RC triggering circuit?
69. What is UJT relaxation oscillator?
70. What is line synchronized UJT triggering circuit?
71. Explain the working operation of UJT relaxation oscillator?
72. Explain the working operation of line synchronized UJT triggering circuit with wave forms at different points?
73. Design of UJT triggering circuit.
74. When UJT will conduct?
75. How UJT exhibits negative resistance property?
76. Why SCR, DIAC, TRIAC are called negative resistance devices?
77. Derive an expression of frequency of UJT triggering pulse?
78. What is the function of pulse Transformer?
79. What are the different types of voltage ratings, current ratings & power ratings? Explain each term
80. Why do we require protection circuits for power devices?
81. What is dv/dt rating? How do you protect SCR against high dv/dt rating? Explain
82. What is dv/dt rating? How do you protect SCR against high dv/dt rating? Explain
83. What is over current? How do you protect SCR against over current? Explain
84. What is over voltage? How do you protect SCR against over voltage? Explain
85. How device will be protected against heavy power dissipation?
86. Why Triac has 4 modes of operations?
87. Why 1st & 2nd mode of operations are operating in 1st quadrant and 3rd & 4th mode of operations are operating 3rd quadrant?
88. Why mode (1) is most sensitive among all modes?
89. What is commutation? What is commutation circuit?
90. Mention the different types of forced commutation circuit?
Explain the working operation of each forced commutation circuit with wave forms & derivation of designed equations
91. (class A, Class B, class C, Class D, Class E & Class F commutation circuit)
92. What is Latching current? What is its significance?
93. What is Holding current? What is its significance?
94. What is dv/dt Rating? What is its significance?
95. What is dual converter?
Why full wave bridge controlled bridge rectifier with RL load (not with freewheeling diode) is preferred in dual converter than half wave bridge controlled rectifier with RL load (not with freewheeling diode).?
96. Why dual converter is called as four quadrant operator?
98. What is semi converter?
99. What is full converter?
100. Why gate is preferred at base of NPN transistor & not at the base of PNP transistor in SCR?
101. Derive an expression of anode current (SCR current)?
102. Explain the working operation of SCR with two transistor analogy?

103. Explain the working operation of each practical power electronics experiments with circuit diagram, wave forms & designed equations?
104. Why output voltage is more at lesser value of firing angle?
105. What are the differences between uncontrolled output & controlled output?
106. How do you design zener voltage regulator?
107. How do you select (design) the value of gate resistor and load resistor concerned to SCR experiment?
108. How do you check SCR, Triac, Diac, Diode, Zener diode, wires by using ohm meter?
109. How do you check an ammeter, voltmeter & power supply?
110. Why load resistor has higher wattage?
111. What is series inverter? Mention the advantages, disadvantages & applications of series inverter? Explain its working operation?
112. What is parallel inverter? Explain its working operation?
113. What is continuous mode & discontinuous mode of operations concerned to rectifier with (a). RL load (b) RL load with freewheeling diode.
114. Input voltage = device voltage + output voltage.
Prove above words
115. What is blocking state or region?
116. What is forward blocking & reverse blocking?
117. What is reverse recovery time?
118. What is gate pulse?
119. Why gate pulses are preferred than continuous gate voltage?
120. S.T. turn on time = $t_d + t_r + t_s$
121. S.T. turn off time = $t_{tr} + t_{gr}$
122. How do you design gate pulse width?
123. What is snubber circuit? How do you design snubber?
124. What is heat sink? Its purpose is what?
125. What is circuit breaker & fuse? Why these are used in power circuit?
126. What is ac voltage controller? Mention different types? What are its applications?
Explain the working operation of
(a). on & off AC voltage controller
127. (b). uni directional or Half wave controller
(c) . Bidirectional or Full wave AC voltage controller
with R load & RL load with wave forms, with equations?
128. Why continuous gate pulses are applied to full wave ac voltage controller with RL load circuit?
129. Explain the working operation of static on load tap changer?
130. Why negative gate voltage should not be applied to gate of SCR?
131. Write symbols, static characteristics of all power devices concerned to syllabus?
132. Name different current controlled power devices?
133. Name different voltage controlled power devices?
134. What is I^2t rating?

Data Sheets



BY127, BY133, EM513, EM516

GENERAL PURPOSE PLASTIC RECTIFIER


Reverse Voltage - 1250 to 1800 Volts

Forward Current - 1.0 Ampere

Features

- The plastic package carries Underwriters Laboratory Flammability Classification 94V-0
- Construction utilizes void-free molded plastic technique
- Low reverse leakage
- Low forward voltage drop
- High current capability
- High reliability
- High surge current capability

DO-41

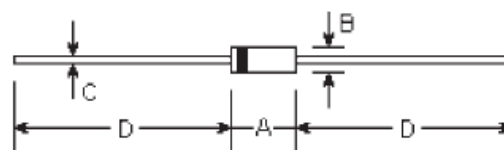

Mechanical Data

- **Case:** Molded plastic, DO-41
- **Lead:** Axial leads, solderable per MIL-STD-202, method 208 guaranteed
- **Polarity:** Color band denotes cathode end
- **Mounting Position:** Any
- **Weight:** 0.012 ounce, 0.33 gram

DIM	DIMENSIONS				Note
	inches		mm		
	Min.	Max.	Min.	Max.	
A	0.165	0.205	4.2	5.2	
B	0.079	0.106	2.0	2.7	ϕ
C	0.028	0.034	0.71	0.86	ϕ
D	1.000	-	25.40	-	

Maximum Ratings and Electrical Characteristics

Ratings at 25°C ambient temperature unless otherwise specified.

Single phase, half wave, 60Hz, resistive or inductive load.

For capacitive load, derate current by 20%.

	Symbols	BY127	BY133	EM513	EM516	Units
Maximum repetitive peak reverse voltage	V_{RRM}	1250	1300	1600	1800	Volts
Maximum RMS voltage	V_{RMS}	875	910	1120	1270	Volts
Maximum DC blocking voltage	V_{DC}	1250	1300	1600	1800	Volts
Maximum average forward rectified current 0.375" (9.5mm) lead length at $T_A=75^\circ\text{C}$	$I_{(AV)}$	1.0				Amp
Peak forward surge current 8.3mS single half sine-wave superimposed on rated load (MIL-STD-750D 4066 method)	I_{FSM}	30.0				Amps
Maximum forward voltage at 1.0A DC and 25°C	V_F	1.1				Volts
Maximum full load reverse current at rated DC blocking voltage $T_A=25^\circ\text{C}$ $T_A=100^\circ\text{C}$	I_R	5.0 200.0				μA
Typical junction capacitance (Note 1)	C_J	15.0				μF
Typical thermal resistance (Note 2)	$R_{\theta JA}$ $R_{\theta JL}$	50.0 25.0				°C/W
Operating and storage temperature range	T_J , T_{STG}	-55 to +150				°C

Notes:

(1) Measured at 1.0MHz and applied reverse voltage of 4.0 VDC

(2) Thermal resistance junction to ambient and from junction to lead at 0.375" (9.5mm) lead length, P.C.B. mounted

	<p>DC COMPONENTS CO., LTD.</p> <p>RECTIFIER SPECIALISTS</p>	<p>1N / RL 4001A / 101 THRU 1N / RL 4007A / 107</p>
---	--	---

TECHNICAL SPECIFICATIONS OF SILICON RECTIFIER
VOLTAGE RANGE - 50 to 1000 Volts CURRENT - 1.0 Ampere


FEATURES

- * High reliability
- * Low leakage
- * Low forward voltage drop
- * High current capability

MECHANICAL DATA

- * Case: Molded plastic
- * Epoxy: UL 94V-0 rate flame retardant
- * Lead: MIL-STD-202E, Method 208 guaranteed
- * Polarity: Color band denotes cathode end
- * Mounting position: Any
- * Weight: 0.22 gram

A-405

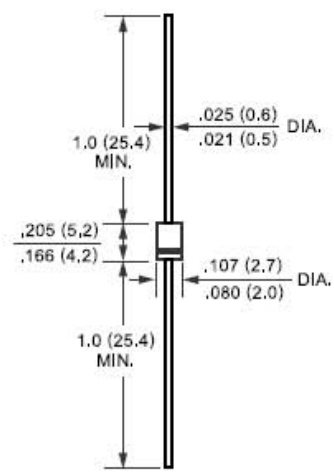

Dimensions in inches and (millimeters)

MAXIMUM RATINGS AND ELECTRICAL CHARACTERISTICS

Ratings at 25 °C ambient temperature unless otherwise specified.
 Single phase, half wave, 60 Hz, resistive or inductive load.
 For capacitive load, derate current by 20%.

		1N4001A	1N4002A	1N4003A	1N4004A	1N4005A	1N4006A	1N4007A	
	SYMBOL	RL101	RL102	RL103	RL104	RL105	RL106	RL107	UNITS
Maximum Recurrent Peak Reverse Voltage	V_{RRM}	50	100	200	400	600	800	1000	Volts
Maximum RMS Voltage	V_{RMS}	35	70	140	280	420	560	700	Volts
Maximum DC Blocking Voltage	V_{DC}	50	100	200	400	600	800	1000	Volts
Maximum Average Forward Rectified Current at $T_A = 55^\circ C$	I_o	1.0							Amps
Peak Forward Surge Current, 8.3 ms single half sine-wave superimposed on rated load (JEDEC Method)	I_{FSM}	30							Amps
Maximum Instantaneous Forward Voltage at 1.0A DC	V_F	1.1							Volts
Maximum DC Reverse Current at Rated DC Blocking Voltage	@ $T_A = 25^\circ C$	5.0							uAmps
	@ $T_A = 100^\circ C$	500							
Maximum Full Load Reverse Current Average, Full Cycle .375" (9.5mm) lead length at $T_L = 75^\circ C$	I_R	30							uAmps
Typical Junction Capacitance (Note)	C_J	15							pF
Typical Thermal Resistance	$R_{\theta JA}$	50							$^\circ C/W$
Operating and Storage Temperature Range	T_J, T_{STG}	-65 to + 175							$^\circ C$

NOTES : Measured at 1 MHz and applied reverse voltage of 4.0 volts



2N2646


SILICON PN UNIJUNCTION TRANSISTOR

DESCRIPTION:

The **2N2646** is a Unijunction Transistor Used in General Purpose Pulse, Timing, Sense and Trigger Applications.

MAXIMUM RATINGS

I_C	2.0 A (PULSED)
V_{CE}	30 V
P_{DISS}	300 mW @ $T_C = 25^\circ\text{C}$
T_J	-65°C to $+125^\circ\text{C}$
T_{STG}	-65°C to $+150^\circ\text{C}$
θ_{JC}	33°C/W

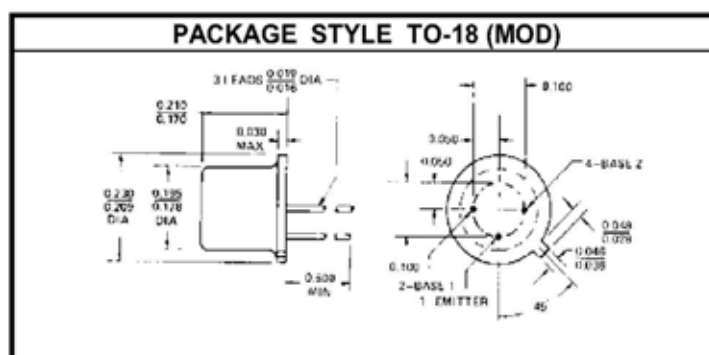


CHARACTERISTICS $T_C = 25^\circ\text{C}$

SYMBOL	TEST CONDITIONS	MINIMUM	TYPICAL	MAXIMUM	UNITS
η	$V_{B2B1} = 10\text{ V}$	0.56		0.75	--
r_{BB}	$V_{B2B1} = 3.0\text{ V}$	4.7		9.1	$\text{K}\Omega$
α_{BB}	$V_{B2B1} = 3.0\text{ V}$ $T_A = -55$ to 125°C	0.1		0.9	$\%/^\circ\text{C}$
$V_{EB1(\text{SAT})}$	$V_{B2B1} = 10\text{ V}$ $I_E = 50\text{ mA}$		3.0		V
$I_{B2(\text{MOD})}$	$V_{B2B1} = 10\text{ V}$ $I_E = 50\text{ mA}$		20		mA
I_{B2EO}	$V_{B2E} = 30\text{ V}$ $I_{B1} = 0$			12	μA
I_P	$V_{B2B1} = 25\text{ V}$			5.0	μA
I_V	$V_{B2B1} = 20\text{ V}$ $R_{B2} = 100\ \Omega$	4.0			mA
V_{OB1}	$V_{B2B1} = 20\text{ V}$ $R_{B1} = 20\ \Omega$	3.0	5.0		V


SCR TRIGGER PULSE TRANSFORMER

Turns Ratio 1 : 1 : 1				
PARAMETER @25°C	MIN.	TYP.	MAX.	UNITS
Inductance		200		μH
Leakage Inductance		1.5		μH
DCR Each Winding		47.7		mΩ
Interwinding Capacitance		8.5		Pf
Hipot	2000			VRMS

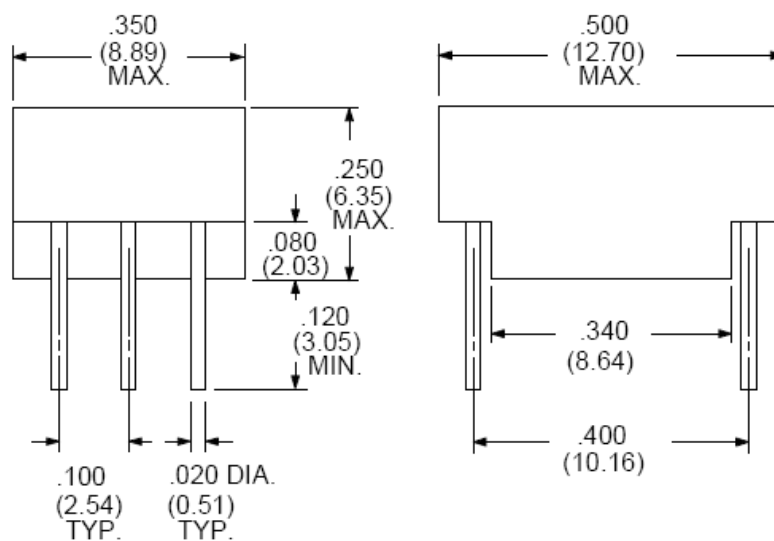PHYSICAL DIMENSIONS All dimensions in inches (mm):



SCHEMATIC DIAGRAM:

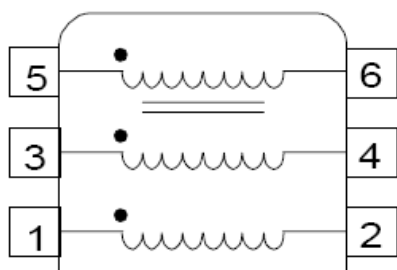

RHOMBUS P/N: T-1214



TYN606
TYN1006

SCR


FEATURES

- High surge capability
- High on-state current
- High stability and reliability

DESCRIPTION

The TYN606 and TYN1006 Family of Silicon Controlled Rectifiers are high performance glass passivated technology.

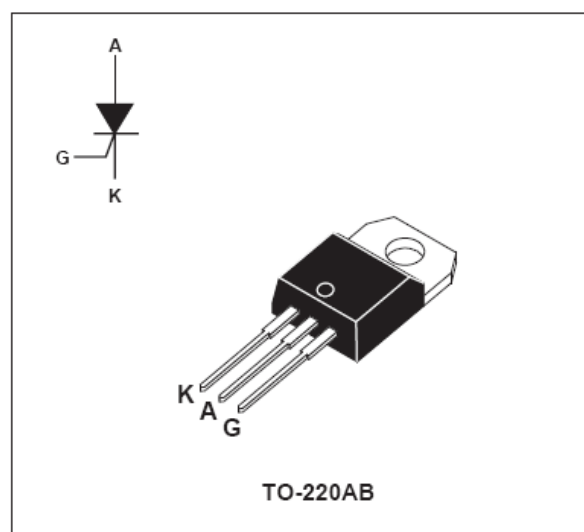This general purpose Family of Silicon Controlled Rectifiers is designed for power supply up to 400Hz on resistive or inductive load.



ABSOLUTE RATINGS (limiting values)

Symbol	Parameter		Value	Unit
$I_{T(RMS)}$	RMS on-state current (180° conduction angle)	$T_c = 110^\circ\text{C}$	6	A
$I_{T(AV)}$	Average on-state current (180° conduction angle, single phase circuit)	$T_c = 110^\circ\text{C}$	3.8	A
I_{TSM}	Non repetitive surge peak on-state current (T_j initial = 25°C)	$t_p = 8.3\text{ms}$	73	A
		$t_p = 10\text{ms}$	70	
I^2t	I^2t value	$t_p = 10\text{ms}$	24.5	A ² s
di/dt	Critical rate of rise of on-state current Gate supply: $I_G = 100\text{mA}$ $di_G/dt = 1\text{A}/\mu\text{s}$		50	A/ μs
T_{stg} T_j	Storage and operating junction temperature range		-40 to +150 -40 to +125	°C
T_I	Maximum lead soldering temperature during 10s at 4.5mm from case		260	°C

Symbol	Parameter	TYN		Unit
		606	1006	
V_{DRM} V_{RRM}	Repetitive peak off-state voltage $T_j = 125^\circ\text{C}$	600	1000	V

TYN606 TYN1006

THERMAL RESISTANCE

Symbol	Parameter	Value	Unit
Rth (j-a)	Junction to ambient	60	°C/W
Rth (j-c) DC	Junction to case for DC	2.5	°C/W

GATE CHARACTERISTICS (maximum values)

$P_{G(AV)} = 1W$ $P_{GM} = 10W$ ($t_p = 20\mu s$) $I_{FGM} = 4A$ ($t_p = 20\mu s$) $V_{RGM} = 5V$

ELECTRICAL CHARACTERISTICS

Symbol	Test conditions	Value	Unit
I_{GT}	$V_D = 12V$ (DC) $R_L = 33\Omega$	$T_j = 25^\circ C$ MAX.	15 mA
V_{GT}	$V_D = 12V$ (DC) $R_L = 33\Omega$	$T_j = 25^\circ C$ MAX.	1.5 V
V_{GD}	$V_D = V_{DRM}$ $R_L = 3.3k\Omega$	$T_j = 110^\circ C$ MIN.	0.2 V
tgt	$V_D = V_{DRM}$ $I_G = 40mA$ $di_G/dt = 0.5A/\mu s$	$T_j = 25^\circ C$ TYP.	2 μs
I_L	$I_G = 1.2I_{GT}$	$T_j = 25^\circ C$ TYP.	50 mA
I_H	$I_T = 100mA$ Gate open	$T_j = 25^\circ C$ MAX.	30 mA
V_{TM}	$I_{TM} = 12A$ $t_p = 380\mu s$	$T_j = 25^\circ C$ MAX.	1.6 V
I_{DRM} I_{RRM}	V_{DRM} rated V_{RRM} rated	$T_j = 25^\circ C$ MAX.	0.01 mA
		$T_j = 110^\circ C$ MAX.	2
dV/dt	Linear slope up to $V_D = 67\% V_{DRM}$ gate open	$T_j = 110^\circ C$ MIN.	200 V/ μs
tq	$V_D = 67\% V_{DRM}$ $I_{TM} = 12A$ $V_R = 25V$ $di_{TM}/dt = 30 A/\mu s$ $dV_D/dt = 50V/\mu s$	$T_j = 110^\circ C$ TYP.	70 μs

Fig. 1: Maximum average power dissipation versus average on-state current.


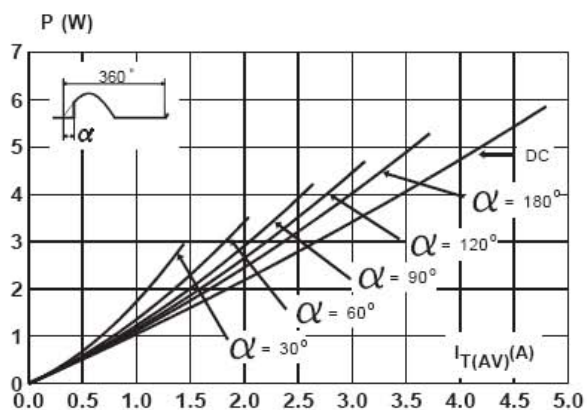


Fig. 2: Correlation between maximum average power dissipation and maximum allowable temperatures (T_{amb} and T_{case}) for different thermal resistances heatsink + contact.

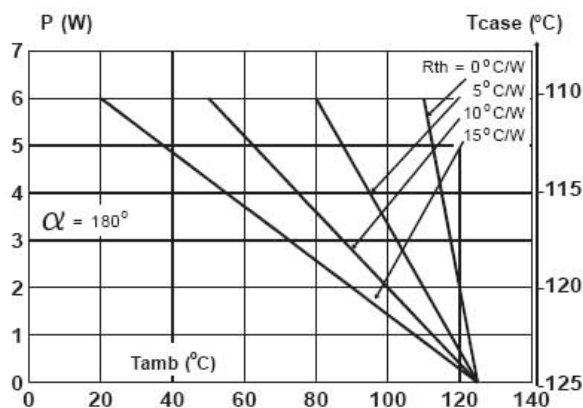

Triacs

BT136 series

GENERAL DESCRIPTION

Glass passivated triacs in a plastic envelope, intended for use in applications requiring high bidirectional transient and blocking voltage capability and high thermal cycling performance. Typical applications include motor control, industrial and domestic lighting, heating and static switching.


QUICK REFERENCE DATA

SYMBOL	PARAMETER	MAX.	MAX.	MAX.	UNIT
V_{DRM}	Repetitive peak off-state voltages	BT136-500F	600	800	V
		BT136-500G	600G	800G	
		BT136-500	600	800	
$I_{T(RMS)}$	RMS on-state current	4	4	4	A
I_{TSM}	Non-repetitive peak on-state current	25	25	25	A


PINNING - TO220AB

PIN	DESCRIPTION
1	main terminal 1
2	main terminal 2
3	gate
tab	main terminal 2

PIN CONFIGURATION

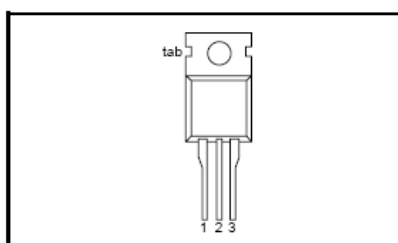

SYMBOL

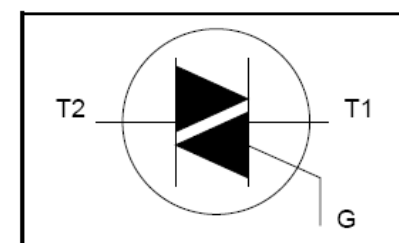

LIMITING VALUES

Limiting values in accordance with the Absolute Maximum System (IEC 134).

SYMBOL	PARAMETER	CONDITIONS	MIN.	MAX.			UNIT
				-500	-600	-800	
V_{DRM}	Repetitive peak off-state voltages		-	500 ¹	600 ¹	800	V
$I_{T(RMS)}$	RMS on-state current	full sine wave; $T_{mb} \leq 107^\circ C$	-	4			A
I_{TSM}	Non-repetitive peak on-state current	full sine wave; $T_j = 25^\circ C$ prior to surge	-	25			A
I^2t	I^2t for fusing	$t = 20\text{ ms}$	-	27			A
		$t = 16.7\text{ ms}$	-	3.1			A ² s
di_T/dt	Repetitive rate of rise of on-state current after triggering	$t = 10\text{ ms}$ $I_{TM} = 6\text{ A}; I_G = 0.2\text{ A}; di_G/dt = 0.2\text{ A}/\mu\text{s}$	-	50			A/ μs
I_{GM}	Peak gate current	T2+ G+	-	50			A/ μs
		T2+ G-	-	50			A/ μs
		T2- G-	-	50			A/ μs
		T2- G+	-	10			A/ μs
V_{GM}	Peak gate voltage		-	2			V
P_{GM}	Peak gate power		-	5			W
$P_{G(AV)}$	Average gate power	over any 20 ms period	-	0.5			W
T_{stg}	Storage temperature		-40	150			$^\circ C$
T_j	Operating junction temperature		-	125			$^\circ C$

1 Although not recommended, off-state voltages up to 800V may be applied without damage, but the triac may switch to the on-state. The rate of rise of current should not exceed 3 A/ μs .

Philips Semiconductors

Product specification

Triacs

BT136 series

THERMAL RESISTANCES

SYMBOL	PARAMETER	CONDITIONS	MIN.	TYP.	MAX.	UNIT
$R_{th\ j-mb}$	Thermal resistance junction to mounting base	full cycle	-	-	3.0	K/W
$R_{th\ j-a}$	Thermal resistance junction to ambient	half cycle in free air	-	60	3.7	K/W

STATIC CHARACTERISTICS $T_j = 25\text{ }^\circ\text{C}$ unless otherwise stated

SYMBOL	PARAMETER	CONDITIONS	MIN.	TYP.	MAX.			UNIT
I_{GT}	Gate trigger current	BT136- $V_D = 12\text{ V}; I_T = 0.1\text{ A}$	-	-F	...G	
		T2+ G+	-	5	35	25	50	mA
		T2+ G-	-	8	35	25	50	mA
		T2- G-	-	11	35	25	50	mA
I_L	Latching current	$V_D = 12\text{ V}; I_{GT} = 0.1\text{ A}$	-	30	70	70	100	mA
		T2- G+	-	7	20	20	30	mA
		T2+ G+	-	16	30	30	45	mA
		T2+ G-	-	5	20	20	30	mA
I_H	Holding current	$V_D = 12\text{ V}; I_{GT} = 0.1\text{ A}$	-	5	15	15	30	mA
		T2- G+	-	7	30	30	45	mA
V_T	On-state voltage	$I_T = 5\text{ A}$	-	1.4	1.70			V
V_{GT}	Gate trigger voltage	$V_D = 12\text{ V}; I_T = 0.1\text{ A}$	-	0.7	1.5			V
		$V_D = 400\text{ V}; I_T = 0.1\text{ A};$ $T_j = 125\text{ }^\circ\text{C}$	0.25	0.4	-			V
I_D	Off-state leakage current	$V_D = V_{DRM(max)}$; $T_j = 125\text{ }^\circ\text{C}$	-	0.1	0.5			mA

DYNAMIC CHARACTERISTICS $T_j = 25\text{ }^\circ\text{C}$ unless otherwise stated


SYMBOL	PARAMETER	CONDITIONS	MIN.			TYP.	MAX.	UNIT
dV_D/dt	Critical rate of rise of off-state voltage	BT136- $V_{DM} = 67\% V_{DRM(max)}$; $T_j = 125\text{ }^\circ\text{C}$; exponential waveform; gate open circuit	100	50	200	250	-	V/ μs
dV_{com}/dt	Critical rate of change of commutating voltage	$V_{DM} = 400\text{ V}; T_j = 95\text{ }^\circ\text{C};$ $I_{T(RMS)} = 4\text{ A};$ $dI_{com}/dt = 1.8\text{ A/ms}$; gate open circuit	-	-	10	50	-	V/ μs
t_{gt}	Gate controlled turn-on time	$I_{TM} = 6\text{ A}; V_D = V_{DRM(max)}$; $I_G = 0.1\text{ A}; dI_G/dt = 5\text{ A}/\mu\text{s}$	-	-	-	2	-	μs

TRIGGER DIODES
FEATURES

- V_{BO} : 32V / 34V / 40V VERSIONS
- LOW BREAKOVER CURRENT

DESCRIPTION

High reliability glass passivation insuring parameter stability and protection against junction contamination.

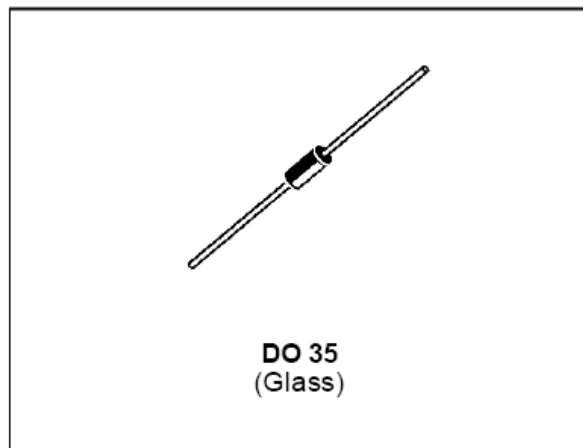
ABSOLUTE RATINGS (limiting values)

Symbol	Parameter		Value	Unit
P	Power dissipation on printed circuit (L = 10 mm)	$T_a = 65\text{ }^\circ\text{C}$	150	mW
I_{TRM}	Repetitive peak on-state current	$t_p = 20\text{ }\mu\text{s}$ $F = 100\text{ Hz}$	2	A
T_{stg} T_j	Storage and operating junction temperature range		- 40 to + 125 - 40 to + 125	$^\circ\text{C}$ $^\circ\text{C}$

THERMAL RESISTANCES

Symbol	Parameter	Value	Unit
$R_{th(j-a)}$	Junction to ambient	400	$^\circ\text{C/W}$
$R_{th(j-l)}$	Junction-leads	150	$^\circ\text{C/W}$

DB3 / DB4 / DC34

ELECTRICAL CHARACTERISTICS (Tj = 25°C)

Symbol	Parameter	Test Conditions		Value			Unit
				DB3	DC34	DB4	
V _{BO}	Breakover voltage *	C = 22nF ** see diagram 1	MIN	28	30	35	V
			TYP	32	34	40	
			MAX	36	38	45	
[+V _{BO} - V _{BO}]	Breakover voltage symmetry	C = 22nF ** see diagram 1	MAX	± 3			V
ΔV± I	Dynamic breakover voltage *	ΔI = [I _{BO} to I _F =10mA] see diagram 1	MIN	5			V
V _O	Output voltage *	see diagram 2	MIN	5			V
I _{BO}	Breakover current *	C = 22nF **	MAX	100	50	100	μA
t _r	Rise time *	see diagram 3	TYP	1.5			μs
I _B	Leakage current *	V _B = 0.5 V _{BO} max see diagram 1	MAX	10			μA

* Electrical characteristic applicable in both forward and reverse directions.

** Connected in parallel with the devices.

DIAGRAM 1 : Current-voltage characteristics

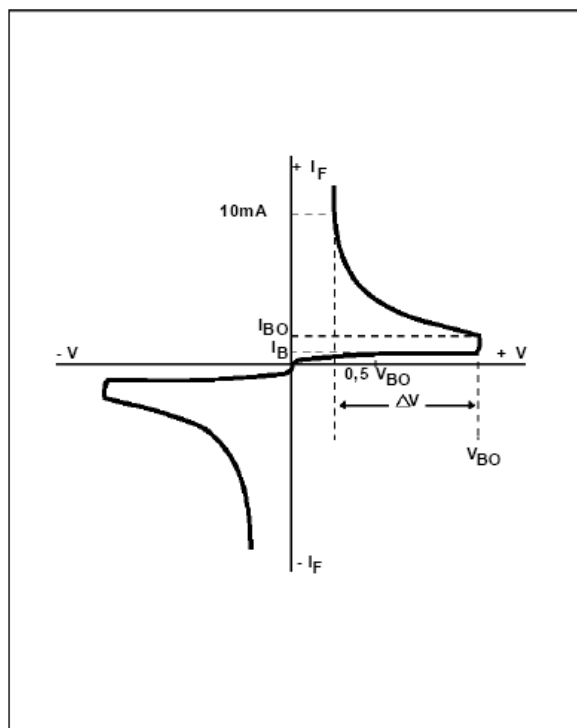


DIAGRAM 2 : Test circuit for output voltage


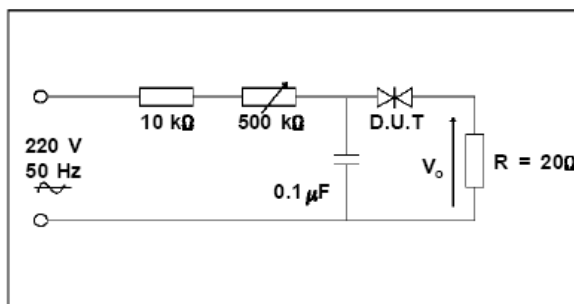


DIAGRAM 3 : Test circuit see diagram 2. Adjust R for I_p=0.5A

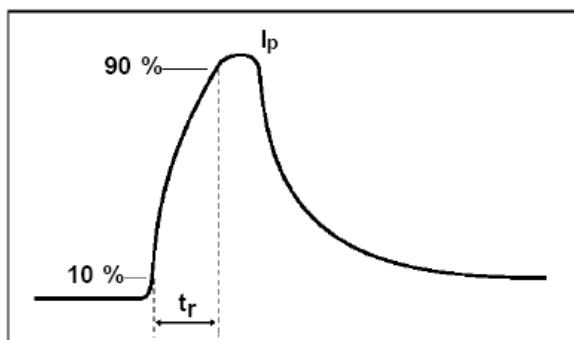



IRF740

N - CHANNEL 400V - 0.48 Ω - 10 A - TO-220
PowerMESH™ MOSFET

TYPE	V _{DSS}	R _{DS(on)}	I _D
IRF740	400 V	< 0.55 Ω	10 A



- TYPICAL R_{DS(on)} = 0.48 Ω
- EXTREMELY HIGH dv/dt CAPABILITY
- 100% AVALANCHE TESTED
- VERY LOW INTRINSIC CAPACITANCES
- GATE CHARGE MINIMIZED

DESCRIPTION

This power MOSFET is designed using the company's consolidated strip layout-based MESH OVERLAY™ process. This technology matches and improves the performances compared with standard parts from various sources.

APPLICATIONS

- HIGH CURRENT SWITCHING
- UNINTERRUPTIBLE POWER SUPPLY (UPS)
- DC/DC CONVERTERS FOR TELECOM, INDUSTRIAL, AND LIGHTING EQUIPMENT.

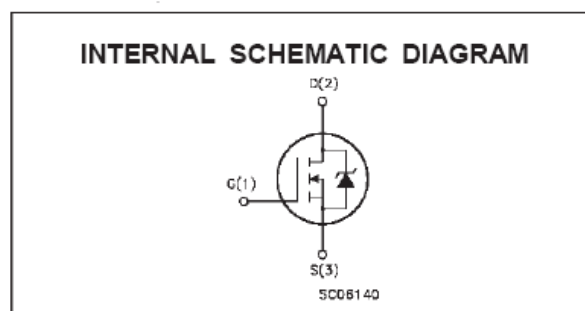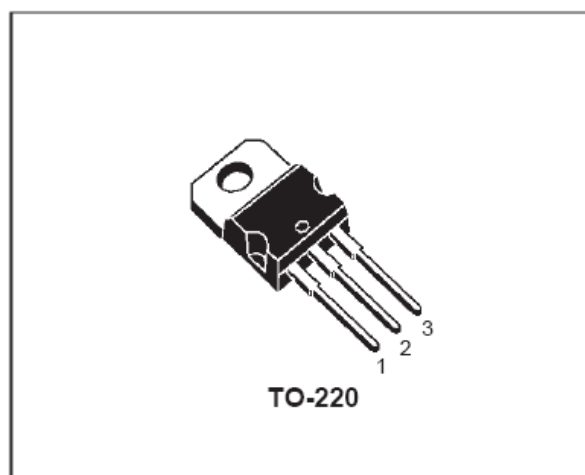**ABSOLUTE MAXIMUM RATINGS**

Symbol	Parameter	Value	Unit
V _{DS}	Drain-source Voltage (V _{GS} = 0)	400	V
V _{DGR}	Drain- gate Voltage (R _{GS} = 20 k Ω)	400	V
V _{GS}	Gate-source Voltage	\pm 20	V
I _D	Drain Current (continuous) at T _c = 25 °C	10	A
I _D	Drain Current (continuous) at T _c = 100 °C	6.3	A
I _{DM} (*)	Drain Current (pulsed)	40	A
P _{tot}	Total Dissipation at T _c = 25 °C	125	W
	Derating Factor	1.0	W/°C
dv/dt(1)	Peak Diode Recovery voltage slope	4.0	V/ns
T _{stg}	Storage Temperature	-65 to 150	°C
T _j	Max. Operating Junction Temperature	150	°C

(*) Pulse width limited by safe operating area

(1) I_{SD} \leq 10 A, di/dt \leq 120 A/ μ s, V_{DD} \leq V_{(BR)DSS}, T_j \leq T_{JMAX}
 First Digit of the Datecode Being Z or K Identifies Silicon Characterized in this Datasheet

IRF740

THERMAL DATA

$R_{thj-case}$	Thermal Resistance Junction-case	Max	1.0	$^{\circ}C/W$
$R_{thj-amb}$	Thermal Resistance Junction-ambient	Max	62.5	$^{\circ}C/W$
$R_{thc-sink}$	Thermal Resistance Case-sink	Typ	0.5	$^{\circ}C/W$
T_I	Maximum Lead Temperature For Soldering Purpose		300	$^{\circ}C$

AVALANCHE CHARACTERISTICS

Symbol	Parameter	Max Value	Unit
I_{AR}	Avalanche Current, Repetitive or Not-Repetitive (pulse width limited by T_j max)	10	A
E_{AS}	Single Pulse Avalanche Energy (starting $T_j = 25^{\circ}C$, $I_D = I_{AR}$, $V_{DD} = 50$ V)	520	mJ

ELECTRICAL CHARACTERISTICS ($T_{case} = 25^{\circ}C$ unless otherwise specified)

OFF

Symbol	Parameter	Test Conditions	Min.	Typ.	Max.	Unit
$V_{(BR)DSS}$	Drain-source Breakdown Voltage	$I_D = 250 \mu A$ $V_{GS} = 0$	400			V
I_{DSS}	Zero Gate Voltage Drain Current ($V_{GS} = 0$)	$V_{DS} = \text{Max Rating}$ $V_{DS} = \text{Max Rating}$ $T_c = 125^{\circ}C$			1 50	μA μA
I_{GSS}	Gate-body Leakage Current ($V_{DS} = 0$)	$V_{GS} = \pm 20$ V			± 100	nA

ON (*)


Symbol	Parameter	Test Conditions	Min.	Typ.	Max.	Unit
$V_{GS(th)}$	Gate Threshold Voltage	$V_{DS} = V_{GS}$ $I_D = 250 \mu A$	2	3	4	V
$R_{DS(on)}$	Static Drain-source On Resistance	$V_{GS} = 10$ V $I_D = 5.3$ A		0.48	0.55	Ω
$I_{D(on)}$	On State Drain Current	$V_{DS} > I_{D(on)} \times R_{DS(on)max}$ $V_{GS} = 10$ V	10			A

DYNAMIC

Symbol	Parameter	Test Conditions	Min.	Typ.	Max.	Unit
$g_{fs} (*)$	Forward Transconductance	$V_{DS} > I_{D(on)} \times R_{DS(on)max}$ $I_D = 6$ A	5.8			S
C_{iss}	Input Capacitance	$V_{DS} = 25$ V $f = 1$ MHz $V_{GS} = 0$		1400		pF
C_{oss}	Output Capacitance			220		pF
C_{rss}	Reverse Transfer Capacitance			27		pF

Features

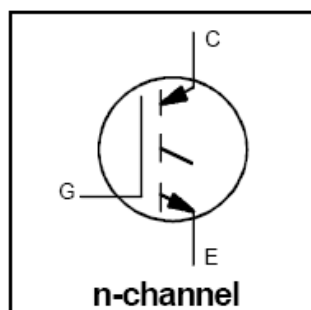- Switching-loss rating includes all "tail" losses
- Optimized for medium operating frequency (1 to 10kHz) See Fig. 1 for Current vs. Frequency curve




$$V_{CES} = 600V$$

$$V_{CE(sat)} \leq 2.8V$$

$$@V_{GE} = 15V, I_C = 9.0A$$

Description

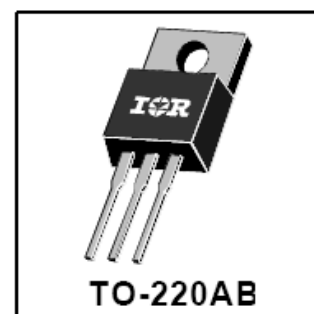Insulated Gate Bipolar Transistors (IGBTs) from International Rectifier have higher usable current densities than comparable bipolar transistors, while at the same time having simpler gate-drive requirements of the familiar power MOSFET. They provide substantial benefits to a host of high-voltage, high-current applications.



Absolute Maximum Ratings

	Parameter	Max.	Units
V_{CES}	Collector-to-Emitter Voltage	600	V
$I_C @ T_C = 25^\circ C$	Continuous Collector Current	16	A
$I_C @ T_C = 100^\circ C$	Continuous Collector Current	9.0	
I_{CM}	Pulsed Collector Current ①	64	
I_{LM}	Clamped Inductive Load Current ②	64	
V_{GE}	Gate-to-Emitter Voltage	± 20	V
E_{ARV}	Reverse Voltage Avalanche Energy ③	5.0	mJ
$P_D @ T_C = 25^\circ C$	Maximum Power Dissipation	60	W
$P_D @ T_C = 100^\circ C$	Maximum Power Dissipation	24	
T_J	Operating Junction and Storage Temperature Range	-55 to +150	°C
T_{STG}			
	Soldering Temperature, for 10 sec.	300 (0.063 in. (1.6mm) from case)	
	Mounting torque, 6-32 or M3 screw.	10 lbf·in (1.1N·m)	

Thermal Resistance

	Parameter	Min.	Typ.	Max.	Units
$R_{\theta JC}$	Junction-to-Case	—	—	2.1	°C/W
$R_{\theta CS}$	Case-to-Sink, flat, greased surface	—	0.50	—	
$R_{\theta JA}$	Junction-to-Ambient, typical socket mount	—	—	80	
Wt	Weight	—	2.0 (0.07)	—	g (oz)



1N4728A - 1N4752A Series One Watt Zeners

Absolute Maximum Ratings*

TA = 25°C unless otherwise noted

Tolerance: A = 5%

Parameter	Value	Units
Storage Temperature Range	-85 to +200	°C
Maximum Junction Operating Temperature	+ 200	°C
Lead Temperature (1/16" from case for 10 seconds)	+ 230	°C
Total Device Dissipation Derate above 50°C	1.0 6.67	W mW/°C
Thermal resistance Junction to Lead	63.5	°C/W
Thermal resistance Junction to Ambient	100	°C/W
Surge Power**	10	W



*These ratings are limiting values above which the serviceability of the diode may be impaired.

**Non-recurrent square wave PW= 8.3 ms, TA= 55 degrees C.

NOTES:

- 1) These ratings are based on a maximum junction temperature of 200 degrees C.
- 2) These are steady state limits. The factory should be consulted on applications involving pulsed or low duty cycle operations.

Electrical Characteristics

TA = 25°C unless otherwise noted

Device	V _Z (V)	Z _Z (Ω)	@ I _{ZT} (mA)	Z _{ZK} (Ω)	@ I _{ZK} (mA)	V _R (V)	@ I _R (μA)	I _{SURGE} (mA)	I _{ZM} (mA)
1N4728A	3.3	10	76	400	1.0	1.0	100	1,380	276
1N4729A	3.6	10	69	400	1.0	1.0	100	1,260	252
1N4730A	3.9	9.0	64	400	1.0	1.0	50	1,190	234
1N4731A	4.3	9.0	58	400	1.0	1.0	10	1,070	217
1N4732A	4.7	8.0	53	500	1.0	1.0	10	970	193
1N4733A	5.1	7.0	49	550	1.0	1.0	10	890	178
1N4734A	5.6	5.0	45	600	1.0	2.0	10	810	162
1N4735A	6.2	2.0	41	700	1.0	3.0	10	730	146
1N4736A	6.8	3.5	37	700	1.0	4.0	10	660	133
1N4737A	7.5	4.0	34	700	0.5	5.0	10	605	121
1N4738A	8.2	4.5	31	700	0.5	6.0	10	550	110
1N4739A	9.1	5.0	28	700	0.5	7.0	10	500	100
1N4740A	10	7.0	25	700	0.25	7.6	10	454	91
1N4741A	11	8.0	23	700	0.25	8.4	5.0	414	83
1N4742A	12	9.0	21	700	0.25	9.1	5.0	380	76
1N4743A	13	10	19	700	0.25	9.9	5.0	344	69
1N4744A	15	14	17	700	0.25	11.4	5.0	304	61
1N4745A	16	16	15.5	700	0.25	12.2	5.0	285	57
1N4746A	18	20	14	750	0.25	13.7	5.0	250	50
1N4747A	20	22	12.5	750	0.25	15.2	5.0	225	45
1N4748A	22	23	11.5	750	0.25	16.7	5.0	205	41
1N4749A	24	25	10.5	750	0.25	18.2	5.0	190	38
1N4750A	27	35	9.5	750	0.25	20.6	5.0	170	34
1N4751A	30	40	8.5	1,000	0.25	22.8	5.0	150	30
1N4752A	33	45	7.5	1,000	0.25	25.1	5.0	135	27

V_F Forward Voltage = 1.2 V Maximum @ I_F = 200 mA for all 1N4700 series

IRGBC20F

Electrical Characteristics @ $T_J = 25^\circ\text{C}$ (unless otherwise specified)

	Parameter	Min.	Typ.	Max.	Units	Conditions
$V_{(BR)CES}$	Collector-to-Emitter Breakdown Voltage	600	—	—	V	$V_{GE} = 0V, I_C = 250\mu A$
$V_{(BR)ECS}$	Emitter-to-Collector Breakdown Voltage ④	20	—	—	V	$V_{GE} = 0V, I_C = 1.0A$
$\Delta V_{(BR)CES}/\Delta T_J$	Temp. Coeff. of Breakdown Voltage	—	0.72	—	V/°C	$V_{GE} = 0V, I_C = 1.0mA$
$V_{CE(on)}$	Collector-to-Emitter Saturation Voltage	—	2.0	2.8	V	$I_C = 9.0A, V_{GE} = 15V$ See Fig. 2, 5
		—	2.6	—		
		—	2.3	—		
$V_{GE(th)}$	Gate Threshold Voltage	3.0	—	5.5		$V_{CE} = V_{GE}, I_C = 250\mu A$
$\Delta V_{GE(th)}/\Delta T_J$	Temp. Coeff. of Threshold Voltage	—	-11	—	mV/°C	$V_{CE} = V_{GE}, I_C = 250\mu A$
g_{fe}	Forward Transconductance ⑤	2.9	5.1	—	S	$V_{CE} = 100V, I_C = 9.0A$
I_{CES}	Zero Gate Voltage Collector Current	—	—	250	μA	$V_{GE} = 0V, V_{CE} = 600V$
		—	—	1000		$V_{GE} = 0V, V_{CE} = 600V, T_J = 150^\circ\text{C}$
I_{GES}	Gate-to-Emitter Leakage Current	—	—	± 100	nA	$V_{GE} = \pm 20V$

Switching Characteristics @ $T_J = 25^\circ\text{C}$ (unless otherwise specified)

	Parameter	Min.	Typ.	Max.	Units	Conditions
Q_g	Total Gate Charge (turn-on)	—	16	21	nC	$I_C = 9.0A, V_{CC} = 400V, V_{GE} = 15V$ See Fig. 8
Q_{ge}	Gate - Emitter Charge (turn-on)	—	2.4	3.4		
Q_{gc}	Gate - Collector Charge (turn-on)	—	7.8	10		
$t_{d(on)}$	Turn-On Delay Time	—	24	—	ns	$T_J = 25^\circ\text{C}$ $I_C = 9.0A, V_{CC} = 480V$ $V_{GE} = 15V, R_G = 50\Omega$ Energy losses include "tail"
t_r	Rise Time	—	13	—		
$t_{d(off)}$	Turn-Off Delay Time	—	160	270		
t_f	Fall Time	—	310	600	mJ	See Fig. 9, 10, 11, 14
E_{on}	Turn-On Switching Loss	—	0.18	—		
E_{off}	Turn-Off Switching Loss	—	0.90	—		
E_{ts}	Total Switching Loss	—	1.08	2.0	ns	$T_J = 150^\circ\text{C}$, $I_C = 9.0A, V_{CC} = 480V$ $V_{GE} = 15V, R_G = 50\Omega$ Energy losses include "tail"
$t_{d(on)}$	Turn-On Delay Time	—	25	—		
t_r	Rise Time	—	18	—		
$t_{d(off)}$	Turn-Off Delay Time	—	210	—		
t_f	Fall Time	—	600	—	mJ	See Fig. 10, 14
E_{ts}	Total Switching Loss	—	1.65	—		
L_E	Internal Emitter Inductance	—	7.5	—	nH	Measured 5mm from package
C_{ies}	Input Capacitance	—	340	—	pF	$V_{GE} = 0V, V_{CC} = 30V, f = 1.0MHz$ See Fig. 7
C_{oes}	Output Capacitance	—	63	—		
C_{res}	Reverse Transfer Capacitance	—	5.9	—		

Notes:

① Repetitive rating; $V_{GE}=20V$, pulse width limited by max. junction temperature. (See fig. 13b)

③ Repetitive rating; pulse width limited by maximum junction temperature.

⑤ Pulse width 5.0 μs , single shot.

② $V_{CC}=80\%(V_{CES}), V_{GE}=20V, L=10\mu H, R_G=50\Omega$, (See fig. 13a)

④ Pulse width $\leq 80\mu s$; duty factor $\leq 0.1\%$.

Philips Semiconductors

Data sheet	
status	Preliminary specification
date of issue	December 1990

2N2646

Silicon unijunction transistor

QUICK REFERENCE DATA


SYMBOL	PARAMETER	CONDITIONS	MIN.	TYP.	MAX.	UNIT
$-V_{EB2}$	emitter-base 2 voltage		-	-	30	V
I_{EM}	emitter current	peak value	-	-	2	A
P_{tot}	total power dissipation		-	-	300	mW
T_j	junction temperature		-	-	125	°C
R_{BB}	static inter-base resistance	$V_{EB1} = 3\text{ V}$ $I_E = 0$	-	7	-	kΩ
V_{EB1sat}	emitter-base 1 saturation voltage	$V_{EB1} = 10\text{ V}$ $I_E = 50\text{ mA}$	-	3.5	-	V
$I_{E(V)}$	emitter valley point current		4	6	-	mA
$I_{E(P)}$	emitter peak point current		-	1	5	μA

PINNING - TO-18

Base 2 connected to case.

PIN	DESCRIPTION
1	emitter
2	base 1
3	base 2

PIN CONFIGURATION

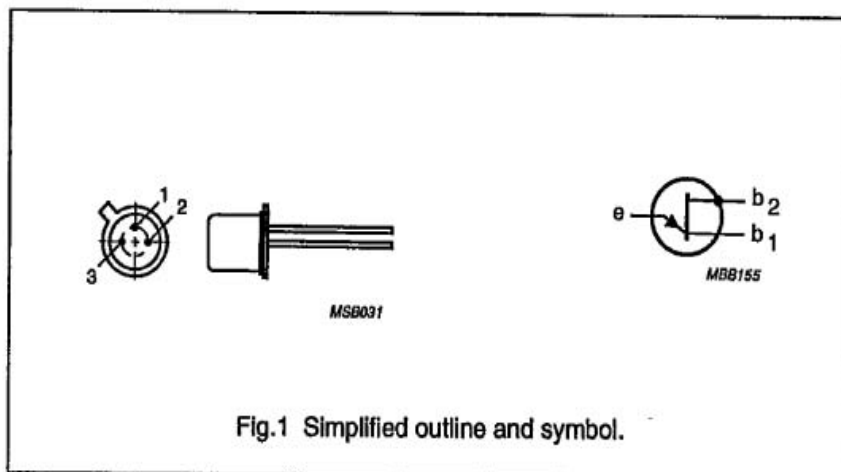

Silicon unijunction transistor

2N2646

CHARACTERISTICS

T_{amb} = 25 °C unless otherwise specified.

SYMBOL	PARAMETER	CONDITIONS	MIN.	TYP.	MAX.	UNIT
R _{BB}	static inter-base resistance	V _{B2B1} = 3 V I _E = 0	4.7	7	9.1	kΩ
TC _{RBB}	inter-base resistance temperature coefficient	V _{B2B1} = 3 V I _E = 0 T _{amb} = -55 to 125 °C	0.1	-	0.9	%/K
-I _{EB20}	emitter cut-off current	-V _{EB2} = 30 V I _{B1} = 0	-	-	12	V
V _{EB1sat}	emitter-base 1 saturation voltage	V _{B2B1} = 10 V I _E = 50 mA	-	3.5	-	V
I _{B2mod}	inter-base current modulation	V _{B2B1} = 10 V I _E = 50 mA	-	15	-	mA
η	input/output ratio (note 1)	V _{B2B1} = 10 V	0.56	-	0.75	
I _{E(V)}	emitter valley point current	V _{B2B1} = 20 V R _{B2} = 100 Ω	4	6	-	mA
I _{E(P)}	emitter peak point current	V _{B2B1} = 25 V	-	1	5	μA
V _{OB1M}	base 1 impulse/output voltage		3	5	-	V

Note

1. $\eta = \frac{(V_{E(P)} - V_{EB1})}{V_{B2B1}}$, when V_{E(P)} = emitter peak point voltage, V_{EB1} = emitter-base 1 breakdown voltage, (approximately 0.5 V at 10 μA), and V_{B2B1} = inter-base voltage.

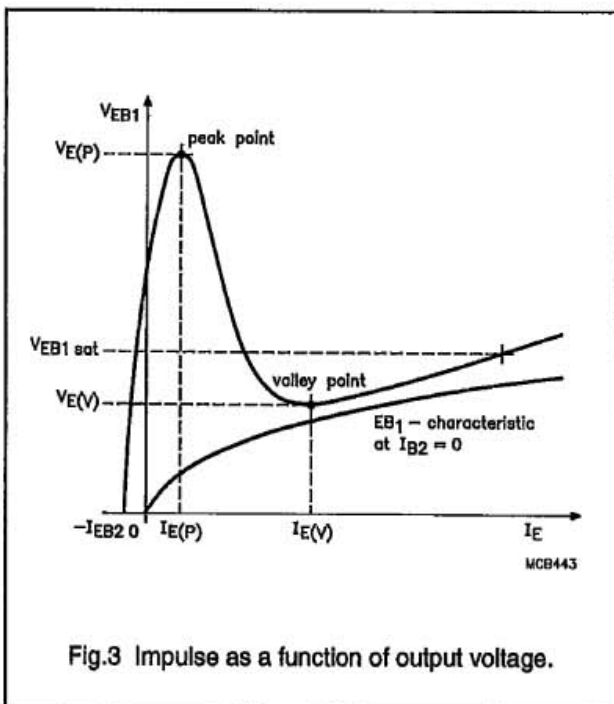


Fig.3 Impulse as a function of output voltage.

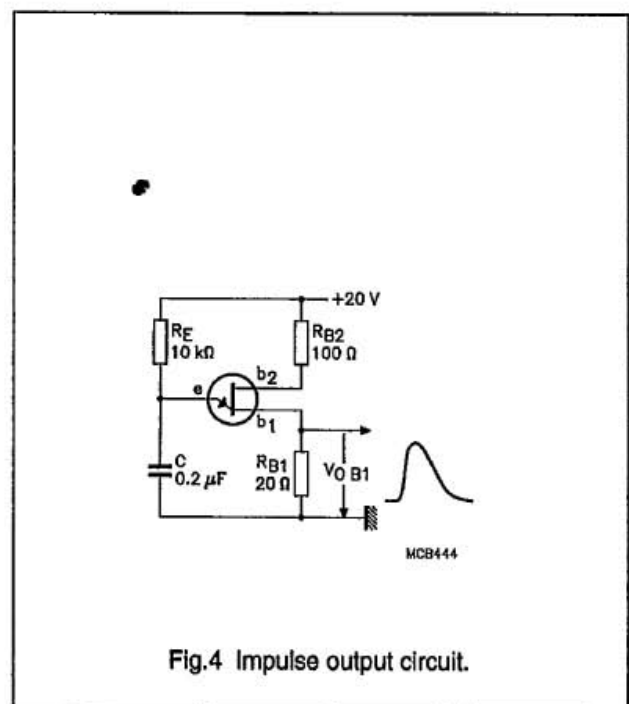


Fig.4 Impulse output circuit.

TRADEMARKS

The following are registered and unregistered trademarks Fairchild Semiconductor owns or is authorized to use and is not intended to be an exhaustive list of all such trademarks.

ACEx™	ISOPLANAR™
CoolFET™	MICROWIRE™
CROSSVOLT™	POP™
E ² CMOS™	PowerTrench™
FACT™	QS™
FACT Quiet Series™	Quiet Series™
FAST®	SuperSOT™-3
FASTr™	SuperSOT™-6
GTO™	SuperSOT™-8
HiSeC™	TinyLogic™

DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS.

LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF FAIRCHILD SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

PRODUCT STATUS DEFINITIONS**Definition of Terms**

Datasheet Identification	Product Status	Definition
Advance Information	Formative or In Design	This datasheet contains the design specifications for product development. Specifications may change in any manner without notice.
Preliminary	First Production	This datasheet contains preliminary data, and supplementary data will be published at a later date. Fairchild Semiconductor reserves the right to make changes at any time without notice in order to improve design.
No Identification Needed	Full Production	This datasheet contains final specifications. Fairchild Semiconductor reserves the right to make changes at any time without notice in order to improve design.
Obsolete	Not In Production	This datasheet contains specifications on a product that has been discontinued by Fairchild semiconductor. The datasheet is printed for reference information only.

