

Solved Problems in:

**ELECTRONIC DEVICES AND
CIRCUITS – 1**

By:

DR. NIZAR KASSAB

Academic Year 2005/2006

SOLVED PROBLEMS ON DIODES

1. A silicon diode, the forward resistance of which is 400 ohm, supplies power to a load resistance 1200 ohm from a 250 V (rms) mains. Calculate (i) the dc load current, (ii) the ac load current, (iii) the dc voltage across the diode, (iv) the dc output power, (v) the conversion efficiency, and (vi) the percentage regulation

Ans. As one silicon diode is employed, the circuit is a half-wave rectifier. The peak load current is

$$I_m = \frac{V_m}{R_f + R_L} = \frac{250\sqrt{2}}{400 + 1200} = 0.221 \text{ A}$$

(i) The dc load current is

$$I_{dc} = \frac{I_m}{\pi} = 0.0703 \text{ A}$$

(ii) The rms ac load current is

$$I_{rms} = (I_{rms}^2 - I_{dc}^2)^{1/2},$$

where I_{rms} = rms load current = $\frac{I_m}{2} = 0.1105 \text{ A}$

$$\text{Hence } I_{rms} = [(0.1105)^2 - (0.0703)^2]^{1/2} = 0.0854 \text{ A}$$

(iii) The dc voltage across the diode is

$$I_{dc} R_f = 0.0703 \times 400 = 28.1 \text{ V}$$

(iv) The dc output power is

$$P_{dc} = I_{dc}^2 R_L = (0.0703)^2 \times 1200 = 5.93 \text{ W}$$

(v) The conversion efficiency is

$$\eta = \frac{40.6}{1 + R_f/R_L} = \frac{40.6}{1 + 400/1200} = 40.6 \times \frac{3}{4} = 30.45 \text{ percent}$$

(vi) The percentage regulation is

$$\frac{V_{NL} - V_{RL}}{V_{RL}} \times 100 = \frac{I_{dc} R_f}{I_{dc} R_L} \times 100 = \frac{R_f}{R_L} \times 100 = 33.3\%$$

2. A full-wave rectifier uses a double-diode, the forward resistance of each element being 200 ohm. The rectifier supplies current to a load resistance of 1000 ohm. The primary-to-total secondary turns ratio of the centre-tapped transformer is 1 : 3. The transformer primary is fed from a supply of 240 V (rms). Find (i) the dc load current, (ii) the direct current in each diode, (iii) the dc power output, (iv) the ripple voltage across the load resistance, (v) the percentage regulation, and (vi) the efficiency of rectification.

Ans. The rms secondary voltage is $V_s = V_p/n$, where V_p is the rms primary voltage of the transformer and n is the primary-to-secondary turns ratio. Here $V_s = 24 \times 3 = 720$ V. The secondary voltage from the centre tap is $720/2 = 360$ V (rms). The corresponding peak voltage is $V_m = 360\sqrt{2} = 509$ V.

(i) The dc load current is $I_{dc} = 2 I_m/\pi$, where I_m is the peak current through the load resistance. We have

$$I_m = \frac{V_m}{R_f + R_L} = \frac{509}{200 + 1000} = 0.424 \text{ A.}$$

Hence $I_{dc} = \frac{2 I_m}{\pi} = \frac{2 \times 0.424}{3.14} = 0.27 \text{ A.}$

(ii) The direct current supplied by each diode is $I_{dc}/2 = 0.135 \text{ A}$

(iii) The dc power output is $P_{dc} = I_{dc}^2 R_L = (0.27)^2 \times 1000 = 72.9 \text{ W}$

(iv) The ripple voltage across the load is $I_{rms} R_L = (I_{rms}^2 - I_{dc}^2)^{1/2} R_L$.

Here $I_{rms} = I_m/\sqrt{2} = 0.424/\sqrt{2} = 0.3 \text{ A}$

So, $I_{rms} R_L = (0.3^2 - 0.27^2)^{1/2} \times 1000 = 130.8 \text{ V}$

(v) The percentage regulation is $\frac{R_f}{R_L} \times 100 = \frac{200}{1000} \times 100 = 20\%$

(vi) The efficiency of rectification is

$$\frac{81.2}{1 + R_f/R_L} = \frac{81.2}{1.2} = 67.7\%$$

3. A bridge rectifier feeds a load resistance of 2500Ω from a 100 V (rms) supply. Each diode of the rectifier has a forward resistance of 50Ω . Calculate (i) the dc load voltage, (ii) the ripple voltage at the output, and (iii) the percentage regulation.

Ans. (i) The bridge circuit gives full-wave rectification. So, the dc load current is $I_{dc} = 2 I_m/\pi$, where I_m is the peak load current. Since two diodes in series conduct simultaneously, we have

$$I_m = \frac{V_m}{2 R_f + R_L} = \frac{100\sqrt{2}}{2 \times 50 + 2500} = 0.0544 \text{ A.}$$

Therefore,
$$I_{dc} = \frac{2 I_m}{\pi} = 0.0346 \text{ A}$$

The dc load voltage is $V_{dc} = I_{dc} \times R_L = 0.0346 \times 2500 = 86.5 \text{ V}$.

(ii) The ripple voltage at the output is

$$I_{rms} R_L = (I_{rms}^2 - I_{dc}^2)^{1/2} R_L.$$

Here,
$$I_{rms} = I_m / \sqrt{2} = 0.0385 \text{ A}$$

Hence,
$$I_{rms} R_L = (0.0385^2 - 0.0346^2)^{1/2} \times 2500 = 43.3 \text{ V}$$

(iii) The percentage regulation is

$$\frac{2 R_f}{R_L} \times 100 = \frac{2 \times 50}{2500} \times 100 = 4\%$$

4. In the circuit of Fig. 5.11, the supply voltage is $V = 15$ volt. The 12 V , 0.36 W Zener diode operates at a minimum diode current of 2 mA . Calculate the series resistance R and the range over which the load resistance R_L can be varied.

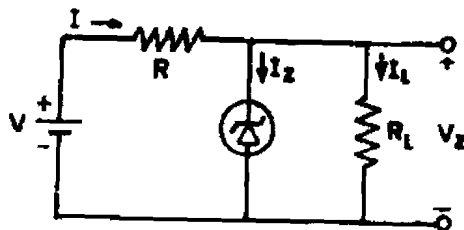


Fig. 5.11

Ans. The maximum allowable Zener current is $\frac{0.36 \text{ W}}{12 \text{ V}} = 0.03 \text{ A} = 30 \text{ mA}$. If the load resistance R_L is infinite, the Zener current I_z attains its maximum value of $I = 30 \text{ mA}$. The voltage drop across the series resistance R is $V_R = V - V_Z = 15 - 12 = 3$ volt. Since the current through R is $I = 30 \text{ mA} = 30 \times 10^{-3} \text{ A}$, we have

$$R = \frac{V_R}{I} = \frac{3}{30 \times 10^{-3}} = 100 \text{ ohm}.$$

As R_L is decreased, the current I_L through it increases and the Zener current I_Z decreases correspondingly, since $I_L + I_Z = I = 30$ mA.

For the minimum value R_{Lm} of R_L , the Zener current I_Z attains its minimum value of 2 mA.

Hence,
$$I_L = 30 - 2 = 28 \text{ mA} .$$

Therefore,
$$R_{Lm} = \frac{12 \text{ volt}}{28 \text{ mA}} = 428.6 \text{ ohm} .$$

Hence the allowable range of variation of R_L is $428.6 \Omega \leq R_L < \infty$.

5. In the circuit of Fig.5.11, the Zener diode has the same specification as in problem 4. In the circuit, $R = 100 \Omega$ and $R_L = 1 \text{ k}\Omega$. Determine the limits between which the supply voltage V can vary without loss of regulation in the circuit.

(cf. C.U. 2001)

Ans. When V is a minimum, the Zener current I_Z attains its minimum value of 2 mA. The load current is $I_L = 12 \text{ volt}/1 \text{ k}\Omega = 12$ mA. Hence the minimum allowable value of I is $12 + 2 = 14$ mA. The corresponding voltage drop across R is $V_R = IR = 14 \times 10^{-3} \times 100 = 1.4$ volt. Thus the minimum value of V is

$$V_{\min} = V_Z + V_R = 12 + 1.4 = 13.4 \text{ volt} .$$

At the maximum value V_{\max} of V , the Zener current becomes a maximum, i.e. 30 mA. Now $I = 30 + 12 = 42$ mA and $V_R = 42 \times 10^{-3} \times 100 = 4.2$ volt. Therefore,

$$V_{\max} = 4.2 + 12 = 16.2 \text{ volt} .$$

So, V can vary between 13.4 volt and 16.2 volt.

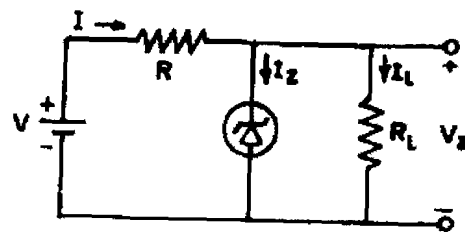


Fig. 5.11

Ans. As one silicon diode is employed, the circuit is a half-wave rectifier. The peak load current is

$$I_m = \frac{V_m}{R_f + R_L} = \frac{250\sqrt{2}}{400 + 1200} = 0.221 \text{ A}$$

(i) The dc load current is

$$I_{dc} = \frac{I_m}{\pi} = 0.0703 \text{ A}$$

(ii) The rms ac load current is

$$I'_{rms} = (I_{rms}^2 - I_{dc}^2)^{1/2},$$

where $I_{rms} = \text{rms load current} = \frac{I_m}{2} = 0.1105 \text{ A}$

Hence $I'_{rms} = [(0.1105)^2 - (0.0703)^2]^{1/2} = 0.0854 \text{ A}$

(iii) The dc voltage across the diode is

$$I_{dc} R_f = 0.0703 \times 400 = 28.1 \text{ V}$$

(iv) The dc output power is

$$P_{dc} = I_{dc}^2 R_L = (0.0703)^2 \times 1200 = 5.93 \text{ W}$$

(v) The conversion efficiency is

$$\eta = \frac{40.6}{1 + R_f/R_L} = \frac{40.6}{1 + 400/1200} = 40.6 \times \frac{3}{4} = 30.45 \text{ percent}$$

(vi) The percentage regulation is

$$\frac{V_{NL} - V_{RL}}{V_{RL}} \times 100 = \frac{I_{dc} R_f}{I_{dc} R_L} \times 100 = \frac{R_f}{R_L} \times 100 = 33.3\%$$

BJT Solved Problems

1. A Transistor having $\alpha = 0.99$ is used in a common-base amplifier. If the load resistance is $4.5 \text{ k } \Omega$ and the dynamic resistance of the emitter junction is $50 \text{ } \Omega$. Find the voltage gain and the power gain.

Ans. The voltage gain is

$$A_v = \alpha \frac{R_L}{r_e}$$

Here $\alpha = 0.99$, $R_L = 4.5 \text{ k } \Omega = 4500 \text{ } \Omega$, and $r_e = 50 \text{ } \Omega$.

Hence
$$A_v = 0.99 \times \frac{4500}{50} = 89.1.$$

The power gain is

$$\begin{aligned} A_p &= \text{current gain} \times \text{voltage gain} \\ &= 0.99 \times 89.1 = 88.2. \end{aligned}$$

2. An $n-p-n$ transistor with $\alpha = 0.98$ is operated in the CB configuration. If the emitter current is 3 mA and the reverse saturation current is $I_{CO} = 10 \text{ } \mu\text{A}$, what are the base current and the collector current?

Ans. The collector current I_C for an emitter current I_E is given by

$$I_C = -\alpha I_E + I_{CO}$$

For an $n-p-n$ transistor, I_E is negative. Therefore,

$$I_C = \alpha I_E + I_{CO}$$

Since $\alpha = 0.98$, $I_E = 3 \text{ mA}$, and $I_{CO} = 10 \text{ } \mu\text{A} = 10 \times 10^{-3} \text{ mA}$, we have

$$\begin{aligned} I_C &= 0.98 \times 3 + 10^{-2} \\ &= 2.95 \text{ mA}. \end{aligned}$$

Also, from Kirchhoff's current law,

$$I_E + I_C + I_B = 0$$

For an $n-p-n$ transistor, I_E is negative. Hence

$$-I_E + I_C + I_B = 0$$

or,
$$I_B = I_E - I_C = 3 - 2.95 = 0.05 \text{ mA} = 50 \text{ } \mu\text{A}.$$

3. A transistor having $\alpha = 0.975$ and a reverse saturation current $I_{CO} = 10 \text{ } \mu\text{A}$, is operated in CE configuration. What is β for this configuration? If the base current is $250 \text{ } \mu\text{A}$, calculate the emitter current and the collector current.

Ans. We have

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.975}{0.025} = 39.$$

Also, the collector current is

$$\begin{aligned} I_C &= \beta I_B + (\beta+1)I_{CO} \\ &= 39 \times 0.25 + (39 + 1) \times 0.01 \text{ mA} \\ &= 10.2 \text{ mA} \end{aligned}$$

Since
$$\alpha = \left| \frac{I_C - I_{CO}}{I_E} \right|,$$

we have
$$0.975 = \frac{10.2 - 0.01}{I_E}$$

whence $I_E = 10.4 \text{ mA}$.

4. A transistor is operating in the CE mode (Fig. 7.16). Calculate V_{CE} if $\beta = 125$, assuming $V_{BE} = 0.6 \text{ V}$. (cf. C.U. 1991)

Ans. When $V_{BE} = 0.6 \text{ V}$, the base current is

$$\begin{aligned} I_B &= \frac{10 - V_{BE}}{310 \text{ k}\Omega} = \frac{10 - 0.6}{310} \text{ mA} \\ &= 0.0303 \text{ mA} \end{aligned}$$

Now, $\beta = 125$. Therefore, $I_C = \beta I_B = 125 \times 0.0303 \text{ mA}$

$$= 3.79 \text{ mA} = 3.79 \times 10^{-3} \text{ A}.$$

Again $V_{CE} = 20 - I_C \times 5 \times 10^3 \text{ V}$

$$= 20 - 3.79 \times 5 = 1.05 \text{ V}.$$

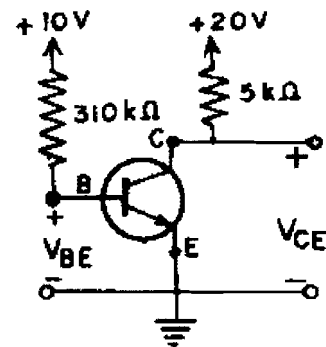


Fig. 7.16. Figure for Problem 4

5. A silicon $n-p-n$ transistor having $\beta = 100$ and $I_{CO} = 22 \text{ nA}$ is operated in the CE configuration (Fig. 7.17). Assuming $V_{BE} = 0.7 \text{ V}$, determine the transistor

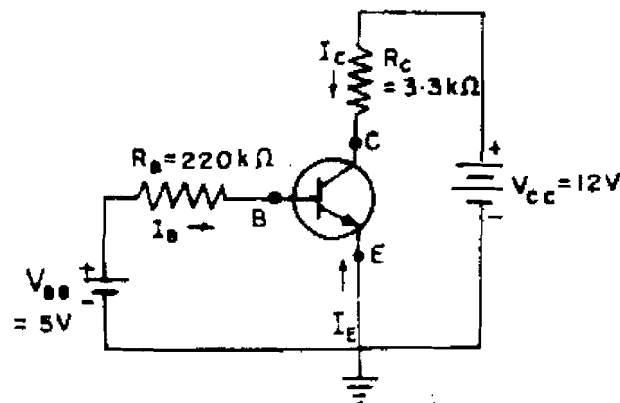


Fig. 7.17 Figure for Problem 5

currents and the region of operation of the transistor. What happens if the resistance R_C is indefinitely increased? (cf. C.U. 1994)

Ans. Since the base is forward-biased, the transistor is not cutoff. So it is either in the active region or in the saturation region.

Let us assume that the transistor is in the active region. Application of Kirchhoff's voltage law to the base circuit gives

$$I_B R_B + V_{BE} = V_{BB}$$

$$\text{or, } I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 - 0.7}{220} \text{ mA} = 0.0195 \text{ mA}$$

$$= 19.5 \mu\text{A.}$$

Here $I_{CQ} \ll I_B$. Therefore,

$$I_C \approx \beta I_B = 100 \times 19.5 \times 10^{-3} \text{ mA} = 1.95 \text{ mA.}$$

To justify the assumption that the transistor operates in the active region, we must show that the collector junction is reverse-biased. Applying Kirchhoff's voltage law to the collector circuit, we get

$$I_C R_C + V_{CB} + V_{BE} = V_{CC}$$

$$\text{or, } V_{CB} = V_{CC} - I_C R_C - V_{BE}$$

$$= 12 - 1.95 \times 3.3 - 0.7$$

$$= 4.86 \text{ V.}$$

A positive value of V_{CB} implies that for the $n-p-n$ transistor, the collector junction is reverse-biased. Therefore, the transistor is actually in the active region.

The emitter current is

$$I_E = -(I_C + I_B) = -(1.95 + 0.0195) \text{ mA}$$

$$= -1.97 \text{ mA.}$$

The negative sign indicates that I_E actually flows in the direction opposite to the arrowhead shown in Fig. 7.17.

In the active region, I_B and I_C do not depend on the collector circuit resistance R_C . So, if R_C is gradually increased, we see from the collector circuit equation that at one stage V_{CB} becomes negative. The transistor is then no longer in the active region; it goes over to the saturation region.

6. Refer to the circuit of Fig. 7.18. At saturation, V_{BE} and V_{CE} are $V_{BE, sat} = 0.85$ V and $V_{CE, sat} = 0.22$ V. If $h_{FE} = 110$, is the transistor operating in the saturation region? (cf. C.U. 1998)

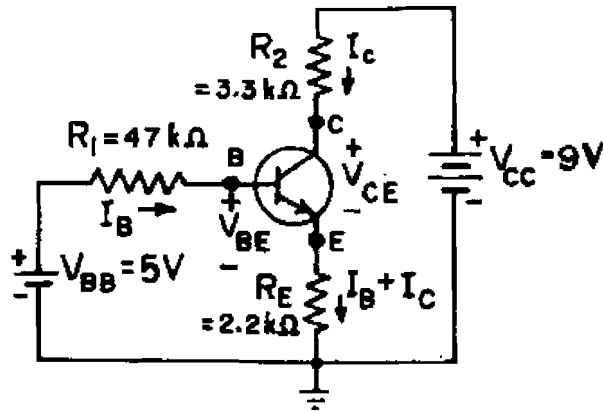


Fig. 7.18 Figure for Problem 6

Ans. Let us assume that the transistor operates in the saturation region. Applying Kirchhoff's voltage law to the base circuit we get

$$R_1 I_B + V_{BE} + R_E (I_C + I_B) = V_{BB} \quad (i)$$

Applying the same to the collector circuit we obtain

$$R_2 I_C + V_{CE} + R_E (I_C + I_B) = V_{CC} \quad (ii)$$

Substituting the numerical values, expressing I_B and I_C in mA, and rearranging, (i) and (ii) are written as

$$49.2 I_B + 2.2 I_C = 4.15. \quad (iii)$$

and $2.2 I_B + 5.5 I_C = 8.78. \quad (iv)$

Solving (iii) and (iv) for I_B and I_C gives

$$I_B = 0.0132 \text{ mA}, I_C = 1.591 \text{ mA}.$$

The minimum base current required for saturation is

$$(I_B)_{\min} = \frac{I_C}{h_{FE}} = \frac{1.591}{110} = 0.0145 \text{ mA}.$$

Since $I_B = 0.0132 \text{ mA}$, $I_B < (I_B)_{\min}$. So, the transistor is not in the saturation region,. It must be in the active region.

7. A transistor operating in the CE mode draws a constant base current I_B of $30 \mu\text{A}$. The collector current I_C is found to change from 3.5 mA to 3.7 mA when the collector-emitter voltage V_{CE} changes from 7.5 V to 12.5 V . Calculate the output resistance and β at $V_{CE} = 12.5 \text{ V}$. What is the value of α ?

Ans: The change in the collector current is $\Delta I_C = 3.7 - 3.5 = 0.2 \text{ mA}$. The corresponding change in the collector-emitter voltage is $\Delta V_{CE} = 12.5 - 7.5 = 5 \text{ V}$.

So, the output resistance is $\frac{\Delta V_{CE}}{\Delta I_C} = \frac{5}{0.2 \times 10^{-3}} \Omega = 25 \text{ k}\Omega$

Since the base current is $I_B = 30 \mu\text{A} = 0.03 \text{ mA}$,

we have $\beta = \frac{I_C}{I_B} = \frac{3.7}{0.03} = 123.3$

Also, $\beta = \frac{\alpha}{1 - \alpha}$, so that $\alpha = \frac{\beta}{\beta + 1} = \frac{123.3}{124.3} = 0.992$.

8. In the circuit of Fig. 7.19, the transistors Q_1 and Q_2 have $\beta = 100$. The Zener diode voltage is $V_Z = 4 \text{ V}$. Given, $I_L = 2 \text{ mA}$, $I_Z = 5 \text{ mA}$, $V_{EB1} = V_{EB2} = 0.7 \text{ V}$. Find R_1 , R_2 , and the range of R_L for Q_1 to remain in the active region. (GATE 2001)

Ans. Let I_E and I_B be the emitter and the base currents, respectively, of Q_1 . Since I_L is the collector current of Q_1 , we have $I_B = I_L/\beta = 2/100 = 0.02 \text{ mA}$.

Also, $I_E = I_B + I_L = 0.02 + 2 = 2.02 \text{ mA}$.

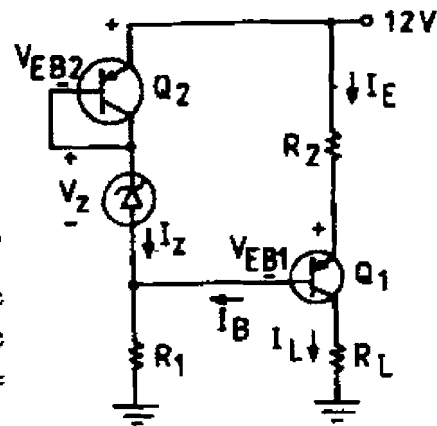


Fig. 7.19 Figure for Problem 8.

If V_{R1} is the voltage drop across R_1 , we obtain

$$V_{R1} = 12 - V_{EB2} - V_Z = 12 - 0.7 - 4 = 7.3 \text{ V}$$

The resistance R_1 is

$$R_1 = \frac{V_{R1}}{I_B + I_Z} = \frac{7.3}{0.02 + 5} = \frac{7.3}{5.02} = 1.45 \text{ k}\Omega,$$

The voltage drop across R_2 is

$$V_{R2} = V_{EB2} + V_Z - V_{EB1} = 4 \text{ V}.$$

$$\text{So, } R_2 = \frac{V_{R2}}{I_E} = \frac{4}{2.02} = 1.98 \text{ k}\Omega$$

The base-collector voltage drop for Q_1 is

$$V_{BC} = 12 - V_{R2} - V_{EB1} - I_L R_L = 7.3 - 2R_L$$

where R_L is in $\text{k}\Omega$. For Q_1 to remain in the active region, $V_{BC} \geq 0$. i.e.,

$$R_L \leq \frac{7.3}{2} \text{ k}\Omega, \text{ or } R_L \leq 3.65 \text{ k}\Omega. \text{ So, } 0 \leq R_L \leq 3.65 \text{ k}\Omega.$$

SBLIMENTARY PROBLEMS on BJT

1. For a $p-n-p$ transistor in CE mode, $\beta = 100$. What is the value of α ? If $I_{CO} = 10 \mu A$, what is the collector current for an emitter current of 2 mA?
(Ans. 0.99, 1.99 mA)
2. If $\beta = 16.5$, $I_E = 1.8$ mA and $I_{CO} = 12 \mu A$, calculate I_C and I_B when the transistor is used in the CE configuration. (Ans. 1.71 mA, 90 μA)
3. For a $p-n-p$ transistor operating in CE configuration, it is found that when V_{CE} is kept at -20 V, a change in the base current from 100 to 150 μA causes a change in the collection current from 2 to 3.8 mA. Find h_{fe} .
(Ans. 36)
4. A silicon $n-p-n$ transistor with $\alpha = 0.995$ and $I_{CO} = 15$ nA, operates in the CE configuration. What is the collector current for a base current of 20 μA ?
(Ans. 3.983 mA)
5. A $p-n-p$ transistor working in the CB mode has an input dynamic resistance of 50 Ω . The current gain on the amplifier is 0.98 and the load resistance in the collector circuit is 3 k Ω . Calculate the voltage gain and the power gain.
(cf. C.U. 1993) (Ans. 58.8, 57.6)
6. An $n-p-n$ transistor with $\alpha = 0.96$ and negligible I_{CO} carries a base current of 0.2 mA in the active region. Determine the emitter and the collector currents.
(Ans. 5mA, 4.8 mA)
7. For a transistor, $I_C = 7$ mA, $I_{CO} = 25 \mu A$ and $I_B = 0.1$ mA. Calculate α , β and I_E .
(Ans. 0.98, 49, 7.1 mA)

8. For the transistor in Fig. 7.20, $\beta = 100$ and the values of V_{BE} and V_{CE} at saturation are $V_{BE,sat} = 0.8 \text{ V}$ and $V_{CE,sat} = 0.2 \text{ V}$. What is the minimum value of R_2 for the transistor to operate in the saturation region? (Ans. $5.13 \text{ k}\Omega$)

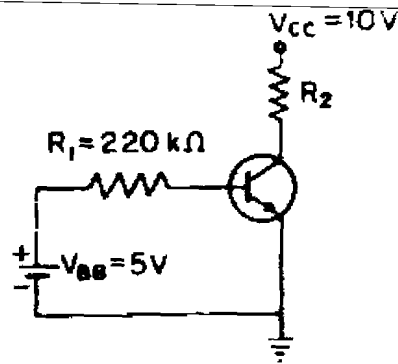


Fig. 7.20 Figure for problem 8

9. Consider an $n-p-n$ transistor in the CE configuration with negligible I_{CO} . Given: $\beta = 50$, $V_{BB} = 4\text{V}$, $R_B = 100 \text{ k}\Omega$, $R_C = 4 \text{ k}\Omega$ and $V_{CC} = 10\text{V}$. Draw the circuit diagram. Calculate the currents I_B and I_C , assuming $V_{BE} = 0.7 \text{ V}$ in the active region. Find the value of R_C for which the transistor will no longer be in the active region.

(C.U. 1991)

(Ans. $33\mu\text{A}$, 1.65 mA , $5.64 \text{ k}\Omega$)

10. Draw the circuit diagram of a common-emitter $n-p-n$ transistor with the following parameters: $V_{BB} = 5 \text{ V}$, $R_B = 100 \text{ k}\Omega$, $R_C = 1 \text{ k}\Omega$, $V_{CC} = 10 \text{ V}$, $V_{BE} = 0.7 \text{ V}$, $I_{CO} = 0$, and $h_{FE} = 100$. Find I_B and I_C . Is the transistor operating in the saturation region?

(C.U. 1993) (Ans. $43 \mu\text{A}$, 4.3 mA , No.)

11. Calculate β of a transistor for which $\alpha = 0.95$. If α changes by 0.1% , what is the per cent change in β ? (Ans. $19, 2\%$)

12. In the circuit of Fig. 7.18, $V_{BB} = 3\text{V}$, $R_1 = 7\text{k}\Omega$, $R_E = 500 \Omega$, $R_2 = 3\text{k}\Omega$ and $V_{CC} = 10\text{V}$. Assume $\beta = h_{FE} = 100$. (i) Determine if the Si transistor is in cutoff, saturation or in the active region. (ii) Calculate the voltage V_0 between the collector C and ground. (iii) Obtain the minimum value of R_E for which the transistor is in the active region. (cf. C.U. 1997)


[Hint. (i) Take $V_{BE,sat} = 0.8\text{V}$ and $V_{CE,sat} = 0.2 \text{ V}$. Assume that the transistor is in saturation and proceed as in worked-out problem no. 6 (Sec. 7.13). (ii) Note that $V_0 = V_{CC} - I_C R_2$. (iii) At the cross-over to the active region, take $V_{CB} = 0$ and $V_{BE} = 0.8\text{V}$. Write Kirchhoff's voltage law equations for the base and collector circuits and solve for R_E taking $I_C = \beta I_B$.] (Ans. saturation, 1.66V , 842Ω)

13. A transistor in the CE configuration is connected with a power supply. The voltage drop across a $5 \text{ k}\Omega$ resistance connected in the collector circuit is 5V . Find the base current. (Given, $\alpha = 0.998$).


(C.U. 2000) (Ans. $2.004 \mu\text{A}$)

Devices-1, Quiz (4)

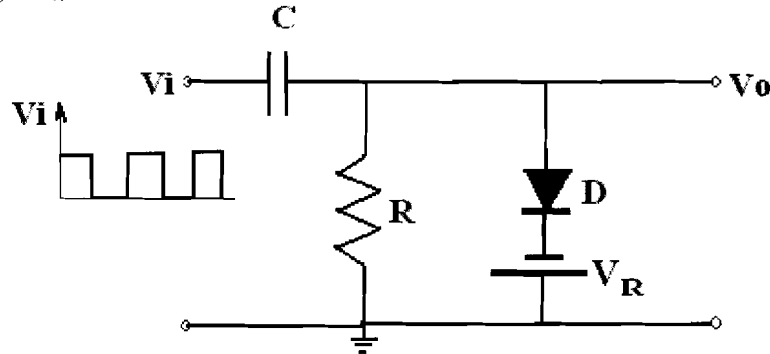1. Draw the full wave voltage-doubler circuit and explain how it works.
2. For the clamping circuit, shown below, if the input wave form is rectangular of peak voltage value of 55 volts; draw the output waveform for
 - a) $V_R = 0V$
 - b) $V_R = 5V$



3. A sinusoidal wave of 12 volts peak is applied to the clipping circuit shown below (fig.2) providing that $V_{R1} = 6V$ and $V_{R2} = 4V$ plot the output wave form against time.

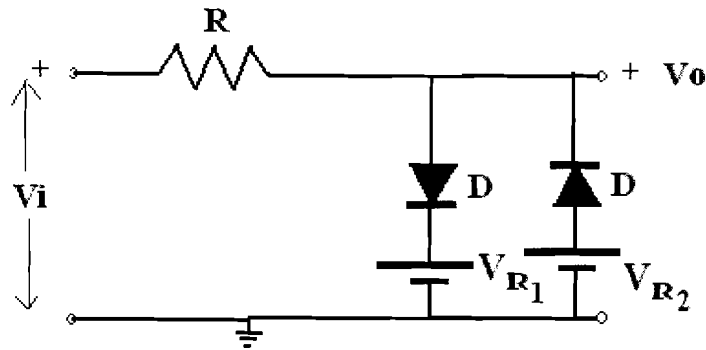

(Fig. 2)

Name	
I.D#	

AJMAN UNIVERSITY OF SCIENCE & TECHNOLOGY
 Faculty of Engineering
 Quiz Test-1, First Semester 2005/6
 Electronic Devices & Circuits (I) #211212

A. Chose the correct answer in the following:

1. The depletion layer width of p-n junction **increases/decreases** when the junction is reverse-biased.
2. The load line of the triode valve defines the amplification working area above the line (**True / False**).
3. In the p-n junction the depletion layer
 - (a) contains electrons
 - (b) contains no electrons or holes
 - (c) occurs in the N-zone
 - (d) occurs in the P-zone

Using the complex model, Determine the reverse voltage in the circuit Fig.1 below, Assume $I_r = 1\mu\text{A}$: (a) 6.3 V (b) 6996.5 mV (c) 7000 mV (d) 3.5 mV

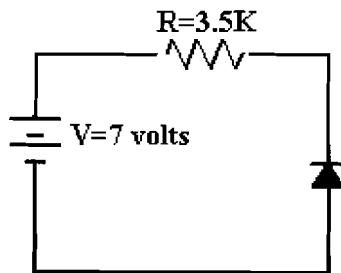


Fig.1

4. If a voltage signal of the waveform shown below, Fig.2, is applied to the input of a half-wave rectifier then the output DC component is:

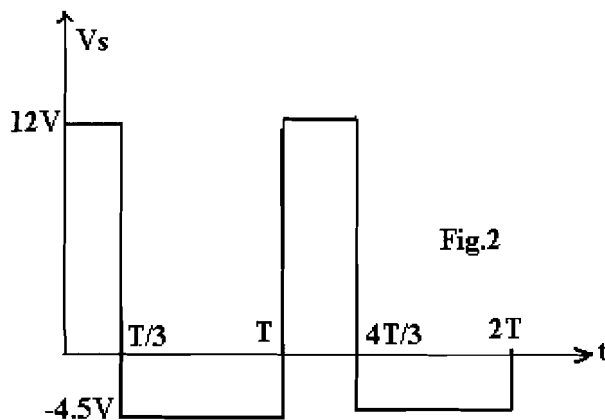


Fig.2

- (a) 4 V (b) 36 V (c) -1.5 V (d) 8 V
5. In the circuit, Fig.3, if $V_z = 200\text{V}$, $V_i = 260\text{V}$, and $P_{\max} = 4\text{W}$, the value of R_s will be (minimum specified zener current = 5 mA):

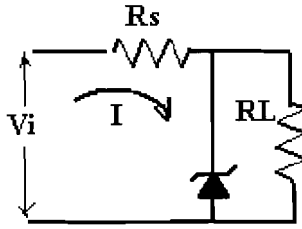


Fig. 3

- (a) $6\text{ K}\Omega$ (b) $12\text{ K}\Omega$ (c) $3\text{ K}\Omega$ (d) $5\text{ K}\Omega$

6. The input resistance of a triode valve is large because -----
 7. The cathode of a Zener diode in a voltage regulator is normally:
 a) more positive than the anode,
 b) more negative than the anode,
 c) at 0.7 V ,
 d) grounded

B. Solve TWO of the following problems:

1. Complete the following rectifying table:

Spec. Rectifying Descriptions	Half-Wave	Full-Wave (C.T)	Full-Wave (Bridge)
Number of Diodes	1	-----	-----
Vdc	-----	$0.637 V_p$	-----
The Diode PIV	-----	-----	V_p
Frequency of Output	input freq. f	-----	$2f$

2. Sketch the output waveforms expected when 100 Hz sine wave (10 V_p) is applied to each of the shown in the (Fig.4):

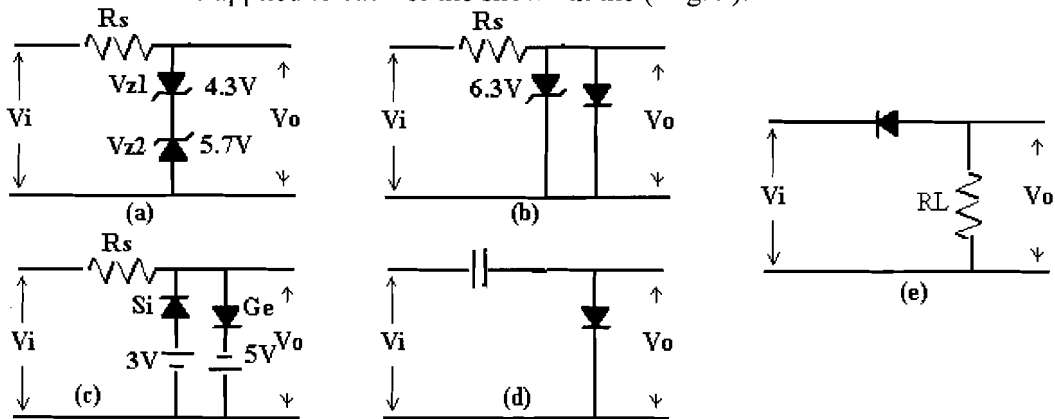


Fig. (4)

3. In the circuit, of Fig. (5), the supply voltage $V=15\text{V}$, the zener diode operates at $V_z = 12\text{ volts}$, $P_{\text{Max}} = 0.36\text{ watts}$ and minimum diode current of 2 mA . Calculate:
 a) The series resistance R , and
 b) The range over which the load resistance R_L varies (i.e. $R_{L(\text{max})}$ and $R_{L(\text{min})}$).

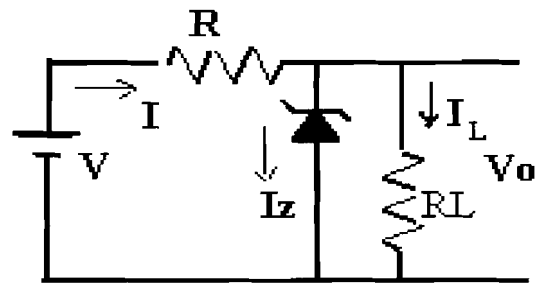


Fig.5

4. For a certain triode the anode current is expressed as:

$$I_p = 8.5 \times 10^{-5} (18 v_g + v_p) \text{ amps.}$$

Where v_p & v_g are the grid and plate voltage in volts respectively. With the operating point at $V_G = -6 \text{ V}$ and $V_P = 208 \text{ V}$, determine: I_p , r_p , g_m and μ .