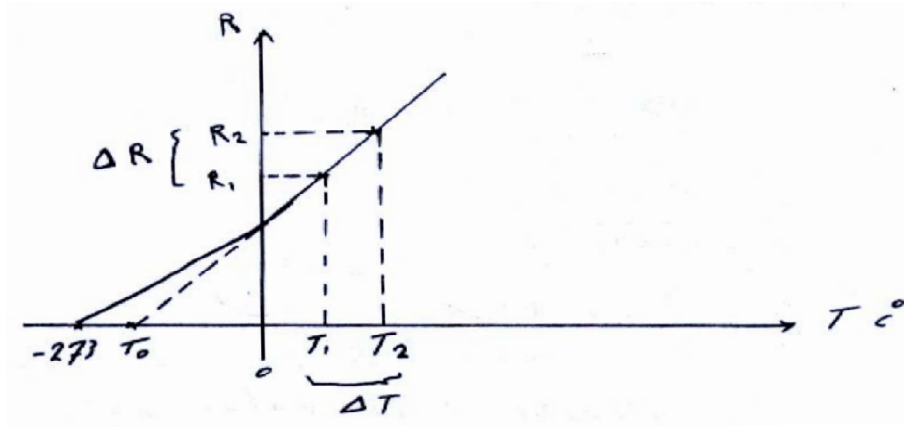


Continue → The Effect of Temperature

$$\text{slop} = \frac{\Delta R}{\Delta T} = \text{constant} = \frac{R_2 - R_1}{T_2 - T_1} = \frac{R_2 - R}{T_2 - T} = \frac{R - R_1}{T - T_1}$$

Example: The resistance of material is 300Ω at 10°C , and 400Ω at 60°C . Find its resistance at 50°C ?

Solution:

$$\text{slop} = \frac{R_2 - R_1}{T_2 - T_1} = \frac{400 - 300}{60 - 10} = 2 \Omega / ^\circ\text{C}$$

$$2 = \frac{R - R_1}{T - T_1} = \frac{R - 300}{50 - 10} = \frac{R - 300}{40}$$

$$R - 300 = 80 \Rightarrow R = 80 + 300 \Rightarrow R = 380 \Omega$$

Also from the above figure we can see

$$\frac{R_2 - 0}{T_2 - T_0} = \frac{R_1 - 0}{T_1 - T_0}$$

$$\frac{R_2}{T_2 - T_0} = \frac{R_1}{T_1 - T_0}$$

$$\therefore \frac{R_2}{R_1} = \frac{T_2 - T_0}{T_1 - T_0}, \text{ hence } \frac{\rho_2 \frac{\ell}{A}}{\rho_1 \frac{\ell}{A}} = \frac{T_2 - T_0}{T_1 - T_0} \Rightarrow \frac{\rho_2}{\rho_1} = \frac{T_2 - T_0}{T_1 - T_0}$$

E-Eng. Fundamentals

Example: Aluminum conductor with length of 75 cm and 1.5 mm^2 cross section area. Find its resistance at 90 C° ?

Solution:

$$R = \frac{\rho \ell}{A} = \frac{(2.83 \times 10^{-8}) \times (75 \times 10^{-2})}{1.5 \times 10^{-6}}$$

$$= 2.83 \times 50 \times 10^{-4} = 141.5 \times 10^{-4} = 14.15 \text{ m}\Omega$$

$$\frac{R_2}{R_1} = \frac{T_2 - T_0}{T_1 - T_0}$$

$$R_2 = 14.15 \left[\frac{90 - (-236)}{20 - (-236)} \right]$$

$$= 14.15 \left[\frac{90 + 236}{20 + 236} \right] = 18 \text{ m}\Omega.$$

Another method

$$\frac{\rho_2}{\rho_1} = \frac{T_2 - T_0}{T_1 - T_0} \Rightarrow \rho_{90} = \rho_{20} \left(\frac{90 + 236}{20 + 236} \right)$$

$$R = \frac{\rho_{90} \ell}{A} = \frac{\rho_{20} \left(\frac{90 + 236}{20 + 236} \right) \times (75 \times 10^{-2})}{1.5 \times 10^{-6}}$$

$$\rho_{20} = 2.83 \times 10^{-8}$$

$$\therefore \rho_{90} = 14.15 \text{ m}\Omega$$

Deriving the temperature coefficient

It can be started by using the previous relationship of the resistance and temperature

$$\begin{aligned} \frac{R_2}{R_1} &= \frac{T_2 - T_0}{T_1 - T_0} \\ R_2 &= R_1 \left(\frac{T_2 - T_0}{T_1 - T_0} \right) \\ R_2 &= R_1 \left(\frac{T_2 - T_0}{T_1 - T_0} + 1 - 1 \right) \\ R_2 &= R_1 \left(1 + \frac{T_2 - T_0}{T_1 - T_0} - 1 \right) \\ R_2 &= R_1 \left(1 + \frac{T_2 - T_0 - (T_1 - T_0)}{T_1 - T_0} \right) \\ R_2 &= R_1 \left(1 + \frac{T_2 - T_1}{T_1 - T_0} \right) \\ R_2 &= R_1 \left[1 + \left(\frac{1}{T_1 - T_0} \right) (T_2 - T_1) \right] \end{aligned}$$

Let $\alpha_1 = \frac{1}{T_1 - T_0}$ temperature coefficient of resistance at a temperature T_1

$$\therefore R_2 = R_1 [1 + \alpha_1 (T_2 - T_1)]$$

Where T_0 for copper = -234.5

In some resource, T_0 take an absolute value, which means $|T_0| = 234.5$, hence

we can sca

$$\alpha_1 = \frac{1}{|T_0| + T_1} \quad \& \quad \frac{R_2}{R_1} = \frac{|T_0| + T_2}{|T_0| + T_1}$$

Example:

- Find the value of α_1 at ($T_1 = 40 \text{ C}^\circ$) for copper wire.
- Using the result of (a), find the resistance of a copper wire at 75 C° if its resistance is 30Ω at 40 C° ?

Solution:

$$a) \quad \alpha_1 = \frac{1}{T_1 - T_0} = \frac{1}{40 - (-234.5)} = \frac{1}{274.5} = 0.00364 \quad 1/K$$

$$\text{Or} \quad \alpha_1 = \frac{1}{|T| + T_1} = \frac{1}{234.5 + 40} = \frac{1}{274.5} = 0.00364 \quad 1/K$$

$$b) \quad R_2 = R_1[1 + \alpha_1(T_2 - T_1)] \\ = 30[1 + 0.00364(75 - 40)] = 33.8\Omega$$

Exercise/ A coil has a resistance of 18 Ohm when its mean temperature is 20°C and of 20 Ohm temperature is 50°C. Find its mean temperature rise when its resistance is 21 Ohm and the surrounding temperature is 15° C.

OHM'S LAW


Consider the following relationship:

$$\text{Effect} = \frac{\text{cause}}{\text{opposition}}$$

Every conversion of energy from one form to another can be related to this equation. In electric circuits, the *effect* we are trying to establish is the flow of charge, or *current*. The *potential difference*, or voltage, between two points is the *cause* ("pressure"), and the opposition is the *resistance* encountered.

when its mean
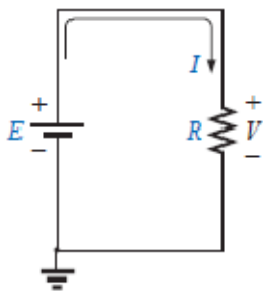
$$\text{Current} = \frac{\text{potential difference}}{\text{resistance}}$$




$$I = \frac{E}{R} \quad (\text{amperes, A})$$


$$E = IR \quad (\text{volts, V})$$

$$R = \frac{E}{I} \quad (\text{ohms, } \Omega)$$
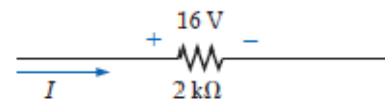
$$E = IR = (1.5 \text{ A})(80 \Omega) = 120 \text{ V}$$


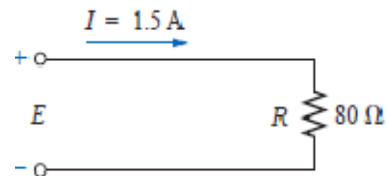
$$I = \frac{V}{R} = \frac{16 \text{ V}}{2 \times 10^3 \Omega} = 8 \text{ mA}$$



PLOTTING OHM'S LAW

If we write Ohm's law in the following manner and relate it to the basic straight-line equation



$$I = \frac{1}{R} \cdot E + 0$$

$$\begin{array}{cccc} \downarrow & \downarrow & \downarrow & \downarrow \\ y & = & m \cdot x & + b \end{array}$$

we find that the slope is equal to 1 divided by the resistance value, as indicated by the following:

$$m = \text{slope} = \frac{\Delta y}{\Delta x} = \frac{\Delta I}{\Delta V} = \frac{1}{R}$$

$$R = \frac{\Delta V}{\Delta I} \quad (\text{ohms})$$

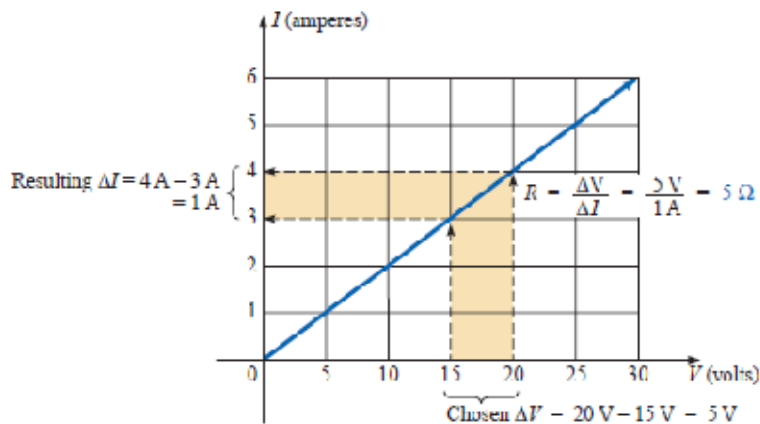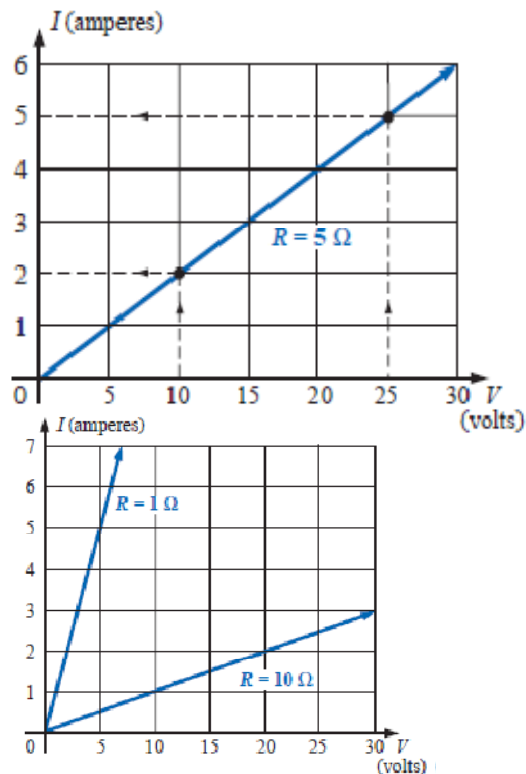

EXAMPLE 4.5 Determine the resistance associated with the curve of Fig. 4.9 using Eqs. (4.5) and (4.7), and compare results.

Solution: At $V = 6 \text{ V}$, $I = 3 \text{ mA}$, and

$$R_{dc} = \frac{V}{I} = \frac{6 \text{ V}}{3 \text{ mA}} = 2 \text{ k}\Omega$$

For the interval between 6 V and 8 V,

$$R = \frac{\Delta V}{\Delta I} = \frac{2 \text{ V}}{1 \text{ mA}} = 2 \text{ k}\Omega$$

The results are equivalent.

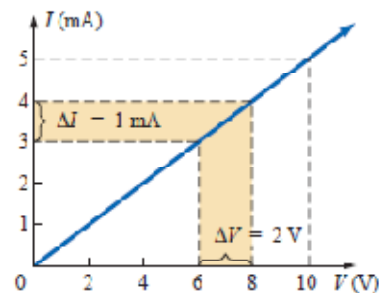


FIG. 4.9

Semiconductor diode characteristicAt $V = +1$ V,

$$R_{\text{diode}} = \frac{V}{I} = \frac{1 \text{ V}}{50 \text{ mA}} = \frac{1 \text{ V}}{50 \times 10^{-3} \text{ A}}$$

$$= 20 \Omega$$


(a relatively low value for most applications)

At $V = -1$ V,

$$R_{\text{diode}} = \frac{V}{I} = \frac{1 \text{ V}}{1 \mu\text{A}}$$

$$= 1 \text{ M}\Omega$$

(which is often represented by an open-circuit equivalent)

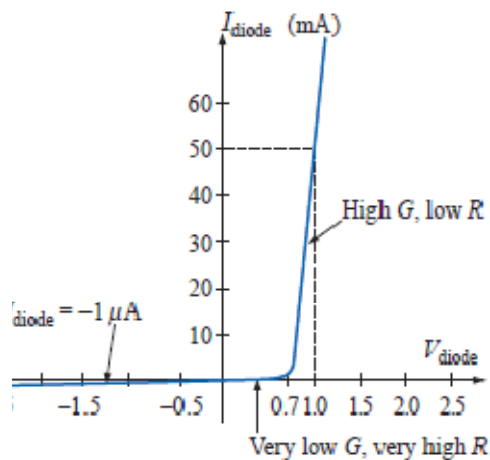**POWER**

Power is an indication of how much work (the conversion of energy from one form to another) can be done in a specified amount of time, that is, a *rate* of doing work.

$$1 \text{ watt (W)} = 1 \text{ joule/second (J/s)}$$

In equation form, power is determined by

$$P = \frac{W}{t} \quad (\text{watts, W, or joules/second, J/s})$$

$$1 \text{ horsepower} \cong 746 \text{ watts}$$

The power delivered to, or absorbed by, an electrical device or system can be found in terms of the current and voltage by first substituting Eq.

$$P = \frac{W}{t} = \frac{QV}{t} = V \frac{Q}{t}$$

But

$$I = \frac{Q}{t}$$

so that

$$P = VI \quad (\text{watts})$$

$$P = VI = V \left(\frac{V}{R} \right)$$

and

$$P = \frac{V^2}{R} \quad (\text{watts})$$

or

$$P = VI = (IR)I$$

and

$$P = I^2R \quad (\text{watts})$$

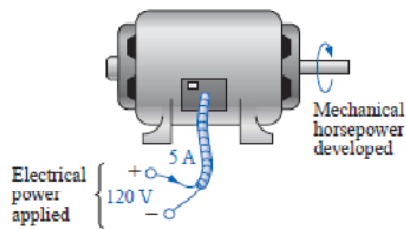


FIG. 4.14
Example 4.6.

EXAMPLE 4.6 Find the power delivered to the dc motor of Fig. 4.14.

Solution:

$$P = VI = (120 \text{ V})(5 \text{ A}) = 600 \text{ W} = 0.6 \text{ kW}$$

EXAMPLE 4.7 What is the power dissipated by a 5- Ω resistor if the current is 4 A?

Solution:

$$P = I^2R = (4 \text{ A})^2(5 \Omega) = 80 \text{ W}$$

Sometimes the power is given and the current or voltage must be determined. Through algebraic manipulations, an equation for each variable is derived as follows:

$$P = I^2R \Rightarrow I^2 = \frac{P}{R}$$

and

$$I = \sqrt{\frac{P}{R}} \quad (\text{amperes}) \quad (4.14)$$

$$P = \frac{V^2}{R} \Rightarrow V^2 = PR$$

and

$$V = \sqrt{PR} \quad (\text{volts}) \quad (4.15)$$

EXAMPLE Determine the current through a 5-k Ω resistor when the power dissipated by the element is 20 mW.

Solution

$$\begin{aligned} I &= \sqrt{\frac{P}{R}} = \sqrt{\frac{20 \times 10^{-3} \text{ W}}{5 \times 10^3 \Omega}} = \sqrt{4 \times 10^{-6}} = 2 \times 10^{-3} \text{ A} \\ &= 2 \text{ mA} \end{aligned}$$

EFFICIENCY

Conservation of energy requires that

Energy input (W_{in}) = energy output (W_{out}) + energy lost or stored in the system

Dividing both sides of the relationship by t gives

$$\frac{W_{\text{in}}}{t} = \frac{W_{\text{out}}}{t} + \frac{W_{\text{lost or stored by the system}}}{t}$$

Energy flow through a system.

Since $P = W/t$, we have the following:

$$P_i = P_o + P_{\text{lost or stored}}$$


The **efficiency** (η) of the system is then determined by the following equation:

$$\text{Efficiency} = \frac{\text{power output}}{\text{power input}}$$

$$\eta = \frac{P_o}{P_i} \quad (\text{decimal number})$$

$$\eta\% = \frac{P_o}{P_i} \times 100\% \quad (\text{percent})$$
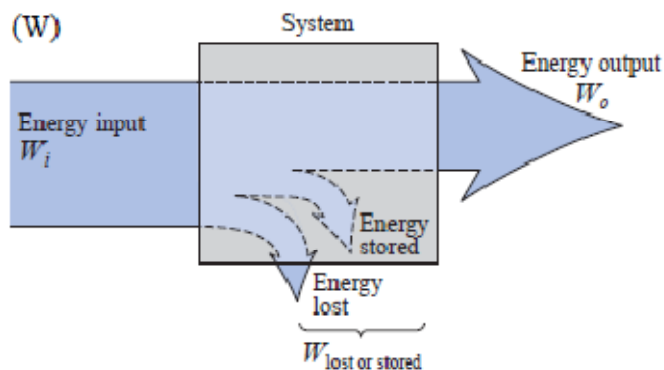
$$\eta\% = \frac{W_o}{W_i} \times 100\% \quad (\text{percent})$$



EXAMPLE A 2-hp motor operates at an efficiency of 75%. What is the power input in watts? If the applied voltage is 220 V, what is the input current?

$$\eta\% = \frac{P_o}{P_i} \times 100\% \quad \text{and} \quad P_i = \frac{1492 \text{ W}}{0.75} = 1989.33 \text{ W}$$

$$0.75 = \frac{(2 \text{ hp})(746 \text{ W/hp})}{P_i} \quad P_i = EI \quad \text{or} \quad I = \frac{P_i}{E} = \frac{1989.33 \text{ W}}{220 \text{ V}} = 9.04 \text{ A}$$

EXAMPLE 4.11 What is the output in horsepower of a motor with an efficiency of 80% and an input current of 8 A at 120 V?

Solution:

$$\eta\% = \frac{P_o}{P_i} \times 100\%$$


$$0.80 = \frac{P_o}{(120 \text{ V})(8 \text{ A})}$$

and $P_o = (0.80)(120 \text{ V})(8 \text{ A}) = 768 \text{ W}$

with $768 \text{ W} \left(\frac{1 \text{ hp}}{746 \text{ W}} \right) = 1.029 \text{ hp}$

Efficiency for Cascade Systems
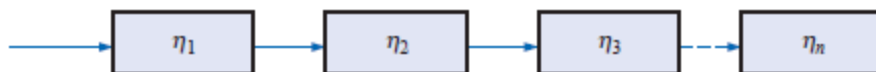
$$\eta_1 = \frac{P_{o1}}{P_{i1}} \quad \eta_2 = \frac{P_{o2}}{P_{i2}} \quad \eta_3 = \frac{P_{o3}}{P_{i3}}$$



If we form the product of these three efficiencies,

$$\eta_1 \cdot \eta_2 \cdot \eta_3 = \frac{P_{o1}}{P_{i1}} \cdot \frac{P_{o2}}{P_{i2}} \cdot \frac{P_{o3}}{P_{i3}}$$

and substitute the fact that $P_{i2} = P_{o1}$ and $P_{i3} = P_{o2}$, we find that the quantities indicated above will cancel, resulting in P_{o3}/P_{i1} , which is a measure of the efficiency of the entire system. In general, for the representative cascaded system of Fig. 4.20,

$$\eta_{\text{total}} = \eta_1 \cdot \eta_2 \cdot \eta_3 \cdots \eta_n$$

(4.20)

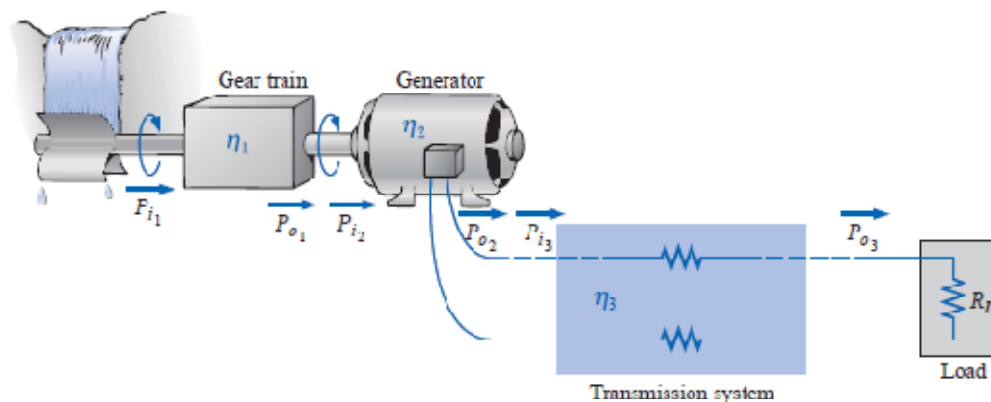


FIG. 4.19

Basic components of a generating system.

EXAMPLE 4.13 Find the overall efficiency of the system of Fig. 4.19 if $\eta_1 = 90\%$, $\eta_2 = 85\%$, and $\eta_3 = 95\%$.

Solution:

$$\eta_T = \eta_1 \cdot \eta_2 \cdot \eta_3 = (0.90)(0.85)(0.95) = 0.727, \text{ or } 72.7\%$$

Energy

$$\text{Energy (Wh)} = \text{power (W)} \times \text{time (h)}$$

$$\text{Energy (kWh)} = \frac{\text{power (W)} \times \text{time (h)}}{1000}$$

EXAMPLE 4.16 How much energy (in kilowatt-hours) is required to light a 60-W bulb continuously for 1 year (365 days)?

Solution:

$$\begin{aligned} W &= \frac{Pt}{1000} = \frac{(60 \text{ W})(24 \text{ h/day})(365 \text{ days})}{1000} = \frac{525,600 \text{ Wh}}{1000} \\ &= 525.60 \text{ kWh} \end{aligned}$$

EXAMPLE 4.17 How long can a 205-W television set be on before using more than 4 kWh of energy?

Solution:

$$\begin{aligned} W &= \frac{Pt}{1000} \Rightarrow t \text{ (hours)} = \frac{(W)(1000)}{P} \\ &= \frac{(4 \text{ kWh})(1000)}{205 \text{ W}} = 19.51 \text{ h} \end{aligned}$$

TABLE 4.1

Typical wattage ratings of some common household items.

| Appliance | Wattage Rating | Appliance | Wattage Rating |
|--------------------------|----------------|----------------------------------|----------------------------------|
| Air conditioner | 860 | Lap-top computer: | |
| Blow dryer | 1,300 | Sleep | < 1 W (Typically 0.3 W to 0.5 W) |
| Cassette player/recorder | 5 | Normal | 10–20 W |
| Cellular phone: | | High | 25–35 W |
| Standby | ≈ 35 mW | Microwave oven | 1,200 |
| Talk | ≈ 4.3 W | Pager | 1–2 mW |
| Clock | 2 | Phonograph | 75 |
| Clothes dryer (electric) | 4,800 | Projector | 1,200 |
| Coffee maker | 900 | Radio | 70 |
| Dishwasher | 1,200 | Range (self-cleaning) | 12,200 |
| Fan: | | Refrigerator (automatic defrost) | 1,800 |
| Portable | 90 | Shaver | 15 |
| Window | 200 | Stereo equipment | 110 |
| Heater | 1,322 | Sun lamp | 280 |
| Heating equipment: | | Toaster | 1,200 |
| Furnace fan | 320 | Trash compactor | 400 |
| Oil-burner motor | 230 | TV (color) | 200 |
| Iron, dry or steam | 1,100 | Videocassette recorder | 110 |
| | | Washing machine | 500 |
| | | Water heater | 4,500 |

Courtesy of General Electric Co.

Problems in pages 125-----126 → the reference is Boylestad

SERIES CIRCUITS


Two elements are in series if

1. *They have only one terminal in common (i.e., one lead of one is connected to only one lead of the other).*
2. *The common point between the two elements is not connected to another current-carrying element.*

The total resistance of a series circuit is the sum of the resistance levels.


$$R_T = R_1 + R_2 + R_3 + \cdots + R_N \quad (\text{ohms, } \Omega)$$
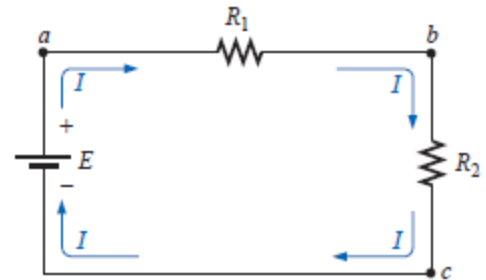
$$I_s = \frac{E}{R_T} \quad (\text{amperes, A})$$



$$V_1 = IR_1, V_2 = IR_2, V_3 = IR_3, \dots, V_N = IR_N \quad (\text{volts, V})$$
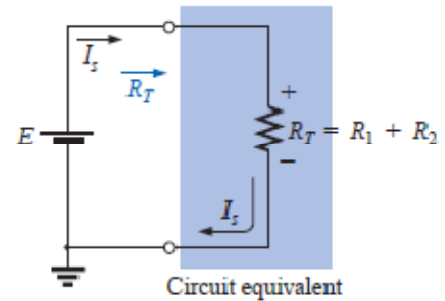
$$P_1 = V_1 I_1 = I_1^2 R_1 = \frac{V_1^2}{R_1} \quad (\text{watts, W})$$



The power delivered by the source is

$$P_{\text{del}} = EI \quad (\text{watts, W})$$

The total power delivered to a resistive circuit is equal to the total power dissipated by the resistive elements.

That is,

$$P_{\text{del}} = P_1 + P_2 + P_3 + \cdots + P_N$$

EXAMPLE 5.1

- Find the total resistance for the series circuit of Fig. 5.7.
- Calculate the source current I_s .
- Determine the voltages V_1 , V_2 , and V_3 .
- Calculate the power dissipated by R_1 , R_2 , and R_3 .
- Determine the power delivered by the source, and compare it to the sum of the power levels of part (d).

Solutions:

$$a. R_T = R_1 + R_2 + R_3 = 2 \Omega + 1 \Omega + 5 \Omega = 8 \Omega$$

$$b. I_s = \frac{E}{R_T} = \frac{20 \text{ V}}{8 \Omega} = 2.5 \text{ A}$$

$$c. V_1 = IR_1 = (2.5 \text{ A})(2 \Omega) = 5 \text{ V}$$

$$V_2 = IR_2 = (2.5 \text{ A})(1 \Omega) = 2.5 \text{ V}$$

$$V_3 = IR_3 = (2.5 \text{ A})(5 \Omega) = 12.5 \text{ V}$$

$$d. P_1 = V_1 I_1 = (5 \text{ V})(2.5 \text{ A}) = 12.5 \text{ W}$$

$$P_2 = I_2^2 R_2 = (2.5 \text{ A})^2 (1 \Omega) = 6.25 \text{ W}$$

$$P_3 = V_3^2 / R_3 = (12.5 \text{ V})^2 / 5 \Omega = 31.25 \text{ W}$$

$$e. P_{\text{del}} = EI = (20 \text{ V})(2.5 \text{ A}) = 50 \text{ W}$$

$$P_{\text{del}} = P_1 + P_2 + P_3$$

$$50 \text{ W} = 12.5 \text{ W} + 6.25 \text{ W} + 31.25 \text{ W}$$

$$50 \text{ W} = 50 \text{ W} \quad (\text{checks})$$

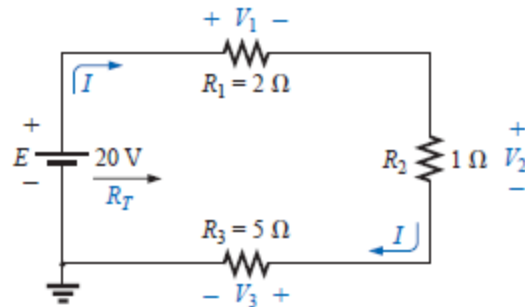


FIG. 5.7
Example 5.1.

EXAMPLE 5.2 Determine R_T , I , and V_2 for the circuit of Fig. 5.8.

Solution: Note the current direction as established by the battery and the polarity of the voltage drops across R_2 as determined by the current direction. Since $R_1 = R_3 = R_4$,

$$R_T = 3R_1 + R_2 = (3)(7 \Omega) + 4 \Omega = 21 \Omega + 4 \Omega = 25 \Omega$$

$$I = \frac{E}{R_T} = \frac{50 \text{ V}}{25 \Omega} = 2 \text{ A}$$

$$V_2 = IR_2 = (2 \text{ A})(4 \Omega) = 8 \text{ V}$$

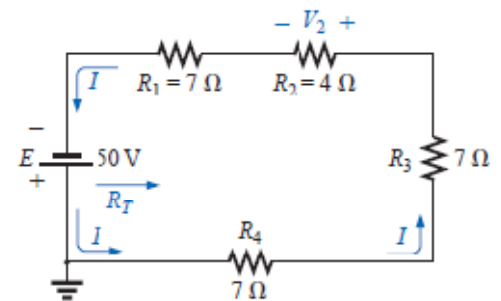


FIG. 5.8
Example 5.2.

EXAMPLE 5.3 Given R_T and I , calculate R_1 and E for the circuit of Fig. 5.9.

$$R_T = R_1 + R_2 + R_3$$

$$12 \text{ k}\Omega = R_1 + 4 \text{ k}\Omega + 6 \text{ k}\Omega$$

$$R_1 = 12 \text{ k}\Omega - 10 \text{ k}\Omega = 2 \text{ k}\Omega$$

$$E = IR_T = (6 \times 10^{-3} \text{ A})(12 \times 10^3 \Omega) = 72 \text{ V}$$

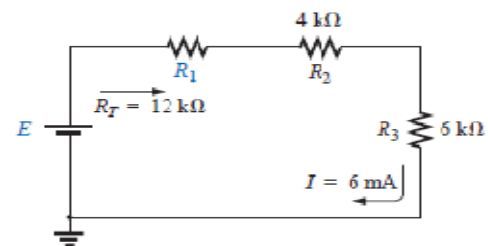
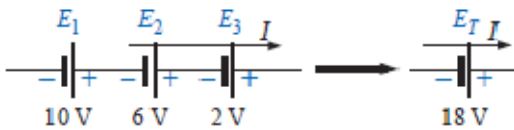


FIG. 5.9
Example 5.3.

VOLTAGE SOURCES IN SERIES

$$E_T = E_1 + E_2 + E_3 = 10\text{ V} + 6\text{ V} + 2\text{ V} = 18\text{ V}$$


KIRCHHOFF'S VOLTAGE LAW

Kirchhoff's voltage law (KVL) states that the algebraic sum of the potential rises and drops around a closed loop (or path) is zero.

$$\sum_{\text{C}} V = 0 \quad (\text{Kirchhoff's voltage law in symbolic form})$$


$$+E - V_1 - V_2 = 0$$

$$E = V_1 + V_2$$


revealing that

the applied voltage of a series circuit equals the sum of the voltage drops across the series elements.
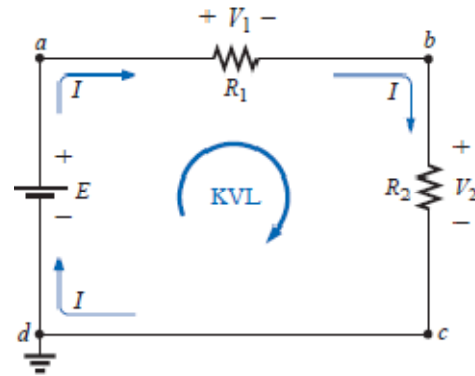
$$\sum_{\text{C}} V_{\text{rises}} = \sum_{\text{C}} V_{\text{drops}}$$




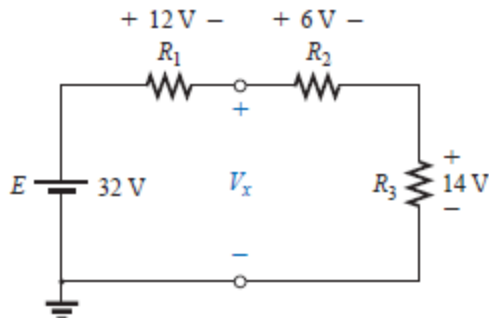Example/ Determine the unknown voltages for the networks



$$+E - V_1 - V_x = 0$$
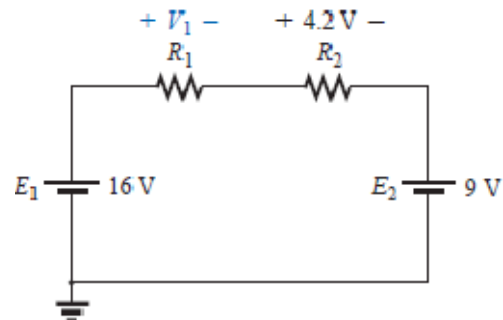
$$V_x = E - V_1 = 32\text{ V} - 12\text{ V} \\ = 20\text{ V}$$



$$+E_1 - V_1 - V_2 - E_2 = 0$$

$$V_1 = E_1 - V_2 - E_2 = 16\text{ V} - 4.2\text{ V} - 9\text{ V} \\ = 2.8\text{ V}$$

Example: For the following circuit diagram, Find I using:-


- Ohm's law.
- K.V.L.

E-Eng. Fundamentals

Solution:

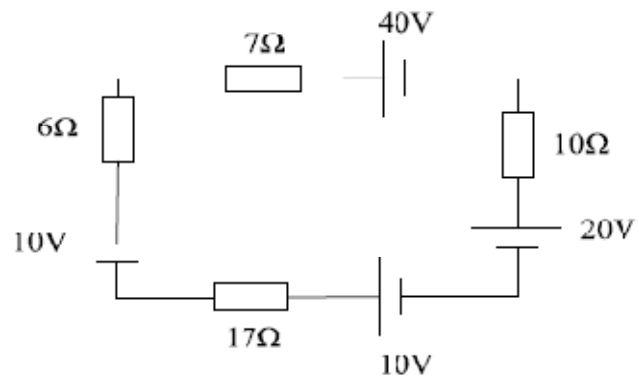a) By applying ohm's law :-

$$I = \frac{E_T}{R} = \frac{20 + 40 - 10 - 10}{10 + 7 + 6 + 17} = \frac{40}{40} = 1A$$




b) By applying K.V.L. :-

$$10 + 6I + 7I - 40 + 10I - 20 + 10 + 17I = 0$$

$$10 - 40 - 20 + 10 + I(6 + 7 + 10 + 17) = 0$$


$$-40 = -I(40) \Rightarrow I = \frac{40}{40} = 1A$$

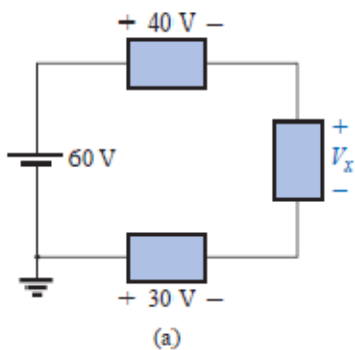EXAMPLE 5.6 Using Kirchhoff's voltage law, determine the unknown voltages for the network of Fig. 5.16.



$$60V - 40V - V_x + 30V = 0$$
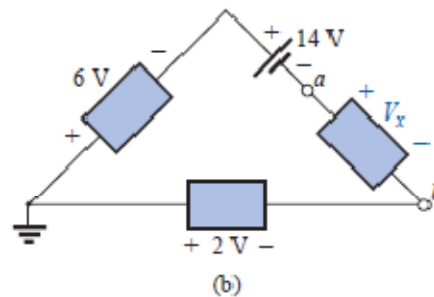
$$V_x = 60V + 30V - 40V = 90V - 40V = 50V$$



$$-6V - 14V - V_x + 2V = 0$$


$$V_x = -20V + 2V = -18V$$

Example :- For the following circuit diagram, find the current ?


Take the loop FABCDEF

$$+8 + V - 15 = 0 \Rightarrow +V - 7 = 0 \Rightarrow V = +7 \text{ volt}$$
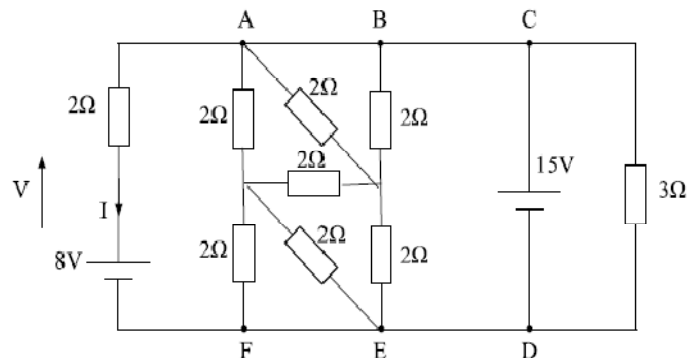
$$V = IR \Rightarrow I = \frac{7}{2} = 3.5A$$



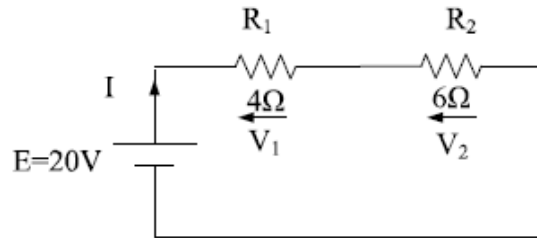Example :- For the following circuit diagram , find ; R_T , I , V_1 , V_2 , $P_{4\Omega}$, $P_{6\Omega}$, P_E , verify by K.V.L. ?



Solution :-

$$R_T = R_1 + R_2 = 4 + 6 = 10$$

$$I = \frac{E}{R_T} = \frac{20}{10} = 2A$$

$$V_1 = IR_1 = 2 \times 4 = 8V$$

$$V_2 = IR_2 = 2 \times 6 = 12V$$

$$P_{4\Omega} = I^2 R_1 = (2)^2 \times 4 = 16W \quad ; \quad \text{or} \quad P_{4\Omega} = \frac{V_1^2}{R_1} = \frac{(8)^2}{4} = 16W$$

$$P_{6\Omega} = I^2 R_2 = (2)^2 \times 6 = 24W \quad ; \quad \text{or} \quad P_{6\Omega} = \frac{V_2^2}{R_2} = \frac{(12)^2}{6} = 24W$$

$$P_E = IE = 2 \times 20 = 40W \quad ; \quad \text{or} \quad P_E = P_{4\Omega} + P_{6\Omega} = 16 + 24 = 40W$$

To verify results by using K.V.L. ; then

$$\sum_{i=1}^N V_i = 0$$

$$E - V_1 - V_2 = 0$$

$$E = V_1 + V_2$$

$$20 = 8 + 12$$

$$20 = 20 \quad \text{checks}$$

VOLTAGE DIVIDER RULE

In a series circuit,
the voltage across the resistive elements will divide as the magnitude of the resistance levels.

$$R_T = R_1 + R_2$$

and

$$I = \frac{E}{R_T}$$

Applying Ohm's law:


$$V_1 = IR_1 = \left(\frac{E}{R_T}\right)R_1 = \frac{R_1 E}{R_T}$$

with

$$V_2 = IR_2 = \left(\frac{E}{R_T}\right)R_2 = \frac{R_2 E}{R_T}$$

Note that the format for V_1 and V_2 is

$$V_x = \frac{R_x E}{R_T} \quad (\text{voltage divider rule})$$

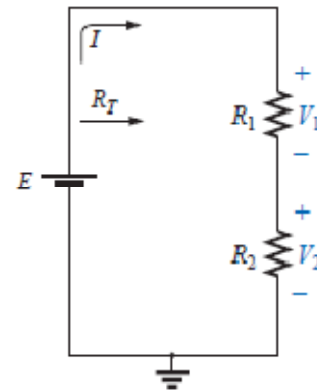

EXAMPLE 5.10 Determine the voltage V_1 for the network of Fig. 5.27.

Solution: Eq. (5.10):

$$V_1 = \frac{R_1 E}{R_T} = \frac{R_1 E}{R_1 + R_2} = \frac{(20 \Omega)(64 \text{ V})}{20 \Omega + 60 \Omega} = \frac{1280 \text{ V}}{80} = 16 \text{ V}$$

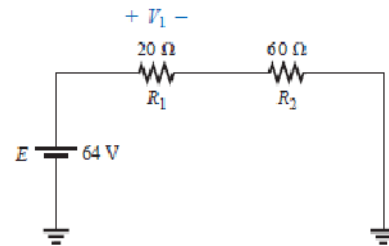


FIG. 5.27
Example 5.10.

EXAMPLE 5.11 Using the voltage divider rule, determine the voltages V_1 and V_3 for the series circuit of Fig. 5.28.

Solution:

$$\begin{aligned} V_1 &= \frac{R_1 E}{R_T} = \frac{(2 \text{ k}\Omega)(45 \text{ V})}{2 \text{ k}\Omega + 5 \text{ k}\Omega + 8 \text{ k}\Omega} = \frac{(2 \text{ k}\Omega)(45 \text{ V})}{15 \text{ k}\Omega} \\ &= \frac{(2 \times 10^3 \Omega)(45 \text{ V})}{15 \times 10^3 \Omega} = \frac{90 \text{ V}}{15} = 6 \text{ V} \\ V_3 &= \frac{R_3 E}{R_T} = \frac{(8 \text{ k}\Omega)(45 \text{ V})}{15 \text{ k}\Omega} = \frac{(8 \times 10^3 \Omega)(45 \text{ V})}{15 \times 10^3 \Omega} \\ &= \frac{360 \text{ V}}{15} = 24 \text{ V} \end{aligned}$$

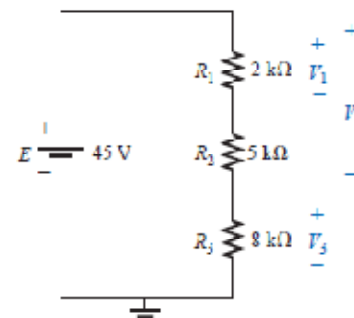


FIG. 5.28
Example 5.11.

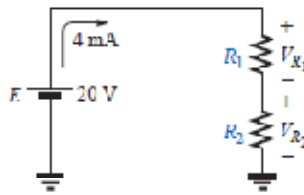


FIG. 5.30
Example 5.13.

EXAMPLE 5.13 Design the voltage divider of Fig. 5.30 such that $V_{R_1} = 4V_{R_2}$.

Solution: The total resistance is defined by

$$R_T = \frac{E}{I} = \frac{20 \text{ V}}{4 \text{ mA}} = 5 \text{ k}\Omega$$

Since $V_{R_1} = 4V_{R_2}$,

$$R_1 = 4R_2$$

Thus

$$R_T = R_1 + R_2 = 4R_2 + R_2 = 5R_2$$

and

$$5R_2 = 5 \text{ k}\Omega$$

$$R_2 = 1 \text{ k}\Omega$$

and

$$R_1 = 4R_2 = 4 \text{ k}\Omega$$

Voltage Sources and Ground

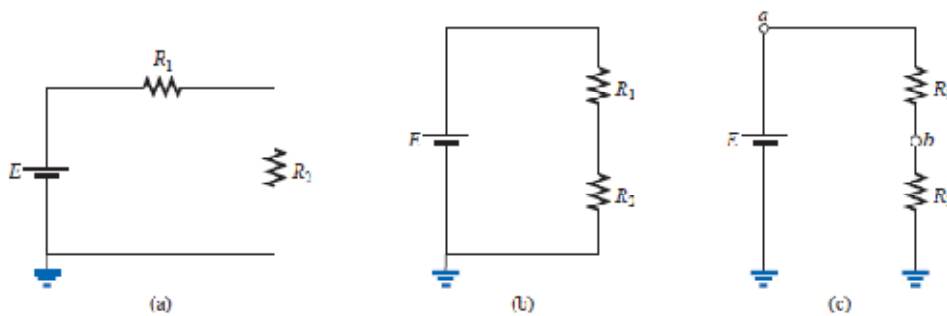


FIG. 5.32

Three ways to sketch the same series dc circuit.

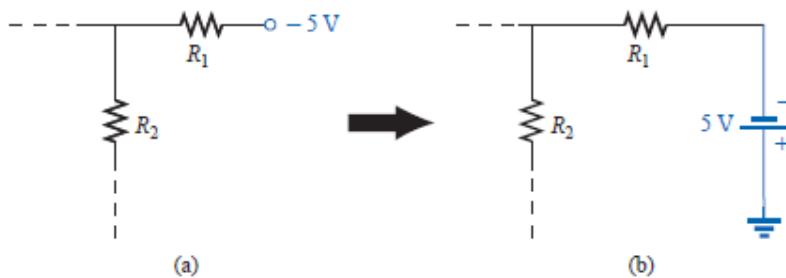


FIG. 5.34

Replacing the notation for a negative dc supply with the standard notation.

EXAMPLE 5.20 For the network of Fig. 5.50:

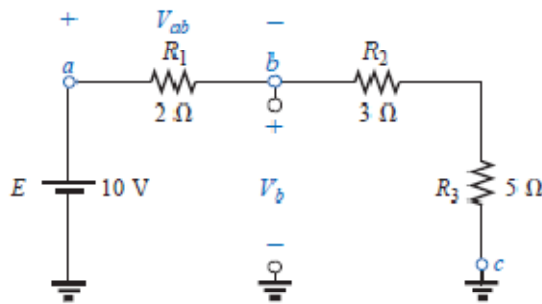


FIG. 5.50
Example 5.20.

- Calculate V_{ab} .
- Determine V_b .
- Calculate V_c .

Solutions:

- a. Voltage divider rule:

$$V_{ab} = \frac{R_1 E}{R_T} = \frac{(2 \Omega)(10 \text{ V})}{2 \Omega + 3 \Omega + 5 \Omega} = +2 \text{ V}$$

- b. Voltage divider rule:

$$V_b = V_{R_2} + V_{R_3} = \frac{(R_2 + R_3)E}{R_T} = \frac{(3 \Omega + 5 \Omega)(10 \text{ V})}{10 \Omega} = 8 \text{ V}$$

$$\text{or } V_b = V_a - V_{ab} = E - V_{ab} = 10 \text{ V} - 2 \text{ V} = 8 \text{ V}$$

- c. $V_c = \text{ground potential} = 0 \text{ V}$

EXAMPLE 5.19 Using the voltage divider rule, determine the voltages V_1 and V_2 of Fig. 5.48.

Solution: Redrawing the network with the standard battery symbol will result in the network of Fig. 5.49. Applying the voltage divider rule,

$$V_1 = \frac{R_1 E}{R_1 + R_2} = \frac{(4 \Omega)(24 \text{ V})}{4 \Omega + 2 \Omega} = 16 \text{ V}$$

$$V_2 = \frac{R_2 E}{R_1 + R_2} = \frac{(2 \Omega)(24 \text{ V})}{4 \Omega + 2 \Omega} = 8 \text{ V}$$

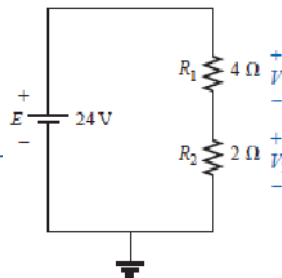


FIG. 5.49

Circuit of Fig. 5.48 redrawn.

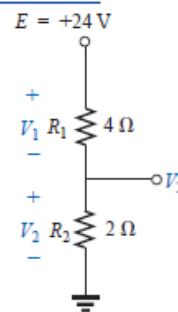


FIG. 5.48