
The Laplace Transform in Circuit Analysis

Reference:

Electric Circuits

James W. Nilsson & Susan A. Riedel

Objectives

- Be able to transform a circuit into the s domain using Laplace transforms.
- Know how to analyze a circuit in the s -domain and be able to transform an s -domain solution back to the time domain.
- Understand the definition and significance of the transfer function and be able to calculate the transfer function for a circuit using s -domain techniques.
- Know how to use a circuit's transfer function to calculate the circuit's unit impulse response, its unit step response, and its steady-state response to a sinusoidal input.

Outline

- Circuit elements in the s domain
- Circuit analysis in the s domain
- The transfer function
- The transfer function in partial fraction expansions
- The transfer function and the steady-state sinusoidal response

Circuit Elements in the s domain

Resistor in the s domain:

In time domain: $v = Ri$



In s domain: $V = RI$




where $V = L\{v\}$ and $I = L\{i\}$

Circuit Elements in the s domain

Inductor in the s domain:


In time domain:

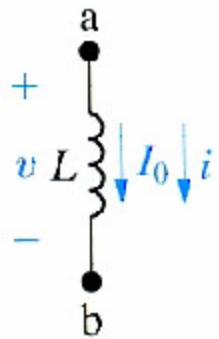

$$v = L \frac{di}{dt}$$



$$i = \frac{1}{L} \int_0^t v dx + I_0$$

In s domain:

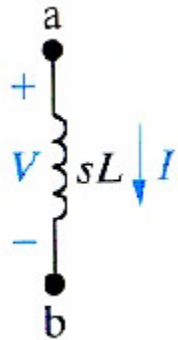

(initial current is 0)

$$V = L[sI - i(0^-)] = sLI - LI_0$$

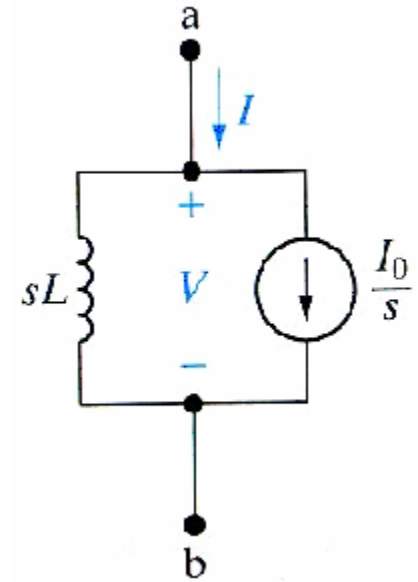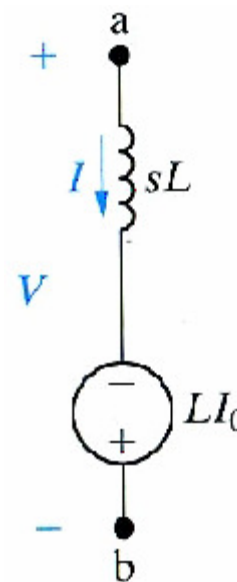


$$I = \frac{V + LI_0}{sL} = \frac{V}{sL} + \frac{I_0}{s}$$

Circuit Elements in the s domain

Capacitor in the s domain:


In time domain:

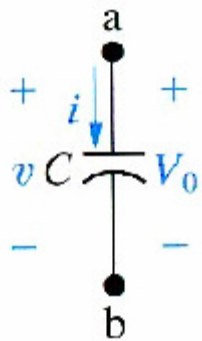

$$i = C \frac{dv}{dt}$$

$$v = \frac{1}{C} \int_0^t i dx + V_0$$

In s domain:


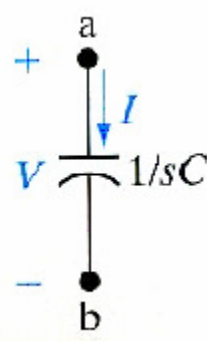


(initial voltage is 0)

$$I = C[sV - v(0^-)]$$

or

$$I = sCV - CV_0$$

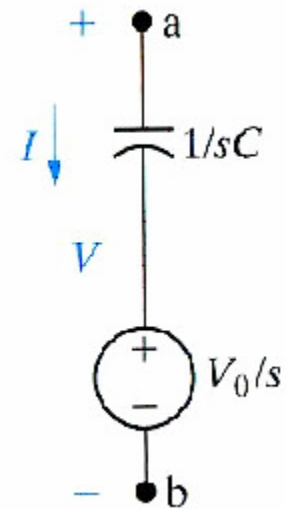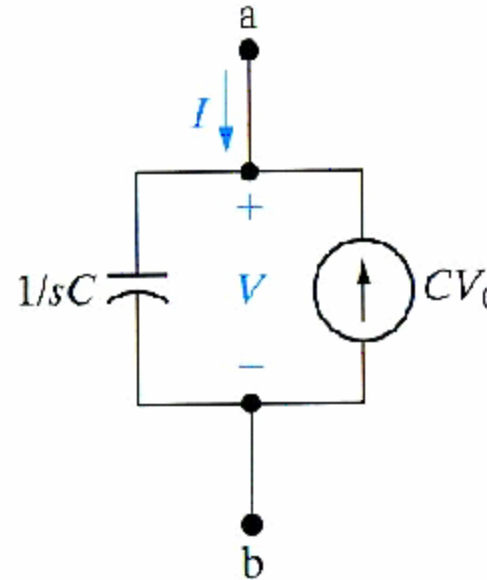

$$V = \left(\frac{1}{sC} \right) I + \frac{V_0}{s}$$

Example: natural response de RC circuit

Circuit analysis in the s domain

Ohm's Law:

$$V = ZI$$

Where Z refers to the s-domain impedance of the element.

- * Resistor has impedance of R ohms
- * Inductor has impedance of sL ohms
- * Capacitor has impedance of $1/sC$ ohms

Kirchhoff's Law:

$$\text{Algebraic } \Sigma I = 0$$

$$\text{Algebraic } \Sigma V = 0$$

Transfer function

The transfer function is defined as the s-domain ratio of the Laplace transform of the output (response) to the Laplace transform of the input (source):

$$H(s) = \frac{Y(s)}{X(s)}$$


$Y(s)$ is the Laplace transform of the output signal

$X(s)$ is the Laplace transform of the input signal

Transfer function

- In computing the transfer function, we restrict our attention to circuits where all initial conditions are zero.
- If a circuit has multiple independent sources, find the transfer function for each source and use superposition to find the response to all sources
- A single circuit can generate many transfer function

Example

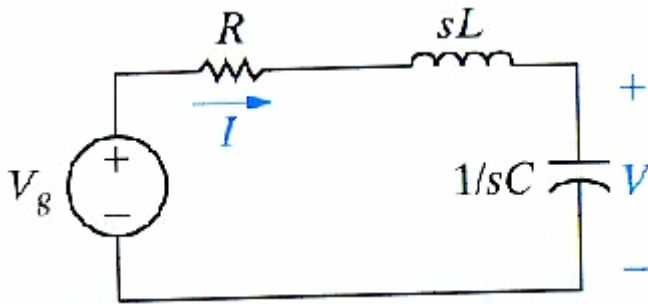

$$H(s) = \frac{I}{V_g} = \frac{V_g}{R + sL + 1/sC} \cdot \frac{1}{V_g} = \frac{sC}{s^2LC + sRC + 1}$$

$$H(s) = \frac{V}{V_g} = \frac{1}{s^2LC + sRC + 1}$$

Transfer function

The location of poles and zeros of $H(s)$

For a linear lumped-parameter circuits:



- $H(s)$ is always a rational function of s .
 - Complex poles and zeros always appear in conjugate pairs.
 - The poles of $H(s)$ must lie in the left half of the s plane.
 - The zeros of $H(s)$ may be lie in either the right half or the left half of the s plane
-

Transfer function in partial fraction expansions

$$Y(s) = H(s)X(s)$$

- Expanding the right-hand side into a sum of partial fractions produces a term for each pole of $H(s)$ and $X(s)$.
- The terms generated by the poles of $H(s)$ give rise to the transient component of the total response.
- The terms generated by the poles of $X(s)$ give rise to the steady-state component of the response.

Example

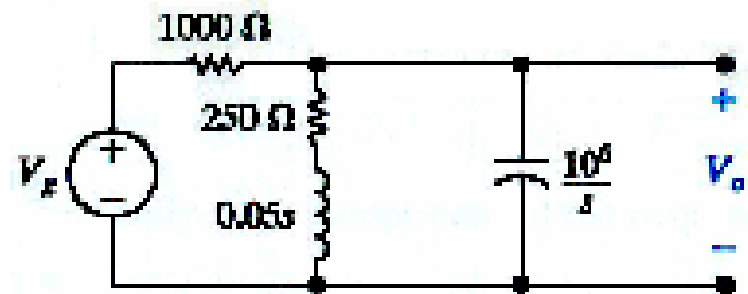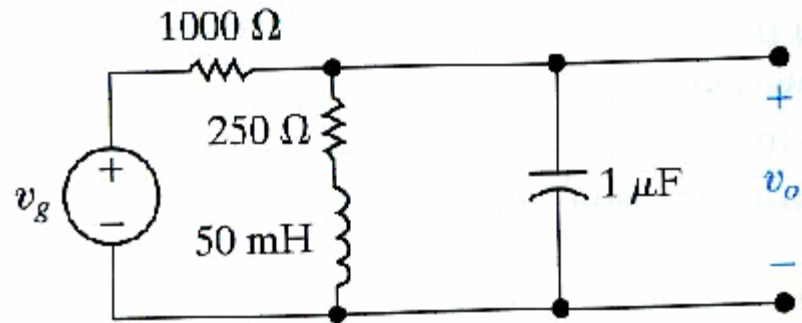

Transfer function:

$$H(s) = \frac{V_o}{V_g} = \frac{1000(s + 5000)}{s^2 + 6000s + 25 \times 10^6}$$

Transfer function and the steady-state response

Given sinusoidal source:

$$x(t) = A \cos(\omega t + \phi)$$

In s domain:

$$X(s) = \frac{A(s \cos \phi - \omega \sin \phi)}{s^2 + \omega^2} = \frac{K_1}{s - j\omega} + \frac{K_1^*}{s + j\omega}$$

$$K_1 = \frac{A}{2} |H(j\omega)| e^{j[\theta(\omega) + \phi]}$$

Transfer function:

$$H(j\omega) = |H(j\omega)| e^{j\theta(\omega)}$$

Transfer function and the steady-state response

The steady state response:

$$y_{ss}(t) = A|H(j\omega)|\cos[\omega t + \phi + \theta(\omega)]$$

- The amplitude of the response equals the amplitude of the source multiplied by the magnitude of the transfer function.
 - The phase angle of the response equals the phase angle of the source plus the phase angle of the transfer function.
-